


<p>This hardware is released under Creative Commons Share-alike 4.0 International (<a href="http://creativecommons.org/licenses/by-sa/4.0/">http://creativecommons.org/licenses/by-sa/4.0/</a>).</p> <p>Note: This is a human-readable summary of (and not a substitute for) the license (<a href="http://creativecommons.org/licenses/by-sa/4.0/legalcode">http://creativecommons.org/licenses/by-sa/4.0/legalcode</a>).</p> <p>You are free to:</p> <p>Share — copy and redistribute the material in any medium or format</p> <p>Adapt — remix, transform, and build upon the material for any purpose, even commercially.</p> <p>The licensor cannot revoke these freedoms as long as you follow the license terms.</p> <p>Under the following terms:</p> <p>Attribution — You must give appropriate credit, provide a link to the license, and indicate if changes were made. You may do so in any reasonable manner, but not in any way that suggests the licensor endorses you or your use.</p> <p>ShareAlike — If you remix, transform, or build upon the material, you must distribute your contributions under the same license as the original.</p> <p>No additional restrictions — You may not apply legal terms or technological measures that legally restrict others from doing anything the license permits.</p> <p>Notices:</p> <p>You do not have to comply with the license for elements of the material in the public domain or where your use is permitted by an applicable exception or limitation.</p> <p>No warranties are given. The license may not give you all of the permissions necessary for your intended use. For example, other rights such as publicity, privacy, or moral rights may limit how you use the material.</p>	DOC.NR.	STATUS	DESCRIPTION
	26.001.00.00.01	FINAL	Pre-amplifier - Frequency response
	26.001.00.01.01	FINAL	Pre-amplifier - Transient response (31.5 Hz)
	26.001.00.01.02	FINAL	Pre-amplifier - Transient response (16 kHz)
	26.001.00.01.03	FINAL	Pre-amplifier - Transient response (1 kHz)
	26.002.00.00.01	FINAL	31.5 Hz Band-pass Filter - Frequency response
	26.002.00.01.01	FINAL	31.5 Hz Band-pass Filter - Transient response (31.5 Hz)
	26.002.00.01.02	FINAL	31.5 Hz Band-pass Filter - Transient response (16 kHz)
	26.002.00.02.01	FINAL	31.5 Hz Band-pass Filter - Transient response (31.5 Hz)
	26.002.00.02.02	FINAL	31.5 Hz Band-pass Filter - Transient response (16 kHz)
	26.002.00.03.01	FINAL	31.5 Hz Band-pass Filter - Transient response (31.5 Hz)
	26.002.00.03.02	FINAL	31.5 Hz Band-pass Filter - Transient response (16 kHz)
	26.003.00.00.01	FINAL	31.5 Hz Detector - Frequency response
	26.003.00.01.01	FINAL	31.5 Hz Detector - Transient response (31.5 Hz)
	26.003.00.02.01	FINAL	31.5 Hz Detector - Transient response (31.5 Hz)
	26.003.00.03.01	FINAL	31.5 Hz Detector - Transient response (31.5 Hz)
	26.004.00.00.01	FINAL	63 Hz Band-pass Filter - Frequency response
	26.004.00.01.01	FINAL	63 Hz Band-pass Filter - Transient response (63 Hz)
	26.004.00.01.01	FINAL	63 Hz Band-pass Filter - Transient response (63 Hz)
	26.004.00.01.02	FINAL	63 Hz Band-pass Filter - Transient response (16 kHz)
	26.004.00.02.01	FINAL	63 Hz Band-pass Filter - Transient response (63 Hz)
	26.004.00.02.02	FINAL	63 Hz Band-pass Filter - Transient response (16 kHz)
	26.004.00.03.01	FINAL	63 Hz Band-pass Filter - Transient response (63 Hz)
	26.004.00.03.02	FINAL	63 Hz Band-pass Filter - Transient response (16 kHz)
	26.005.00.00.01	FINAL	63 Hz Detector - Frequency response
	26.005.00.01.01	FINAL	63 Hz Detector - Transient response (63 Hz)
	26.005.00.02.01	FINAL	63 Hz Detector - Transient response (63 Hz)
	26.005.00.03.01	FINAL	63 Hz Detector - Transient response (63 Hz)
	26.006.00.00.01	FINAL	125 Hz Band-pass Filter - Frequency response
	26.006.00.01.01	FINAL	125 Hz Band-pass Filter - Transient response (125 Hz)
	26.006.00.01.02	FINAL	125 Hz Band-pass Filter - Transient response (16 kHz)
	26.006.00.02.01	FINAL	125 Hz Band-pass Filter - Transient response (125 Hz)
	26.006.00.02.02	FINAL	125 Hz Band-pass Filter - Transient response (16 kHz)
	26.006.00.03.01	FINAL	125 Hz Band-pass Filter - Transient response (125 Hz)
	OCTAVE_FILTER		
	TITLE Front Page		
	FILE: gnuicap/26.000.00.00.01.sch	REVISION: 20240607	A3
	PAGE 01 OF 01	DRAWN BY: Bert Timmerman	

DOC.NR.	STATUS	DESCRIPTION		DOC.NR.	STATUS	DESCRIPTION
26.006.00.03.02	FINAL	125 Hz Band-pass Filter – Transient response (16 kHz)		26.012.00.02.02	FINAL	1 kHz Band-pass Filter – Transient response (16 kHz)
26.007.00.00.01	FINAL	125 Hz Detector – Frequency response		26.012.00.02.03	FINAL	1 kHz Band-pass Filter – Transient response (31.5 Hz)
26.007.00.01.01	FINAL	125 Hz Detector – Transient response (125 Hz)		26.012.00.03.01	FINAL	1 kHz Band-pass Filter – Transient response (1 kHz)
26.007.00.01.01	FINAL	125 Hz Detector – Transient response (125 Hz)		26.012.00.03.02	FINAL	1 kHz Band-pass Filter – Transient response (16 kHz)
26.007.00.02.01	FINAL	125 Hz Detector – Transient response (125 Hz)		26.012.00.03.03	FINAL	1 kHz Band-pass Filter – Transient response (31.5 Hz)
26.007.00.03.01	FINAL	125 Hz Detector – Transient response (125 Hz)		26.013.00.00.01	FINAL	1 kHz Detector – Frequency response
26.008.00.00.01	FINAL	250 Hz Band-pass Filter – Frequency response		26.013.00.01.01	FINAL	1 kHz Detector – Transient response (1 kHz)
26.008.00.01.01	FINAL	250 Hz Band-pass Filter – Transient response (250 Hz)		26.013.00.02.01	FINAL	1 kHz Detector – Transient response (1 kHz)
26.008.00.01.02	FINAL	250 Hz Band-pass Filter – Transient response (16 kHz)		26.013.00.03.01	FINAL	1 kHz Detector – Transient response (1 kHz)
26.008.00.02.01	FINAL	250 Hz Band-pass Filter – Transient response (250 Hz)		26.014.00.00.01	FINAL	2 kHz Band-pass Filter – Frequency response
26.008.00.02.02	FINAL	250 Hz Band-pass Filter – Transient response (16 kHz)		26.014.00.01.01	FINAL	2 kHz Band-pass Filter – Transient response (2 kHz)
26.008.00.03.01	FINAL	250 Hz Band-pass Filter – Transient response (250 Hz)		26.014.00.01.02	FINAL	2 kHz Band-pass Filter – Transient response (16 kHz)
26.008.00.03.02	FINAL	250 Hz Band-pass Filter – Transient response (16 kHz)		26.014.00.01.03	FINAL	2 kHz Band-pass Filter – Transient response (31.5 Hz)
26.009.00.00.01	FINAL	250 Hz Detector – Frequency response		26.014.00.02.01	FINAL	2 kHz Band-pass Filter – Transient response (2 kHz)
26.009.00.01.01	FINAL	250 Hz Detector – Transient response (250 Hz)		26.014.00.02.02	FINAL	2 kHz Band-pass Filter – Transient response (16 kHz)
26.009.00.02.01	FINAL	250 Hz Detector – Transient response (250 Hz)		26.014.00.02.03	FINAL	2 kHz Band-pass Filter – Transient response (31.5 Hz)
26.009.00.03.01	FINAL	250 Hz Detector – Transient response (250 Hz)		26.014.00.03.01	FINAL	2 kHz Band-pass Filter – Transient response (2 kHz)
26.010.00.00.01	FINAL	500 Hz Band-pass Filter – Frequency response		26.014.00.03.02	FINAL	2 kHz Band-pass Filter – Transient response (16 kHz)
26.010.00.01.01	FINAL	500 Hz Band-pass Filter – Transient response (500 Hz)		26.014.00.03.03	FINAL	2 kHz Band-pass Filter – Transient response (31.5 Hz)
26.010.00.01.02	FINAL	500 Hz Band-pass Filter – Transient response (16 kHz)		26.015.00.00.01	FINAL	2 kHz Detector – Frequency response
26.010.00.02.01	FINAL	500 Hz Band-pass Filter – Transient response (500 Hz)		26.015.00.01.01	FINAL	2 kHz Detector – Transient response (2 kHz)
26.010.00.02.02	FINAL	500 Hz Band-pass Filter – Transient response (16 kHz)		26.015.00.02.01	FINAL	2 kHz Detector – Transient response (2 kHz)
26.010.00.03.01	FINAL	500 Hz Band-pass Filter – Transient response (500 Hz)		26.015.00.03.01	FINAL	2 kHz Detector – Transient response (2 kHz)
26.010.00.03.02	FINAL	500 Hz Band-pass Filter – Transient response (16 kHz)		26.016.00.00.01	FINAL	4 kHz Band-pass Filter – Frequency response
26.011.00.00.01	FINAL	500 Hz Detector – Frequency response		26.016.00.01.01	FINAL	4 kHz Band-pass Filter – Transient response (4 kHz)
26.011.00.01.01	FINAL	500 Hz Detector – Transient response (500 Hz)		26.016.00.01.02	FINAL	4 kHz Band-pass Filter – Transient response (16 kHz)
26.011.00.02.01	FINAL	500 Hz Detector – Transient response (500 Hz)		26.016.00.01.03	FINAL	4 kHz Band-pass Filter – Transient response (31.5 Hz)
26.011.00.03.01	FINAL	500 Hz Detector – Transient response (500 Hz)		26.016.00.02.01	FINAL	4 kHz Band-pass Filter – Transient response (4 kHz)
26.012.00.00.01	FINAL	1 kHz Band-pass Filter – Frequency response		26.016.00.02.02	FINAL	4 kHz Band-pass Filter – Transient response (16 kHz)
26.012.00.01.01	FINAL	1 kHz Band-pass Filter – Transient response (1 kHz)		26.016.00.02.03	FINAL	4 kHz Band-pass Filter – Transient response (31.5 Hz)
26.012.00.01.02	FINAL	1 kHz Band-pass Filter – Transient response (16 kHz)		26.016.00.03.01	FINAL	4 kHz Band-pass Filter – Transient response (4 kHz)
26.012.00.01.03	FINAL	1 kHz Band-pass Filter – Transient response (31.5 Hz)		26.016.00.03.02	FINAL	4 kHz Band-pass Filter – Transient response (16 kHz)
26.012.00.02.01	FINAL	1 kHz Band-pass Filter – Transient response (1 kHz)		26.016.00.03.03	FINAL	4 kHz Band-pass Filter – Transient response (31.5 Hz)
				OCTAVE_FILTER		
				TITLE Front Page		
				FILE: gnucap/26.000.00.00.02.sch	REVISION: 20240607	A3
				PAGE 01 OF 01	DRAWN BY: Bert Timmerman	

DOC.NR.	STATUS	DESCRIPTION				
26.017.00.00.01	FINAL	4 kHz Detector – Frequency response				
26.017.00.01.01	FINAL	4 kHz Detector – Transient response (4 kHz)				
26.017.00.02.01	FINAL	4 kHz Detector – Transient response (4 kHz)				
26.017.00.03.01	FINAL	4 kHz Detector – Transient response (4 kHz)				
26.018.00.00.01	FINAL	8 kHz Band–pass Filter – Frequency response				
26.018.00.01.01	FINAL	8 kHz Band–pass Filter – Transient response (8 kHz)				
26.018.00.01.02	FINAL	8 kHz Band–pass Filter – Transient response (16 kHz)				
26.018.00.01.03	FINAL	8 kHz Band–pass Filter – Transient response (31.5 Hz)				
26.018.00.02.01	FINAL	8 kHz Band–pass Filter – Transient response (8 kHz)				
26.018.00.02.02	FINAL	8 kHz Band–pass Filter – Transient response (16 kHz)				
26.018.00.02.03	FINAL	8 kHz Band–pass Filter – Transient response (31.5 Hz)				
26.018.00.03.01	FINAL	8 kHz Band–pass Filter – Transient response (8 kHz)				
26.018.00.03.02	FINAL	8 kHz Band–pass Filter – Transient response (16 kHz)				
26.018.00.03.03	FINAL	8 kHz Band–pass Filter – Transient response (31.5 Hz)				
26.019.00.00.01	FINAL	8 kHz Detector – Frequency response				
26.019.00.01.01	FINAL	8 kHz Detector – Transient response (8 kHz)				
26.019.00.02.01	FINAL	8 kHz Detector – Transient response (8 kHz)				
26.019.00.03.01	FINAL	8 kHz Detector – Transient response (8 kHz)				
26.020.00.00.01	FINAL	16 kHz Band–pass Filter – Frequency response				
26.020.00.01.01	FINAL	16 kHz Band–pass Filter – Transient response (16 kHz)				
26.020.00.01.02	FINAL	16 kHz Band–pass Filter – Transient response (31.5 Hz)				
26.020.00.02.01	FINAL	16 kHz Band–pass Filter – Transient response (16 kHz)				
26.020.00.02.02	FINAL	16 kHz Band–pass Filter – Transient response (31.5 Hz)				
26.020.00.03.01	FINAL	16 kHz Band–pass Filter – Transient response (16 kHz)				
26.020.00.03.02	FINAL	16 kHz Band–pass Filter – Transient response (31.5 Hz)				
26.021.00.00.01	FINAL	16 kHz Detector – Frequency response				
26.021.00.01.01	FINAL	16 kHz Detector – Transient response (16 kHz)				
26.021.00.02.01	FINAL	16 kHz Detector – Transient response (16 kHz)				
26.021.00.03.01	FINAL	16 kHz Detector – Transient response (16 kHz)				

.TITLE OCTAVE FILTER – FUNCTION 001: PRE-AMPLIFIER – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 0.1 100)  
C1 1 2 680n  
R1 0 2 100k  
R2 2 6 10K  
R3 3 7 47k  
R4 7 0 4700  
XOP1 6 7 0 4 5 3 UA741


.PRINT OP Iter(0) V(3)

.PRINT AC VDB(3)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.01 10Meg

.END

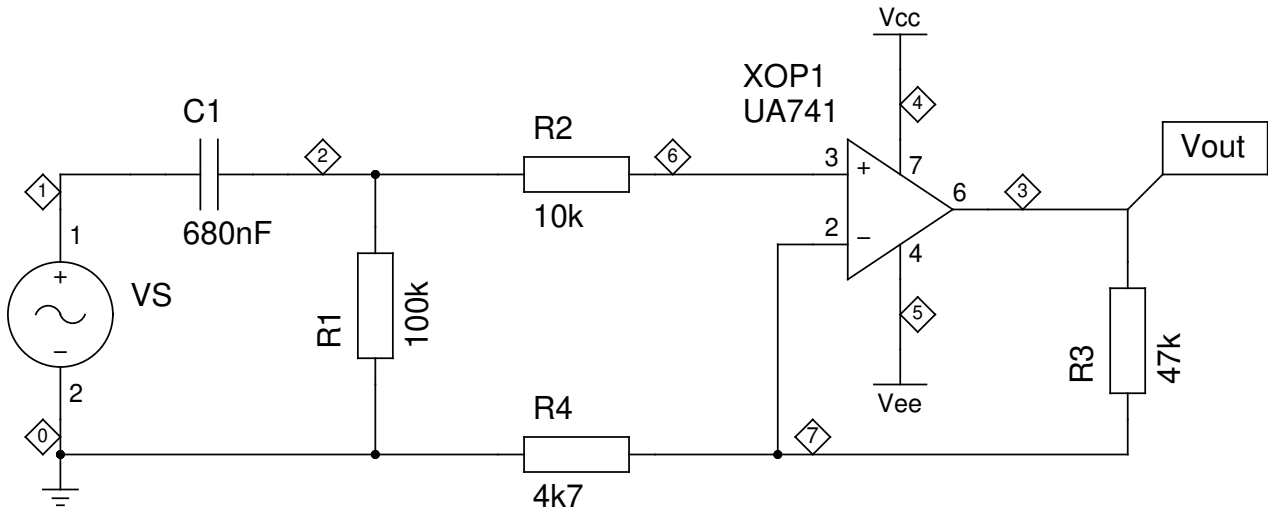

OCTAVE\_FILTER  
Pre-amplifier – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.001.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240524  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 001: PRE-AMPLIFIER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 0.141 31.5)  
C1 1 2 680n  
R1 0 2 100k  
R2 2 6 10K  
R3 3 7 47k  
R4 7 0 4700  
XOP1 6 7 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.4 0.00001 TRACE ALL

.END

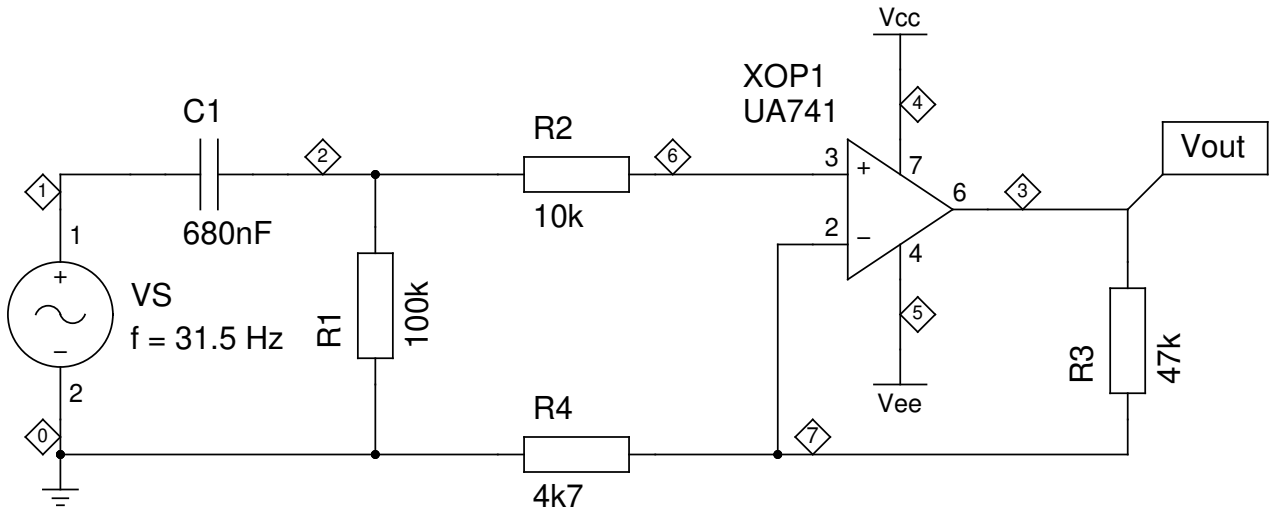

OCTAVE\_FILTER  
Pre-amplifier – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.001.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240524  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 001: PRE-AMPLIFIER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 0.141 16k)  
C1 1 2 680n  
R1 0 2 100k  
R2 2 6 10K  
R3 3 7 47k  
R4 7 0 4700  
XOP1 6 7 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.01 0.000001 TRACE ALL

.END

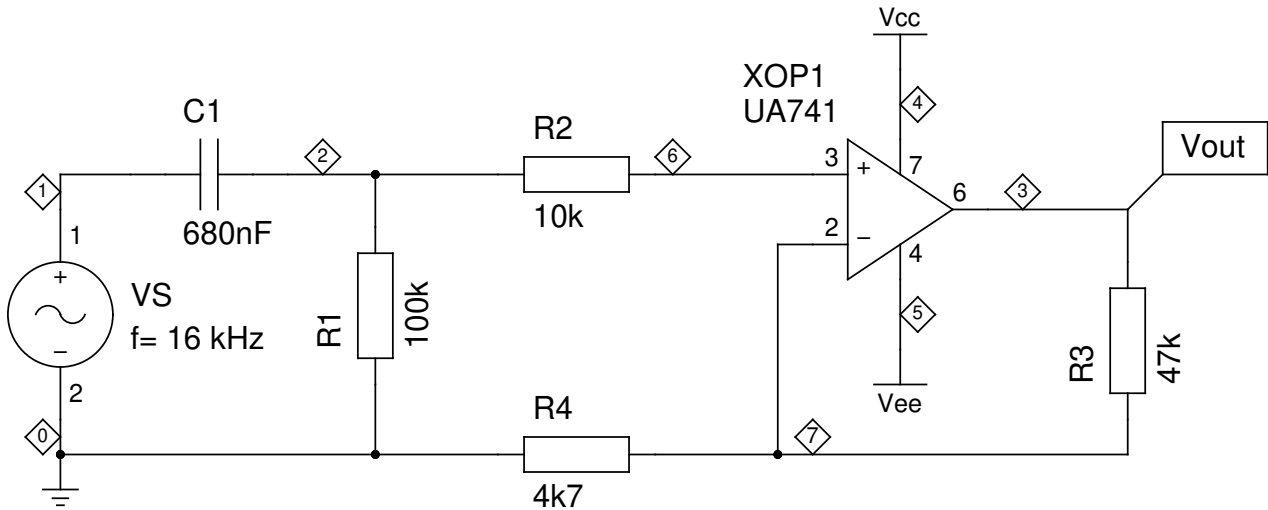

OCTAVE\_FILTER  
Pre-amplifier – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.000.00.01.02.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 001: PRE-AMPLIFIER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 0.141 1k)  
C1 1 2 680n  
R1 0 2 100k  
R2 2 6 10K  
R3 3 7 47k  
R4 7 0 4700  
XOP1 6 7 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.02 0.000001 TRACE ALL

.END

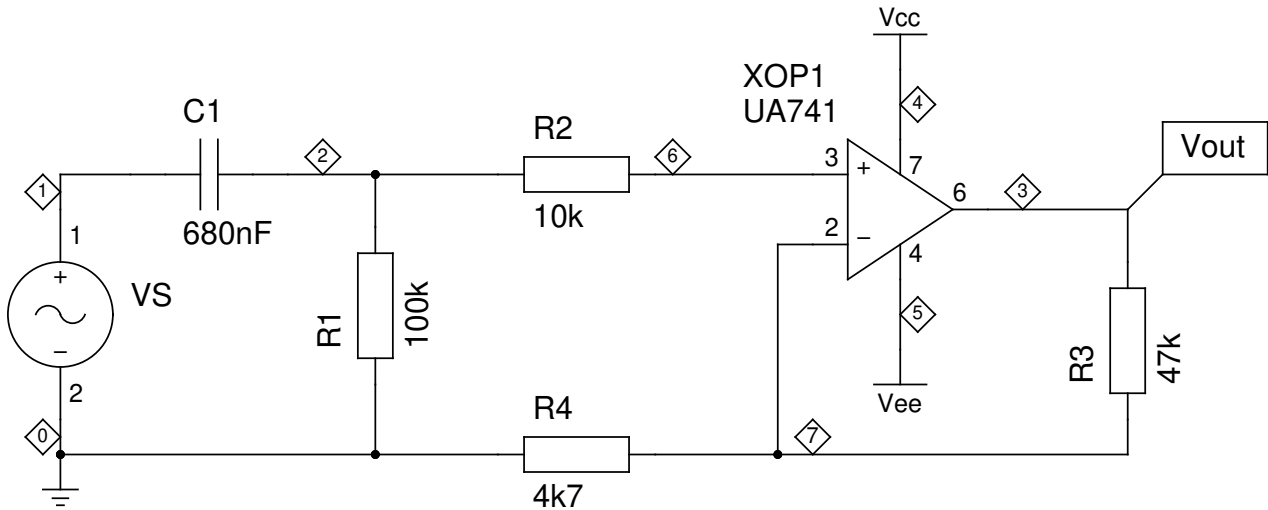

OCTAVE\_FILTER  
Pre-amplifier – Transient response (1 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.001.00.01.03.sch  
PAGE 01 OF 01

REVISION: 20240524  
DRAWN BY: Bert Timmerman





.TITLE OCTAVE FILTER – FUNCTION 002: 31.5 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 14200  
R2 3 6 142K  
R3 0 2 7200  
C1 2 6 220nF  
C2 3 2 220nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.2 0.00001 TRACE ALL

.END

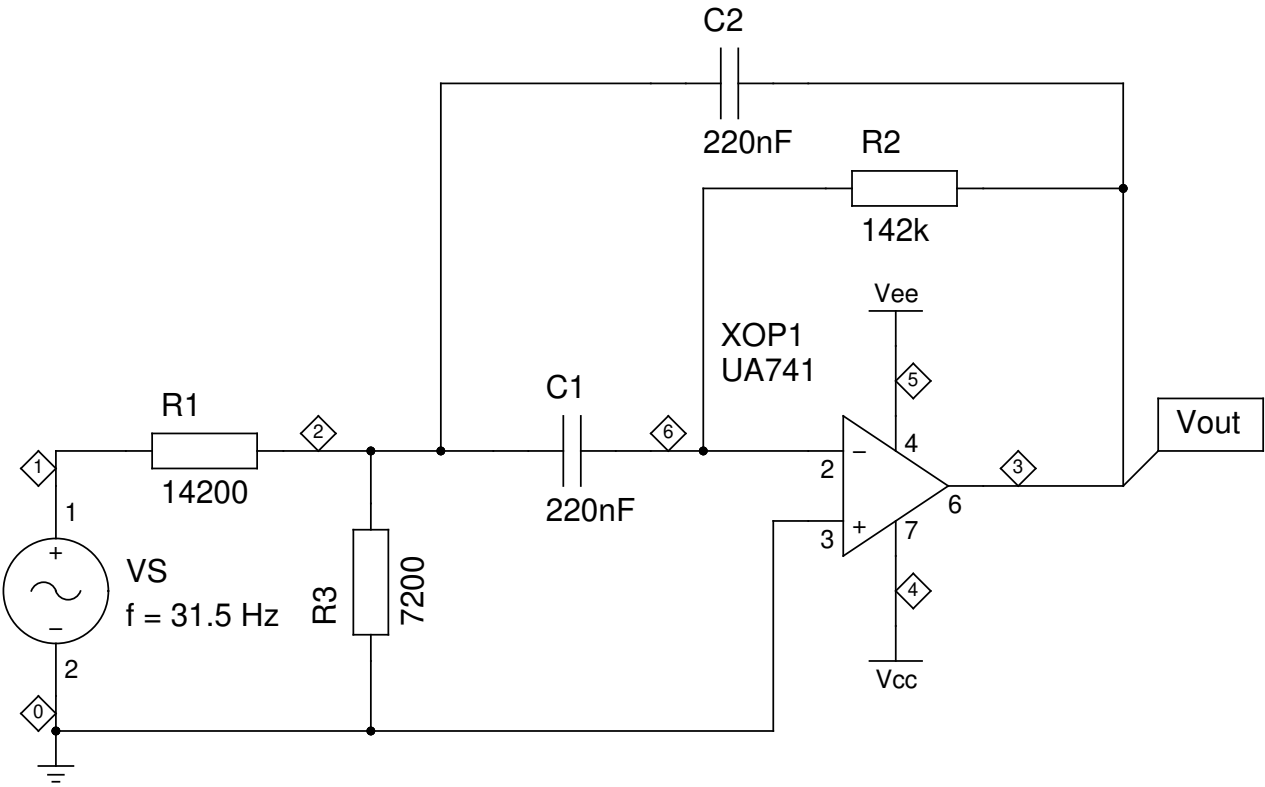

OCTAVE\_FILTER  
31.5 Hz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.002.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240524  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 002: 31.5 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 14200  
R2 3 6 142K  
R3 0 2 7200  
C1 2 6 220nF  
C2 3 2 220nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

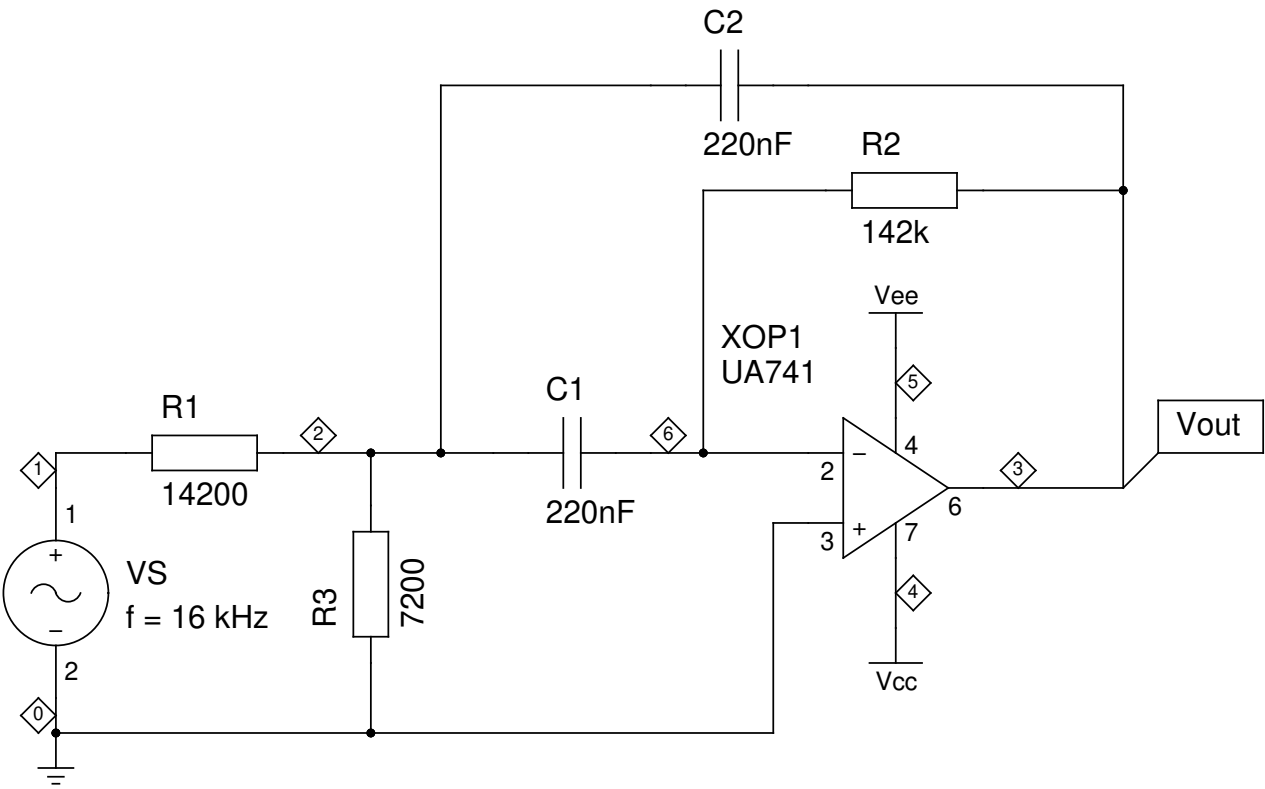

OCTAVE\_FILTER  
31.5 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.002.00.01.02.sch  
PAGE 01 OF 01

REVISION: 20240524  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 002: 31.5 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 14200  
R2 3 6 142K  
R3 0 2 7200  
C1 2 6 220nF  
C2 3 2 220nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

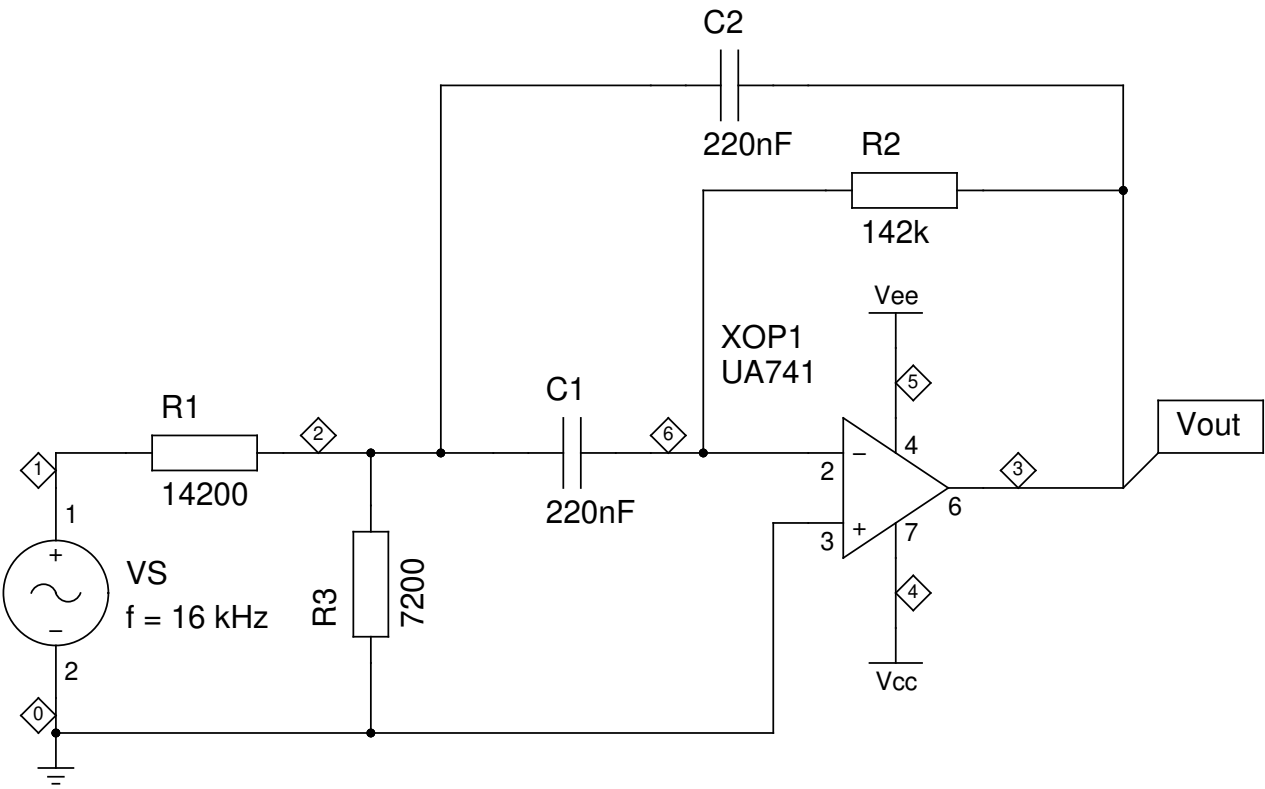

OCTAVE\_FILTER  
31.5 Hz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.002.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240524  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 002: 31.5 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 14200  
R2 3 6 142K  
R3 0 2 7200  
C1 2 6 220nF  
C2 3 2 220nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

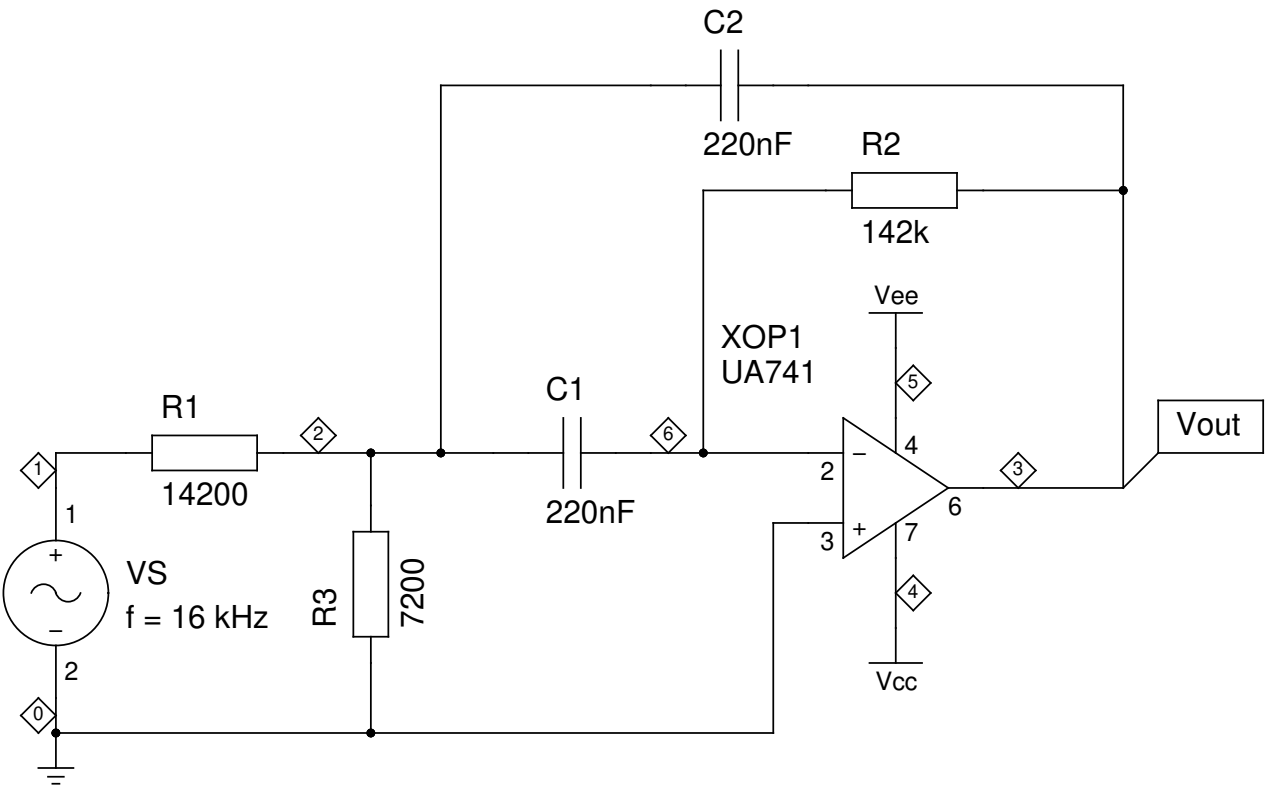

OCTAVE\_FILTER  
31.5 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.002.00.02.02.sch  
PAGE 01 OF 01

REVISION: 20240524  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 002: 31.5 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 14200  
R2 3 6 142K  
R3 0 2 7200  
C1 2 6 220nF  
C2 3 2 220nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.2 0.00001 TRACE ALL

.END

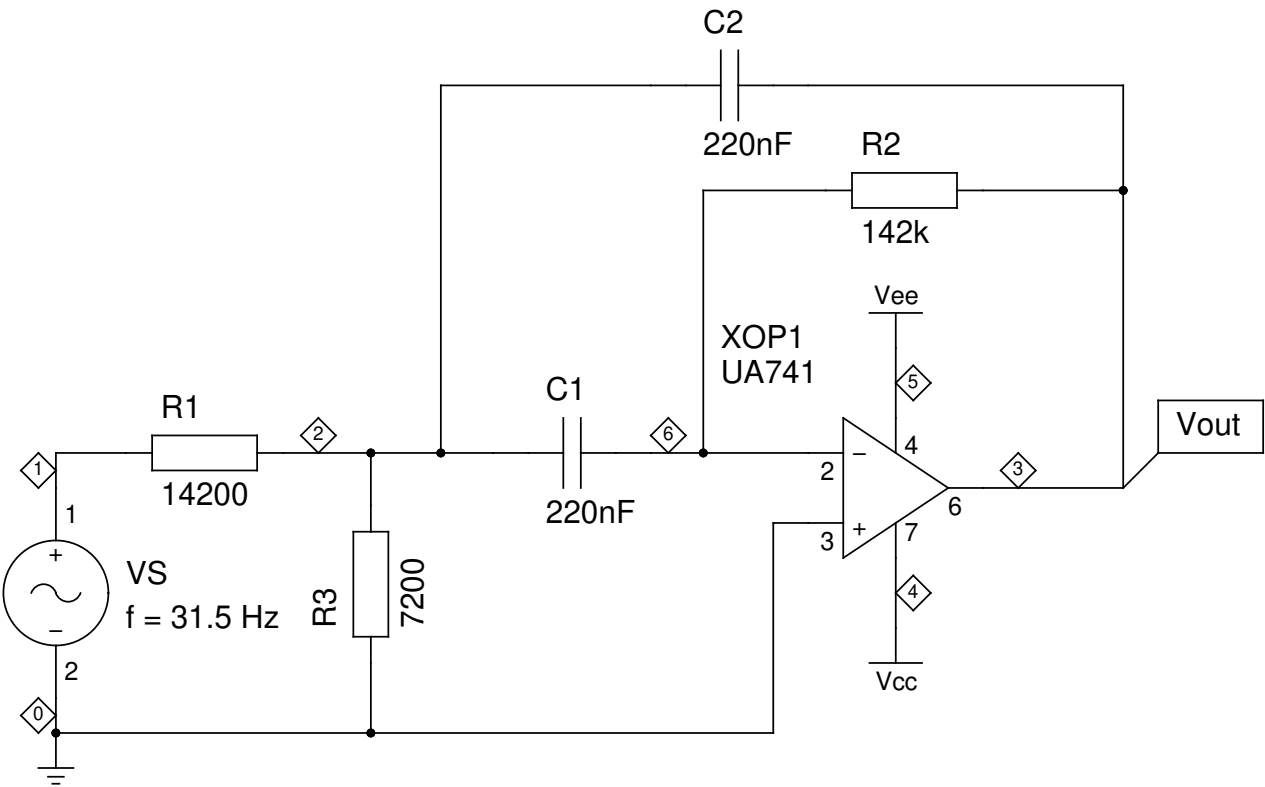

OCTAVE\_FILTER  
31.5 Hz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.002.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 002: 31.5 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 14200  
R2 3 6 142K  
R3 0 2 7200  
C1 2 6 220nF  
C2 3 2 220nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END


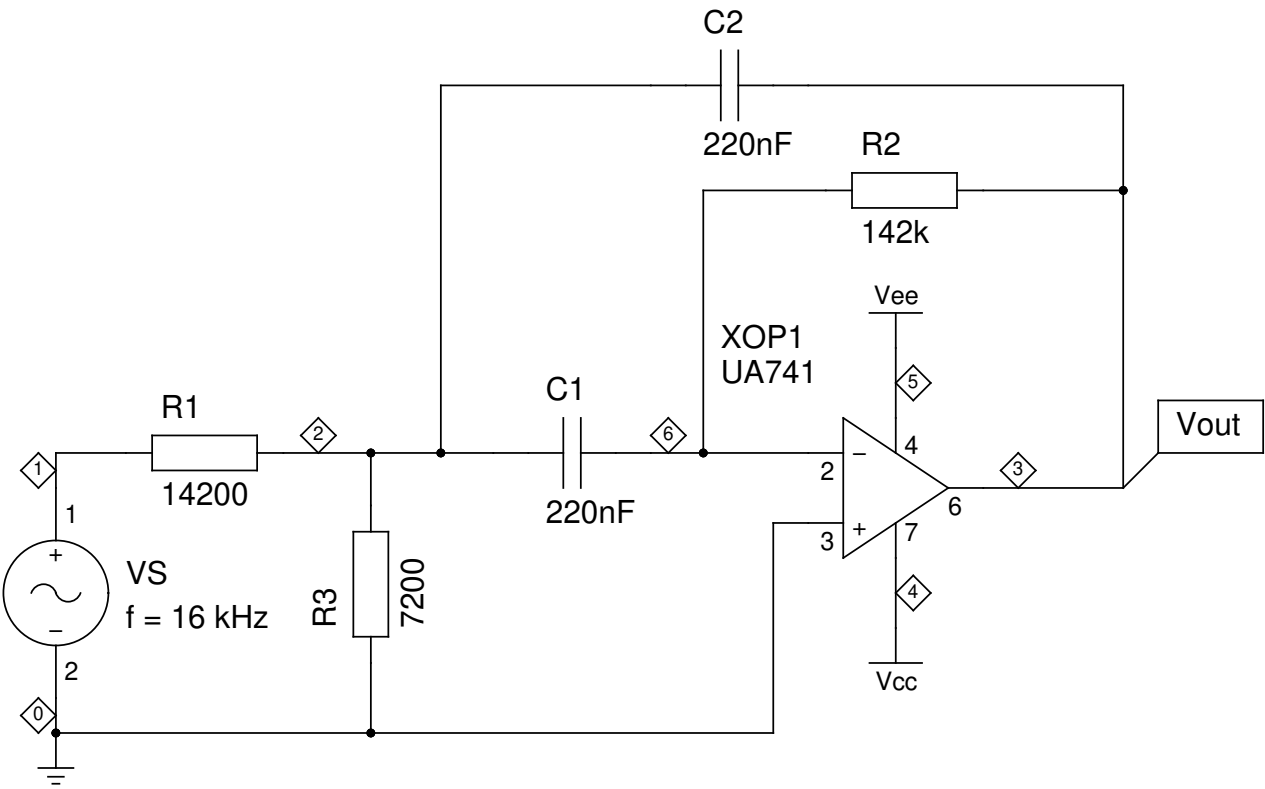


OCTAVE\_FILTER  
31.5 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.002.00.03.02.sch  
PAGE 01 OF 01



REVISION: 20240525  
DRAWN BY: Bert Timmerman

.END

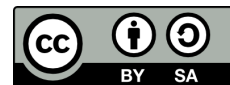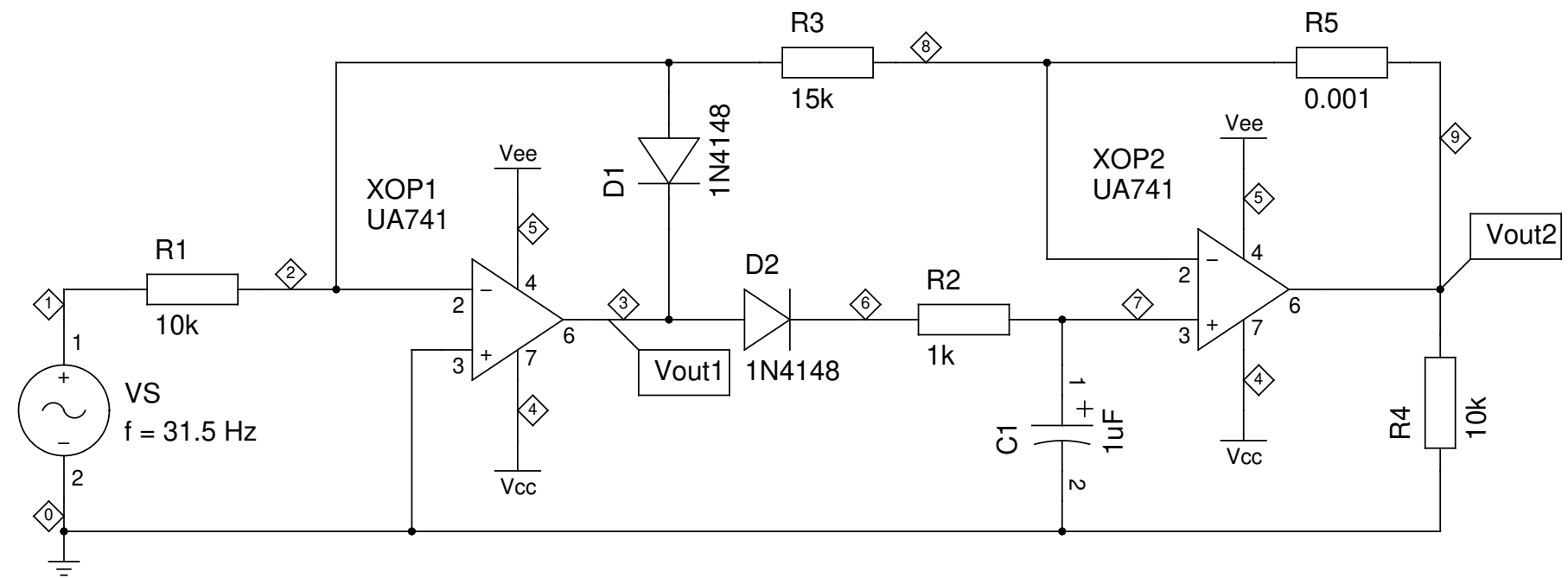

A3

.END

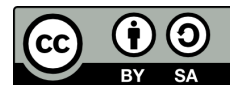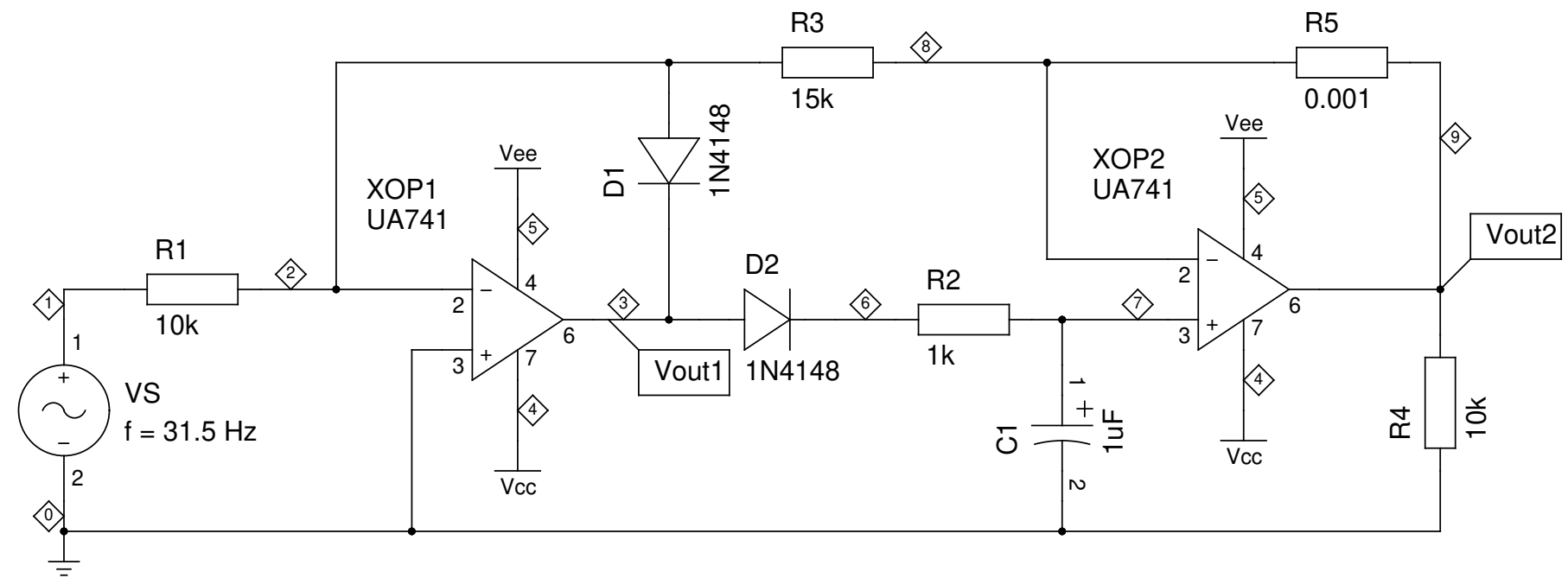

A3



.TITLE OCTAVE FILTER – FUNCTION 003: 31.5 HZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14


VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)

VS 1 0 AC 1 SIN(0 1.41 31.5)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3) I(R4) I(R5) I(D1) I(D2)

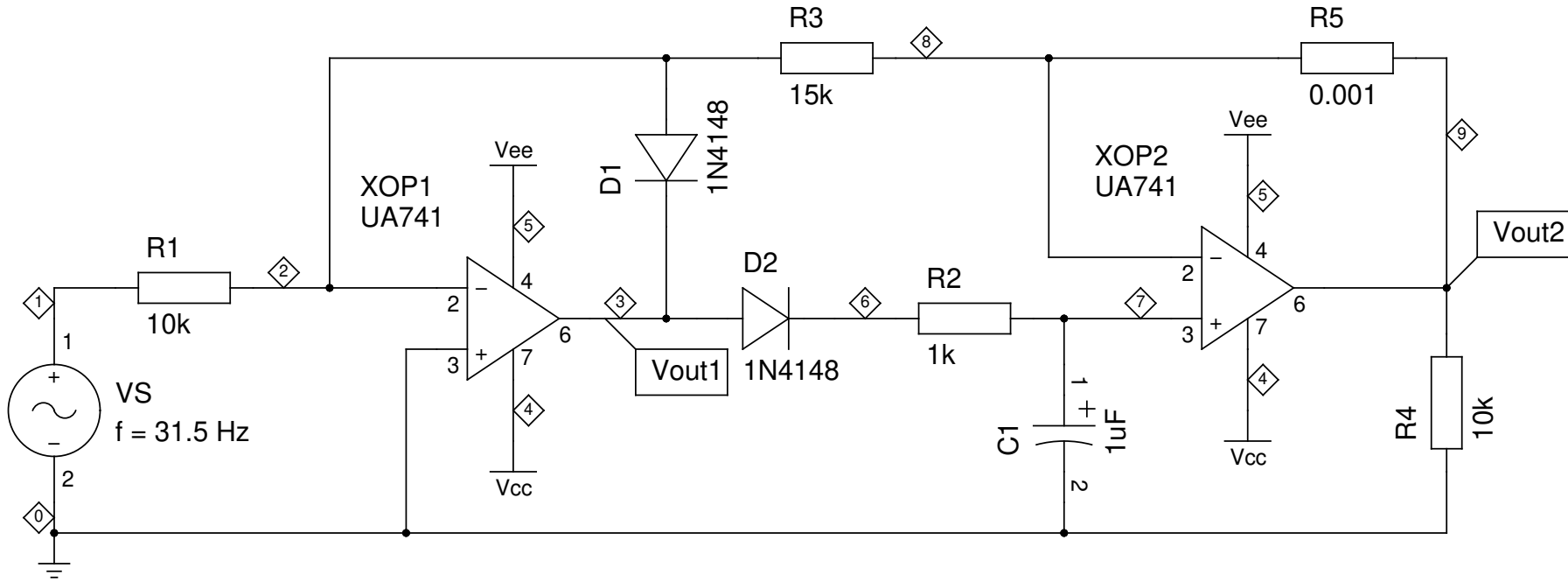\* FROM TO STEP  
.TRAN 0 0.4 0.00001 TRACE ALL  
.END



OCTAVE\_FILTER  
31.5 Hz Detector – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.003.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 003: 31.5 HZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)



VS 1 0 AC 1 SIN(0 1.41 31.5)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3) P(R4) P(R5) P(D1) P(D2)

\* FROM TO STEP  
.TRAN 0 0.4 0.00001 TRACE ALL

.END

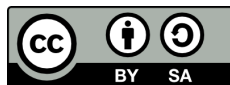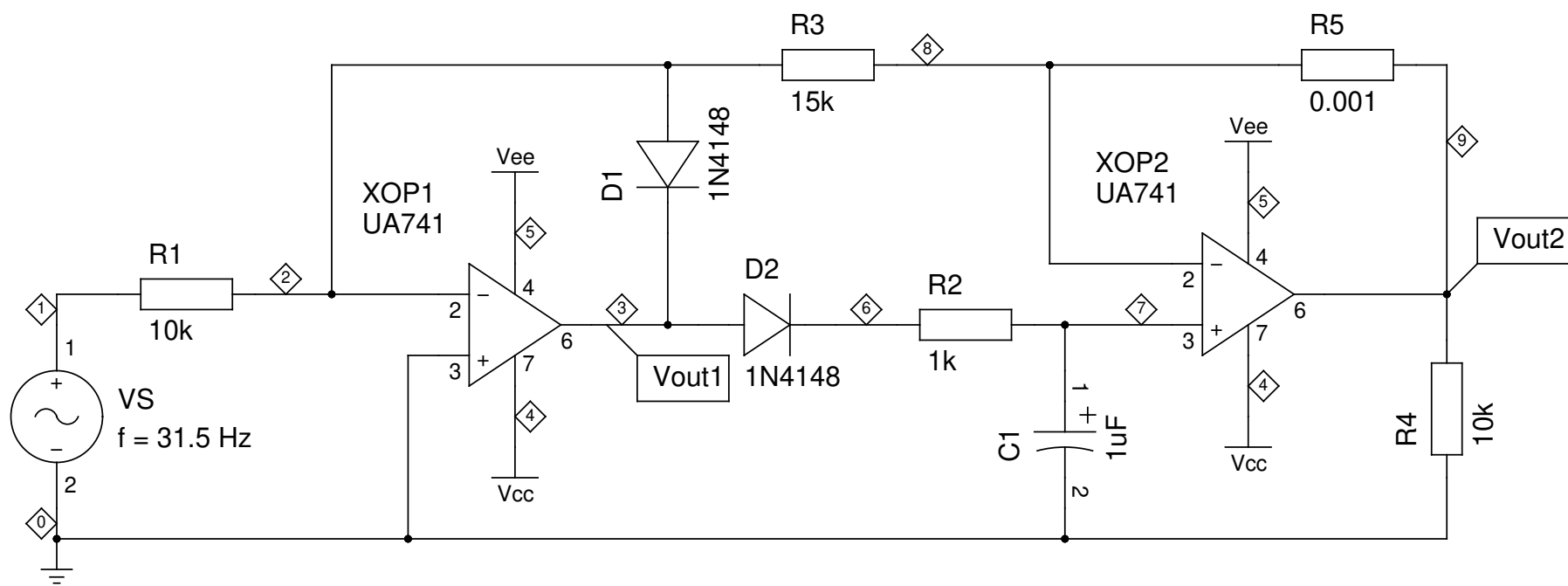

OCTAVE\_FILTER  
31.5 Hz Detector – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.003.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 004: 63 HZ BAND–PASS FILTER – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 0.1 100)  
R1 1 2 15900  
R2 3 6 159K  
R3 0 2 7200  
C1 2 6 100nF  
C2 3 2 100nF  
XOP1 0 6 0 4 5 3 UA741


.PRINT OP Iter(0) V(3)

.PRINT AC VDB(3)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

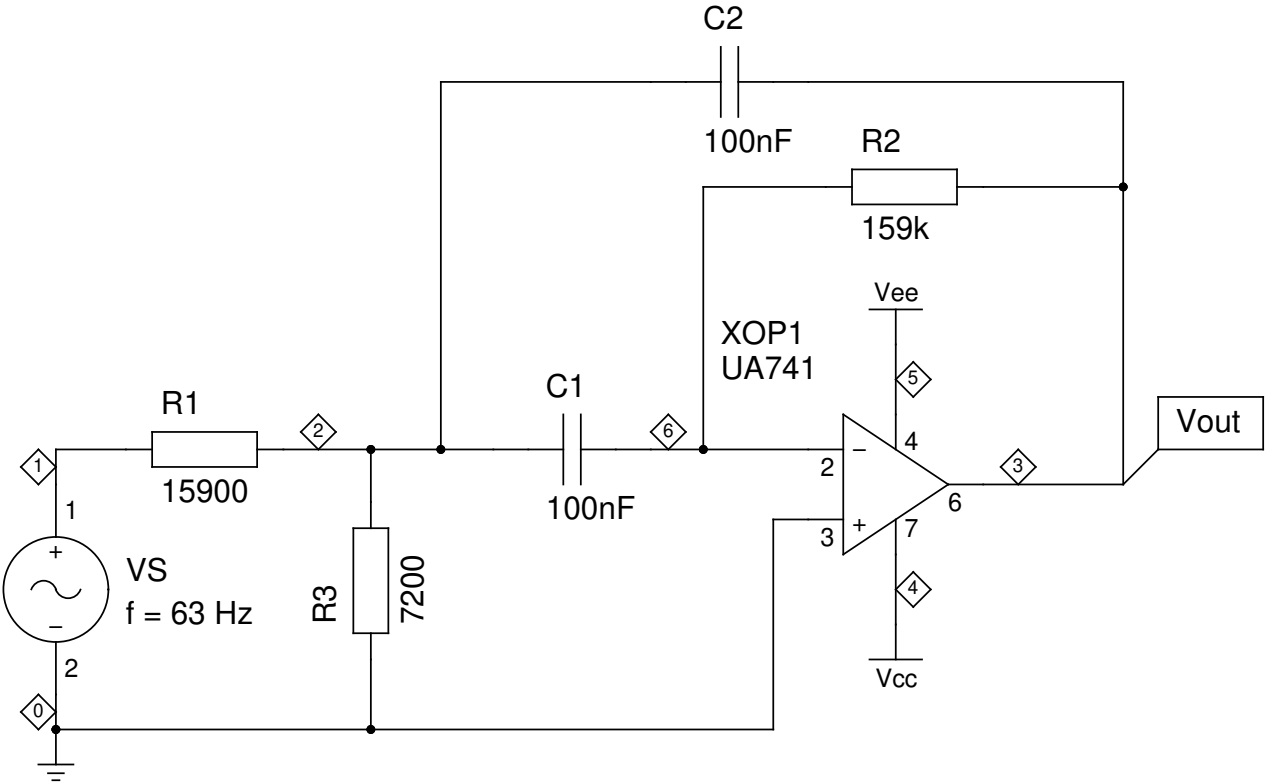

OCTAVE\_FILTER  
63 Hz Band-pass Filter – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.004.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 004: 63 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 63)  
R1 1 2 15900  
R2 3 6 159K  
R3 0 2 7200  
C1 2 6 100nF  
C2 3 2 100nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.2 0.0001 TRACE ALL

.END

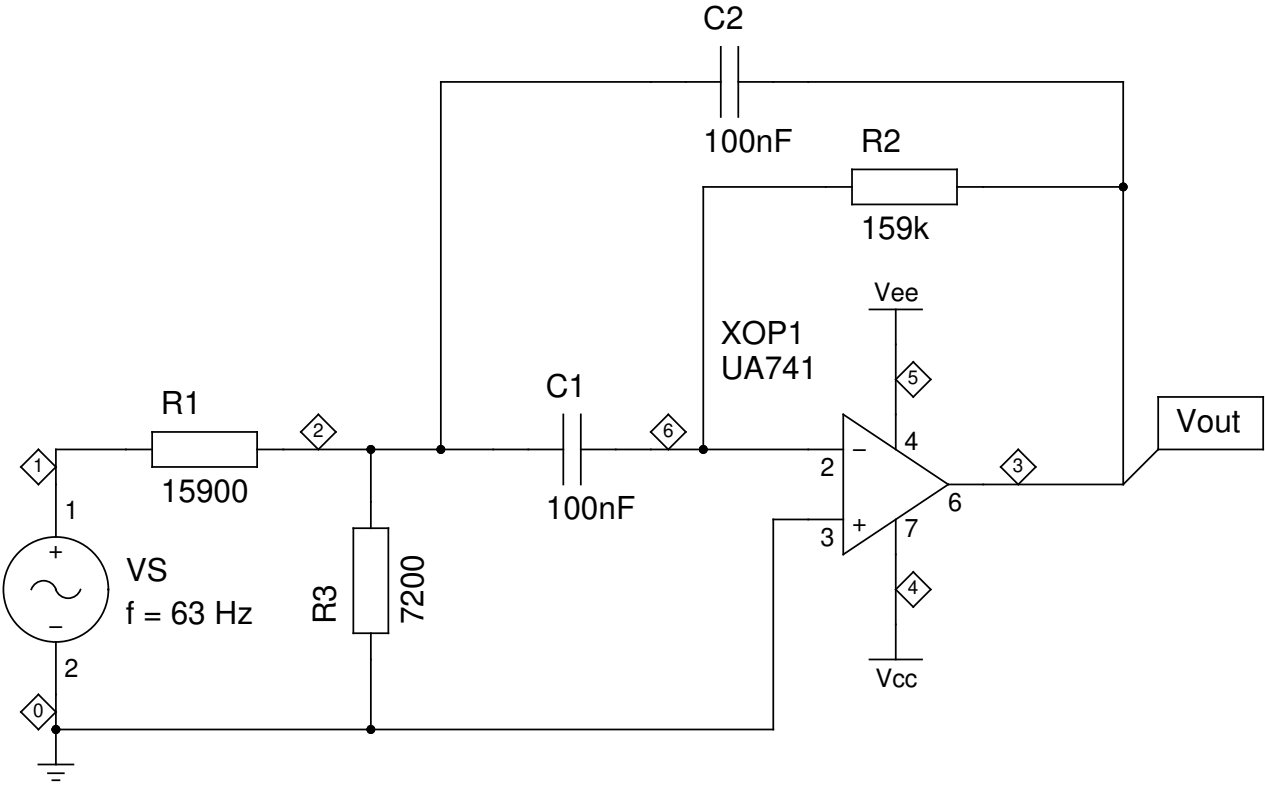

OCTAVE\_FILTER  
63 Hz Band-pass Filter – Transient response (63 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.004.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 004: 63 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 15900  
R2 3 6 159K  
R3 0 2 7200  
C1 2 6 100nF  
C2 3 2 100nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

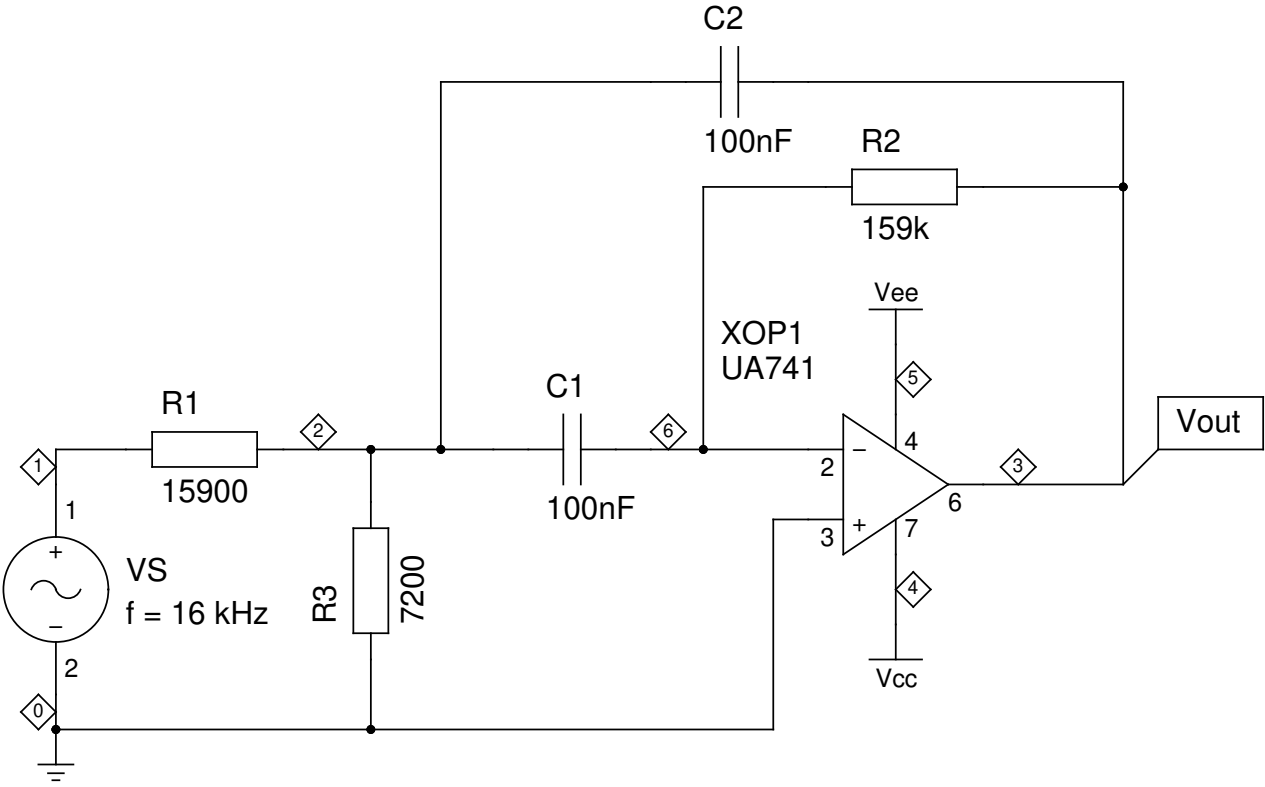

OCTAVE\_FILTER  
63 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.004.00.01.02.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 004: 63 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 63)  
R1 1 2 15900  
R2 3 6 159K  
R3 0 2 7200  
C1 2 6 100nF  
C2 3 2 100nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.2 0.0001 TRACE ALL

.END

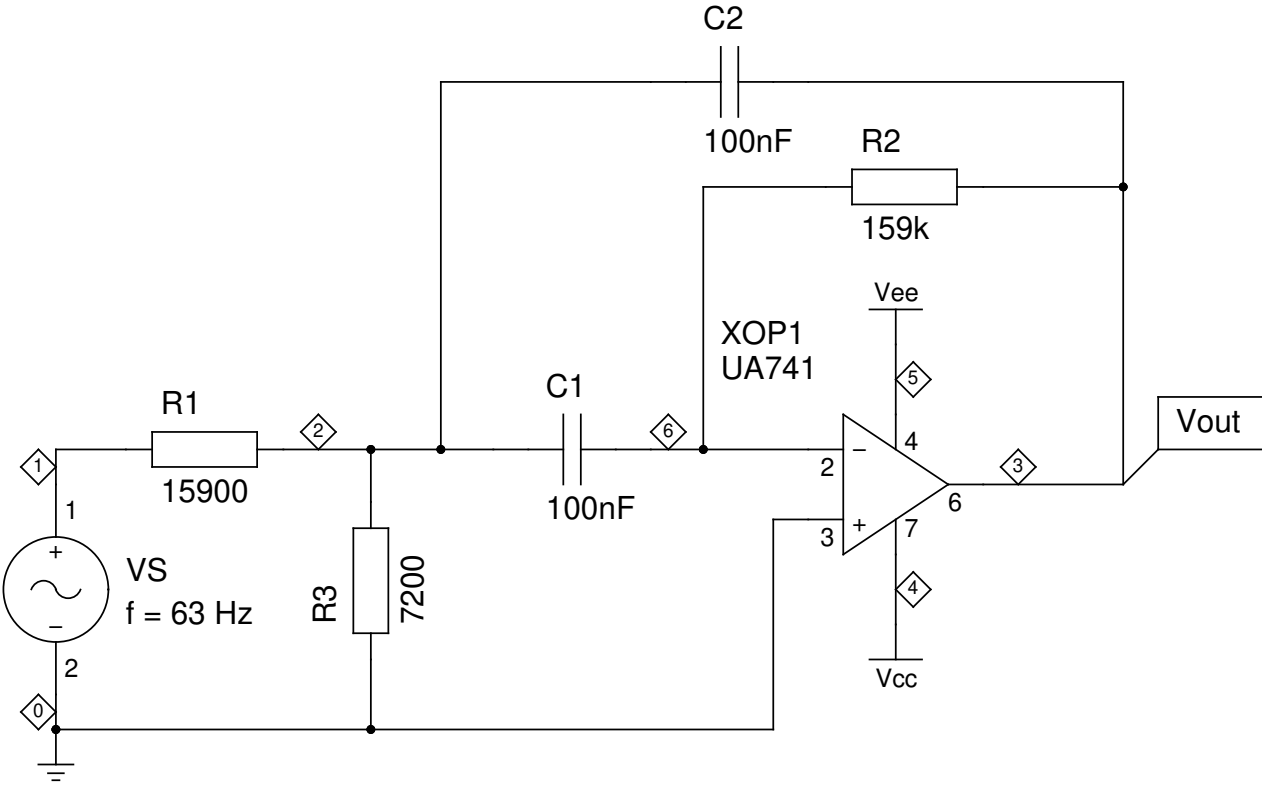

OCTAVE\_FILTER  
63 Hz Band-pass Filter – Transient response (63 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.004.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 004: 63 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 15900  
R2 3 6 159K  
R3 0 2 7200  
C1 2 6 100nF  
C2 3 2 100nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

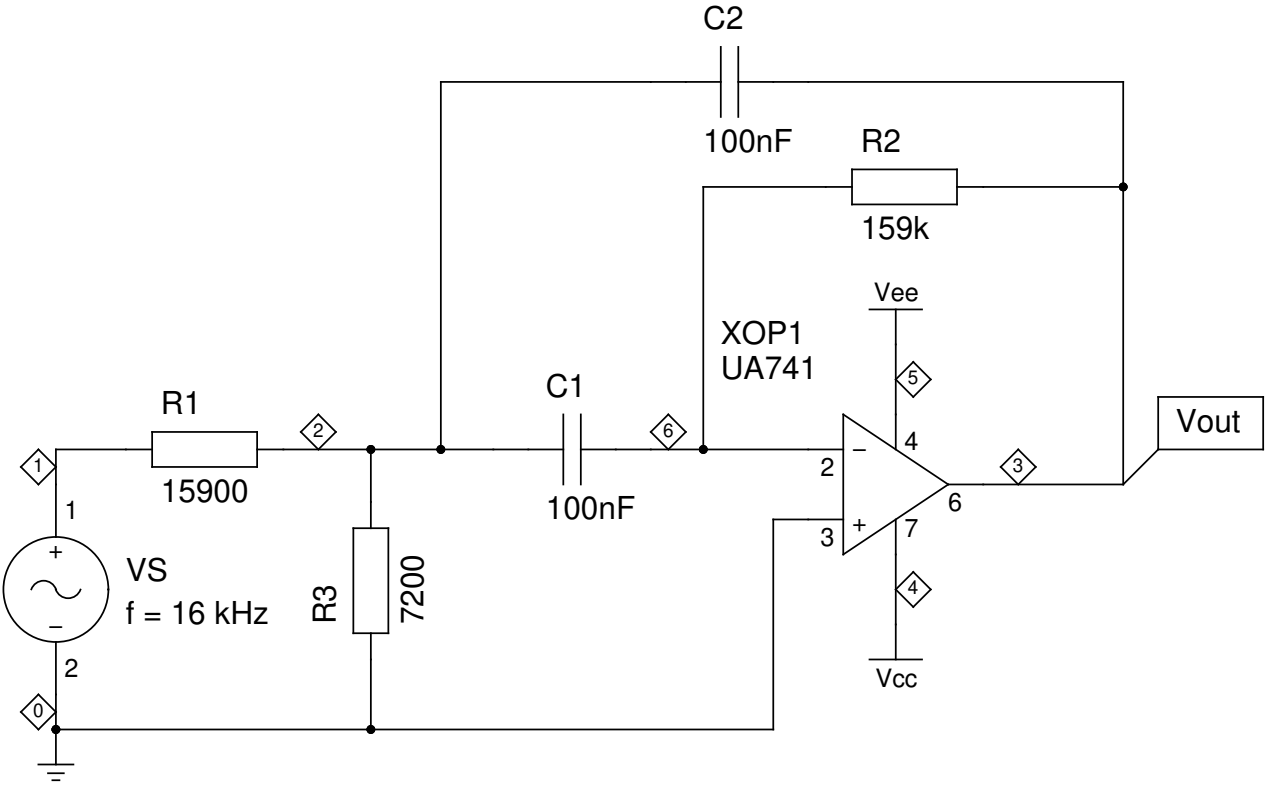

OCTAVE\_FILTER  
63 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.004.00.02.02.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 004: 63 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 63)  
R1 1 2 15900  
R2 3 6 159K  
R3 0 2 7200  
C1 2 6 100nF  
C2 3 2 100nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.2 0.0001 TRACE ALL

.END

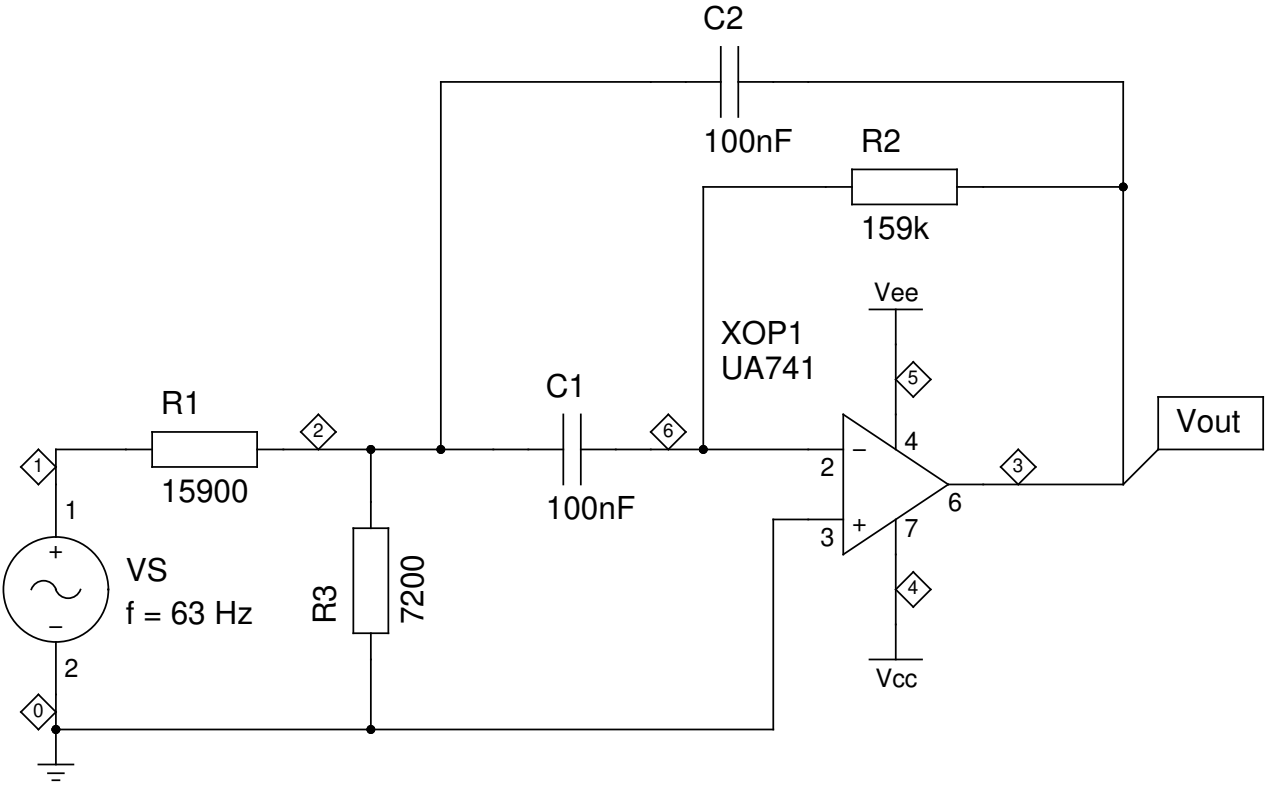

OCTAVE\_FILTER  
63 Hz Band-pass Filter – Transient response (63 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.004.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman



.TITLE OCTAVE FILTER – FUNCTION 004: 63 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 0.141 16k)  
R1 1 2 15900  
R2 3 6 159K  
R3 0 2 7200  
C1 2 6 100nF  
C2 3 2 100nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

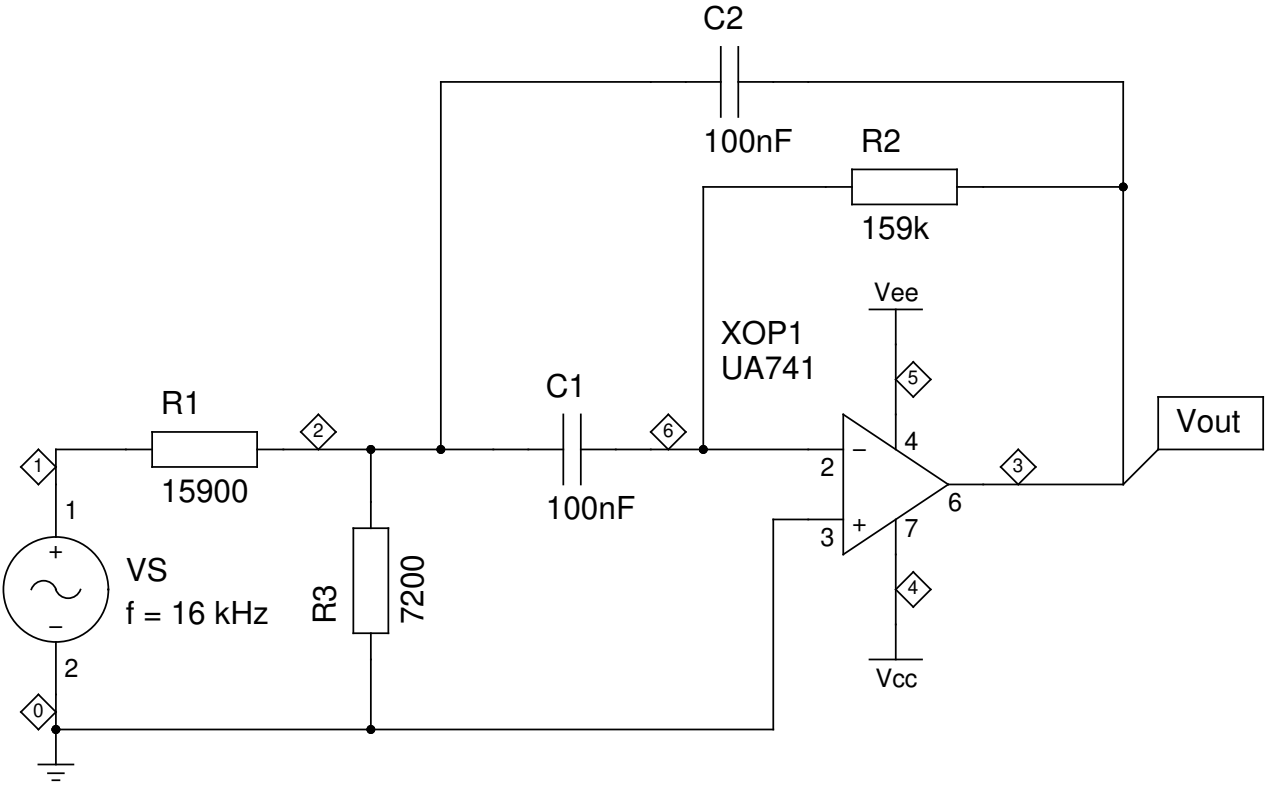

OCTAVE\_FILTER  
63 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.004.00.03.02.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 005: 63 HZ DETECTOR – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 0.1 63)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741


.PRINT OP Iter(0) V(3)

.PRINT AC VDB(3) VDB(9)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

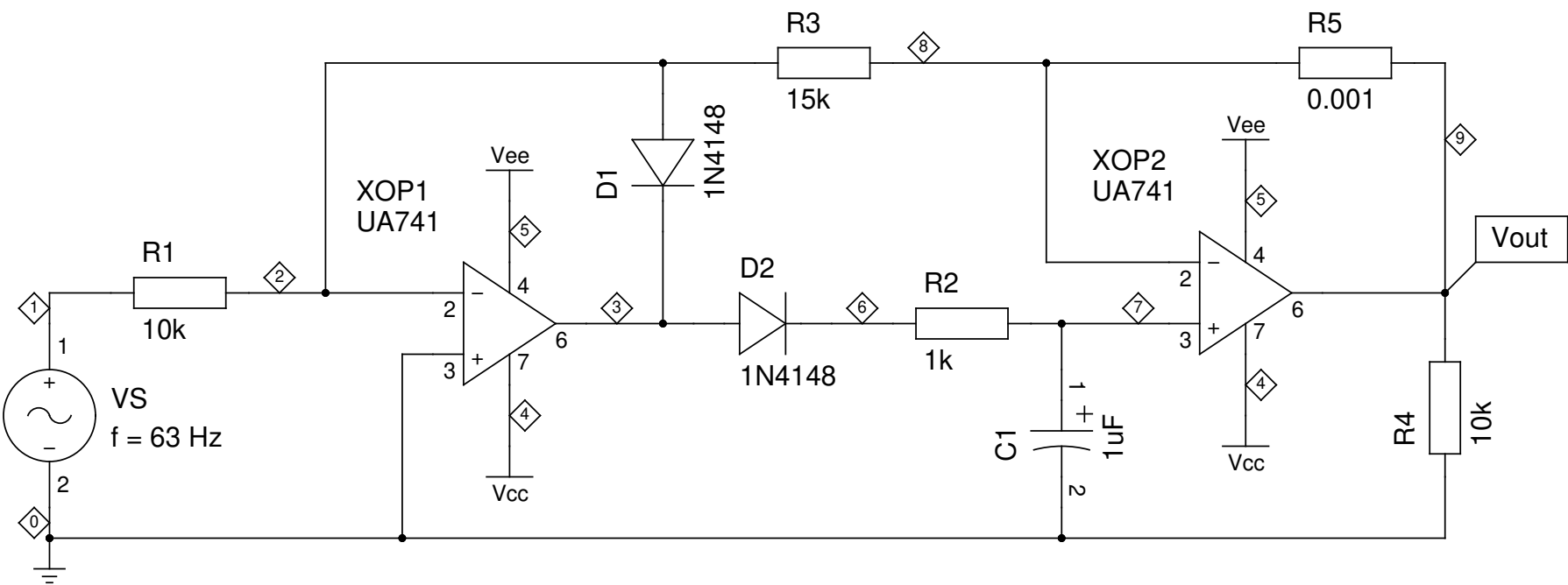

OCTAVE\_FILTER  
63 Hz Detector – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.005.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 005: 63 HZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)



VS 1 0 AC 1 SIN(0 1.41 63)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(9) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.4 0.00001

.END

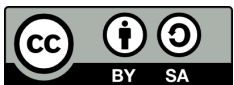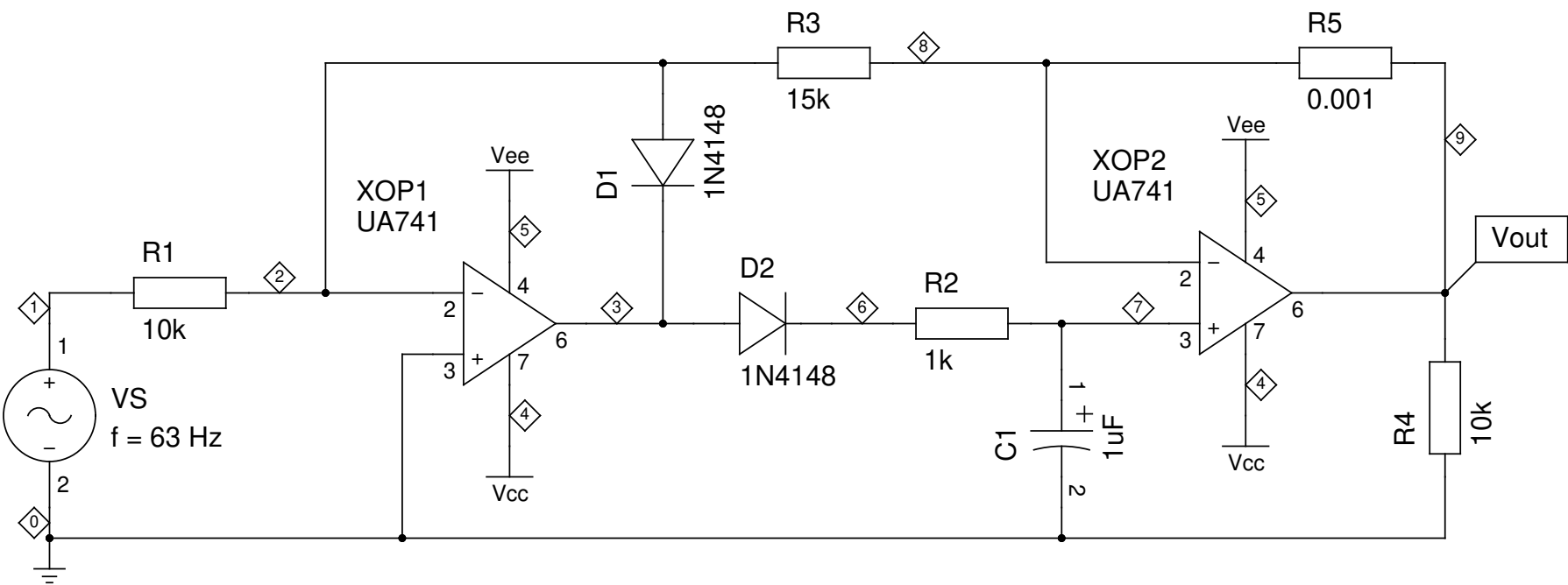

OCTAVE\_FILTER  
63 Hz Detector – Transient response (63 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.005.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 005: 63 HZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 63)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iiter(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3) I(R4) I(R5) I(D1) I(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

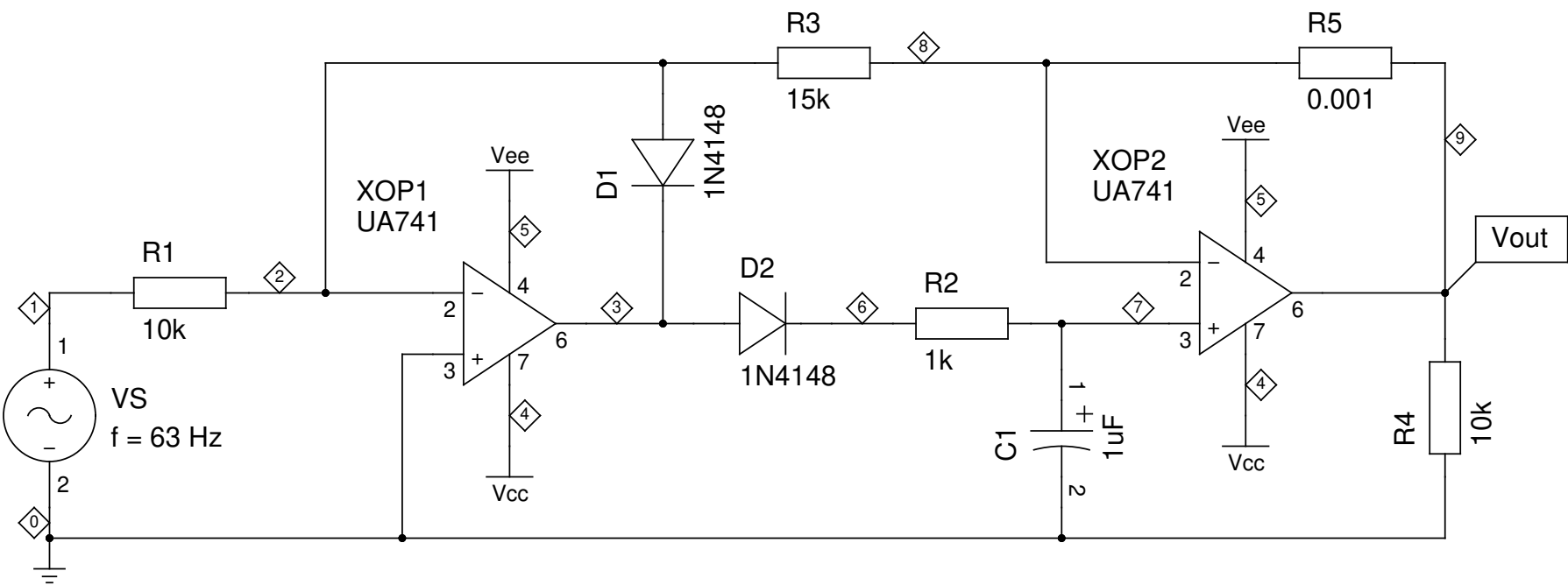

OCTAVE\_FILTER  
63 Hz Detector – Transient response (63 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.005.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 005: 63 DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 63)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iiter(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3) P(R4) P(R5) P(D1) P(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

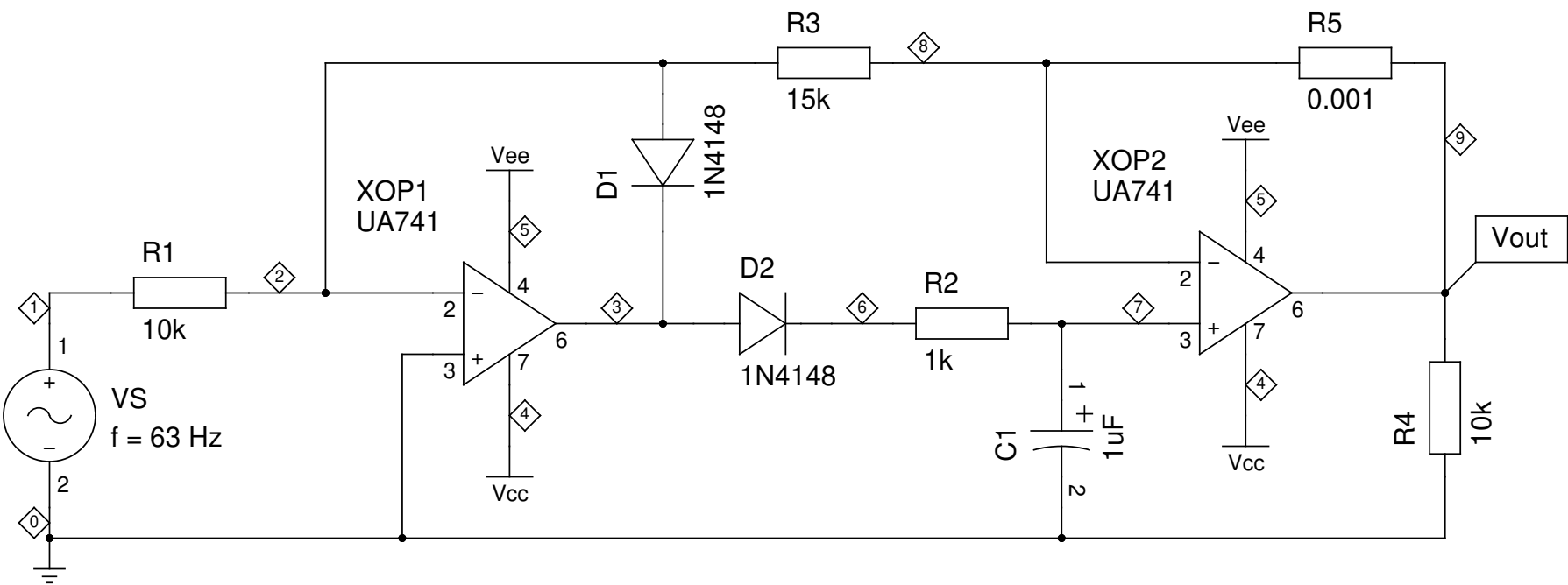

OCTAVE\_FILTER  
63 Hz Detector – Transient response (63 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.005.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 006: 125 HZ BAND–PASS FILTER – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 0.1 100)  
R1 1 2 16800  
R2 3 6 168K  
R3 0 2 7200  
C1 2 6 47nF  
C2 3 2 47nF  
XOP1 0 6 0 4 5 3 UA741


.PRINT OP Iter(0) V(3)

.PRINT AC VDB(3)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

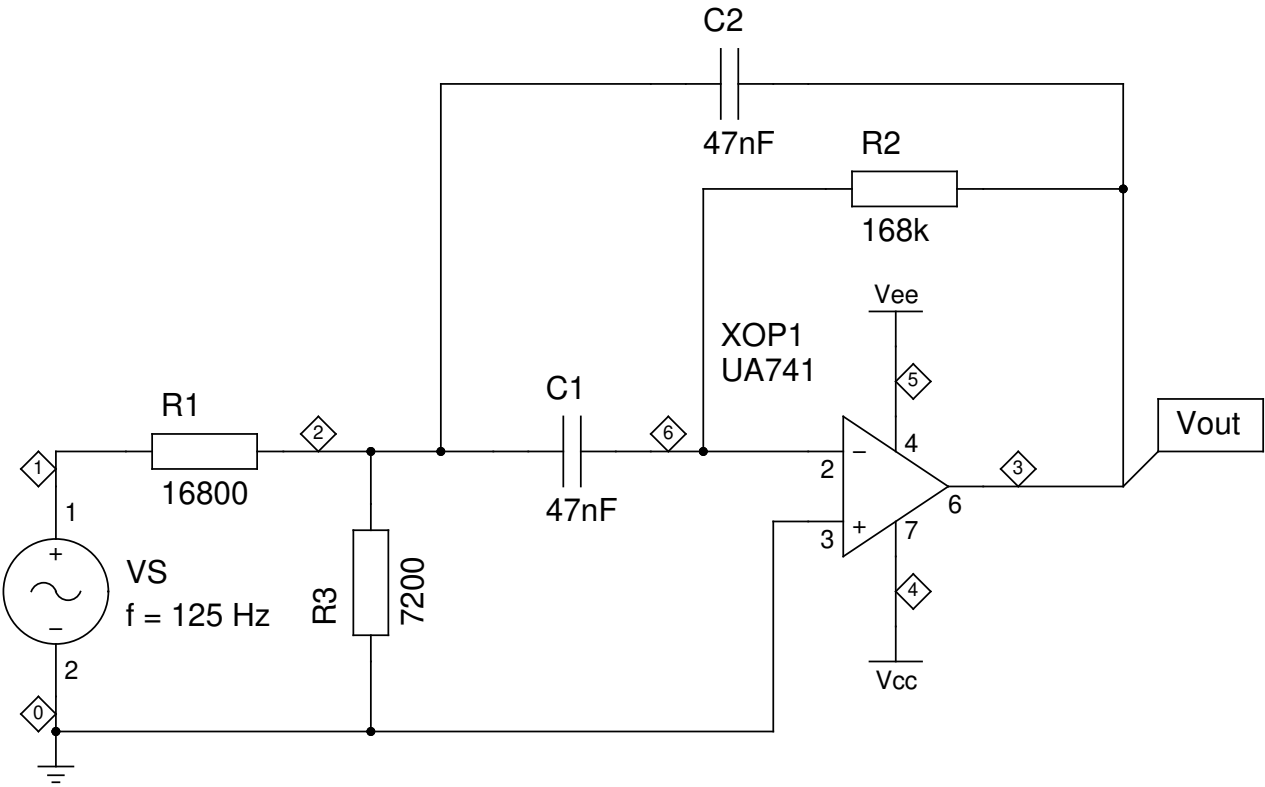

OCTAVE\_FILTER  
125 Hz Band-pass Filter – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.006.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 006: 125 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 125)  
R1 1 2 16800  
R2 3 6 168K  
R3 0 2 7200  
C1 2 6 47nF  
C2 3 2 47nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

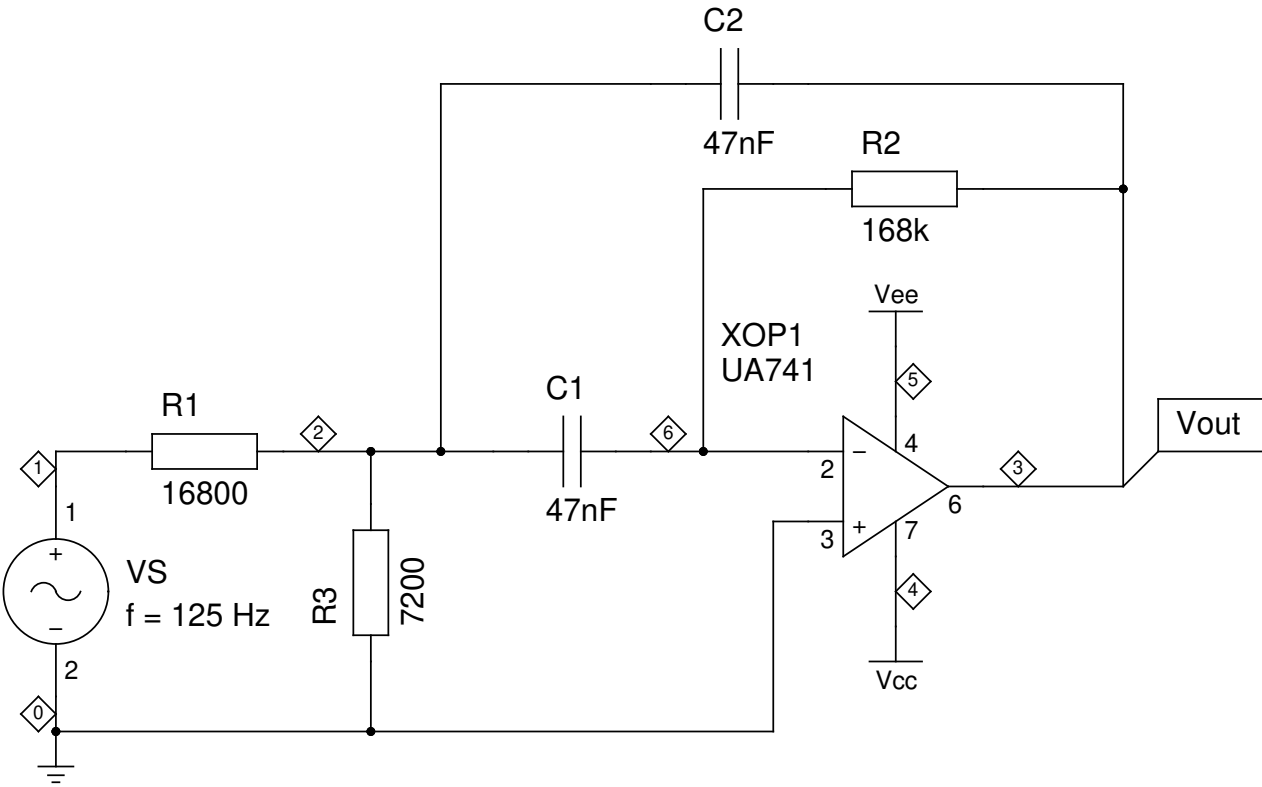

OCTAVE\_FILTER  
125 Hz Band-pass Filter – Transient response (125 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.006.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 006: 125 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 16800  
R2 3 6 168K  
R3 0 2 7200  
C1 2 6 47nF  
C2 3 2 47nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

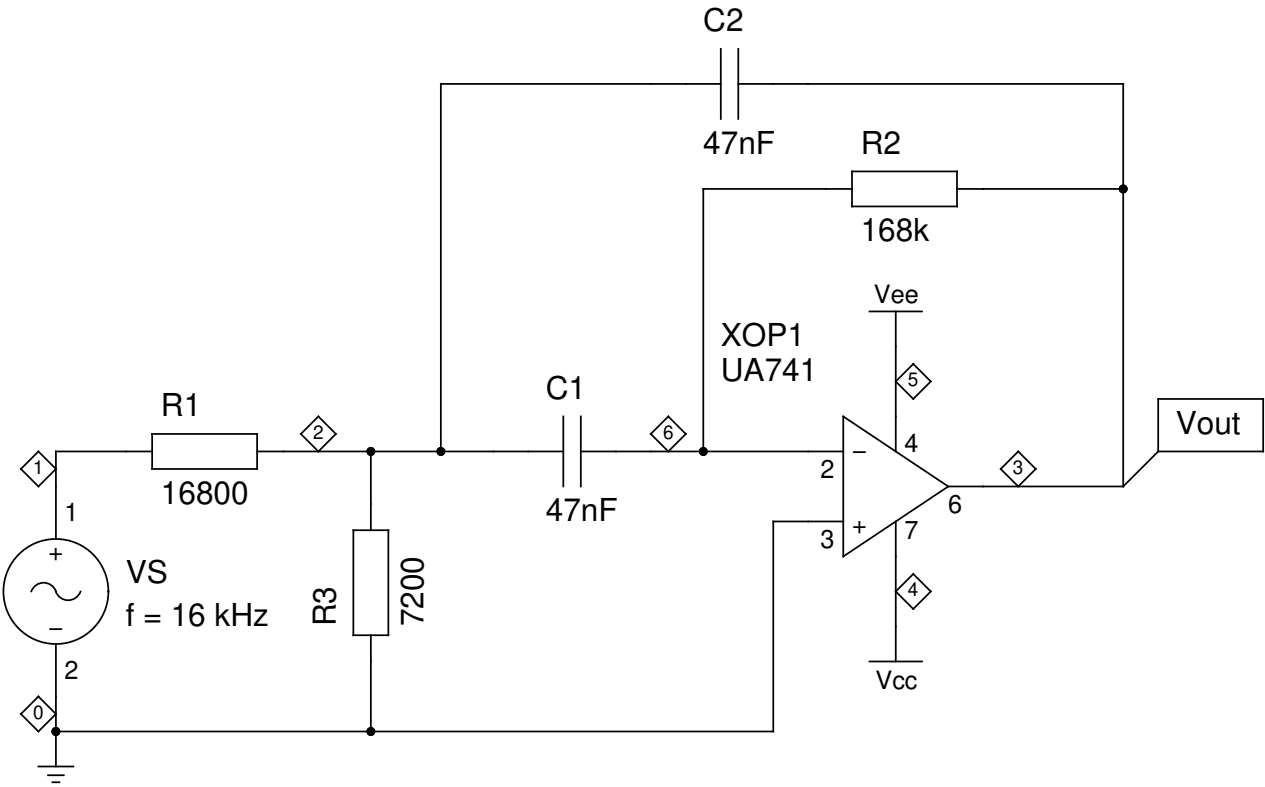

OCTAVE\_FILTER  
125 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.006.00.01.02.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman



.TITLE OCTAVE FILTER – FUNCTION 006: 125 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 125)  
R1 1 2 16800  
R2 3 6 168K  
R3 0 2 7200  
C1 2 6 47nF  
C2 3 2 47nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

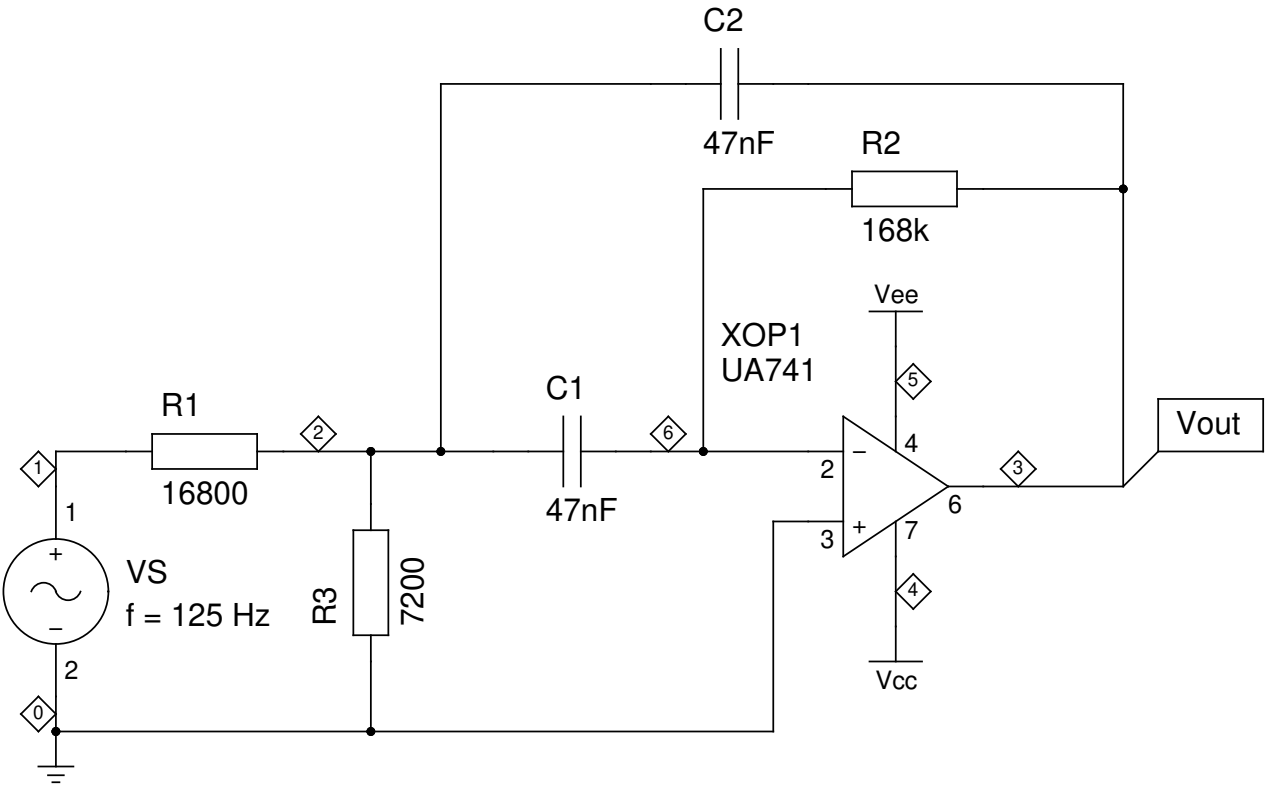

OCTAVE\_FILTER  
125 Hz Band-pass Filter – Transient response (125 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.006.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 006: 125 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 16800  
R2 3 6 168K  
R3 0 2 7200  
C1 2 6 47nF  
C2 3 2 47nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

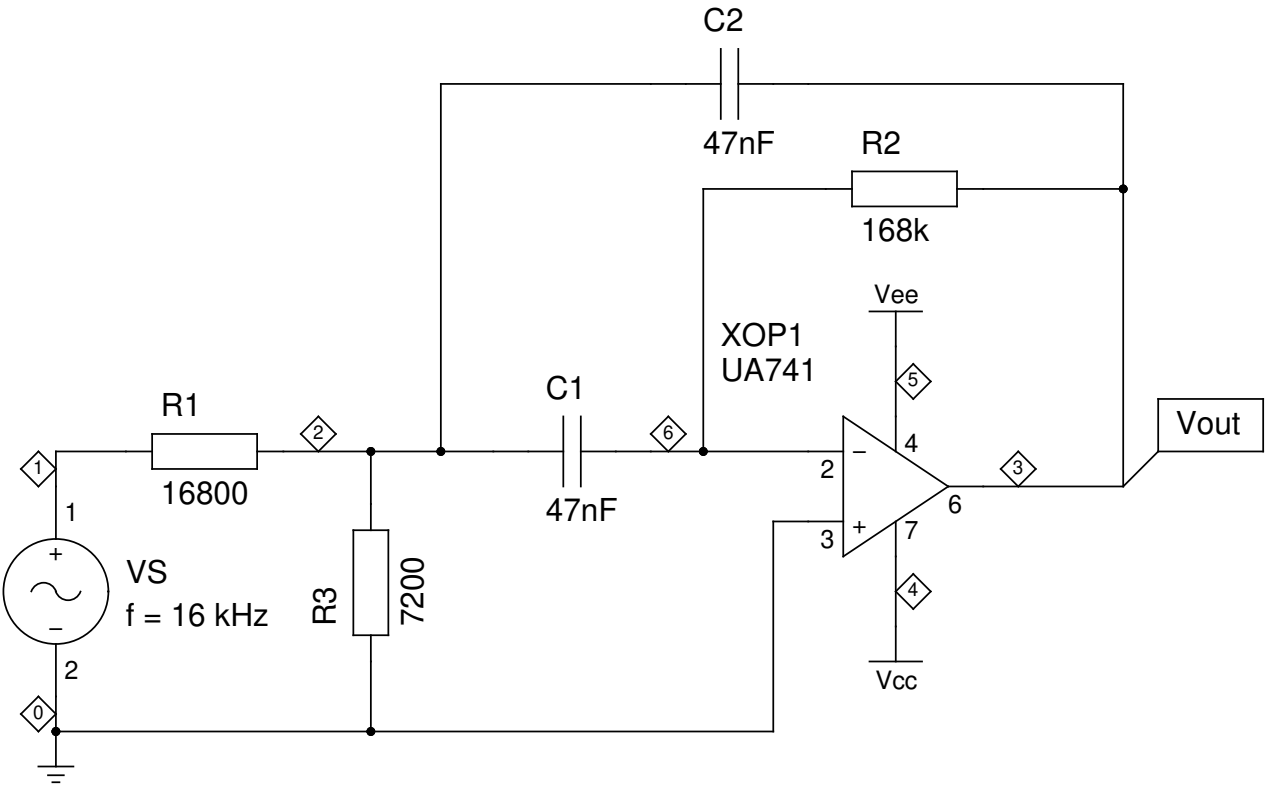

OCTAVE\_FILTER  
125 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.006.00.02.02.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 006: 125 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 125)  
R1 1 2 16800  
R2 3 6 168K  
R3 0 2 7200  
C1 2 6 47nF  
C2 3 2 47nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

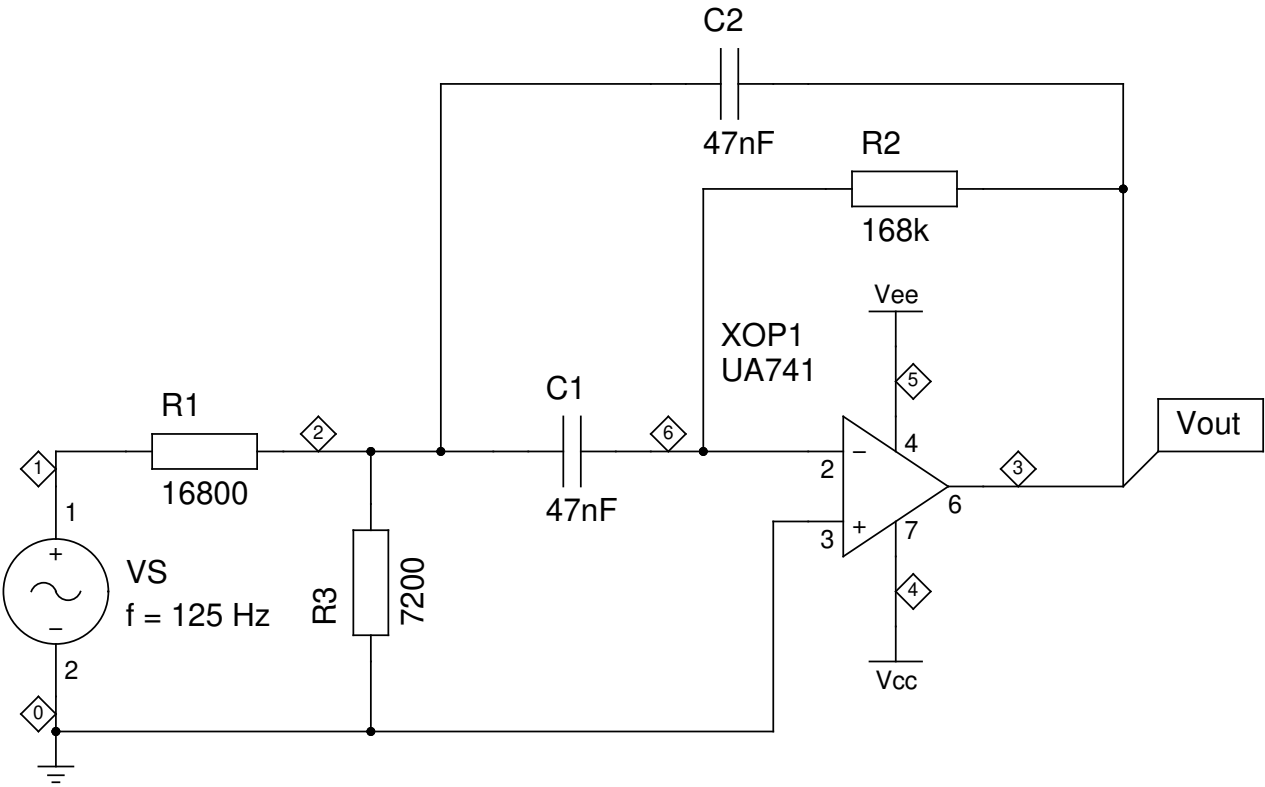

OCTAVE\_FILTER  
125 Hz Band-pass Filter – Transient response (125 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.006.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 007: 125 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 16800  
R2 3 6 168K  
R3 0 2 7200  
C1 2 6 47nF  
C2 3 2 47nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

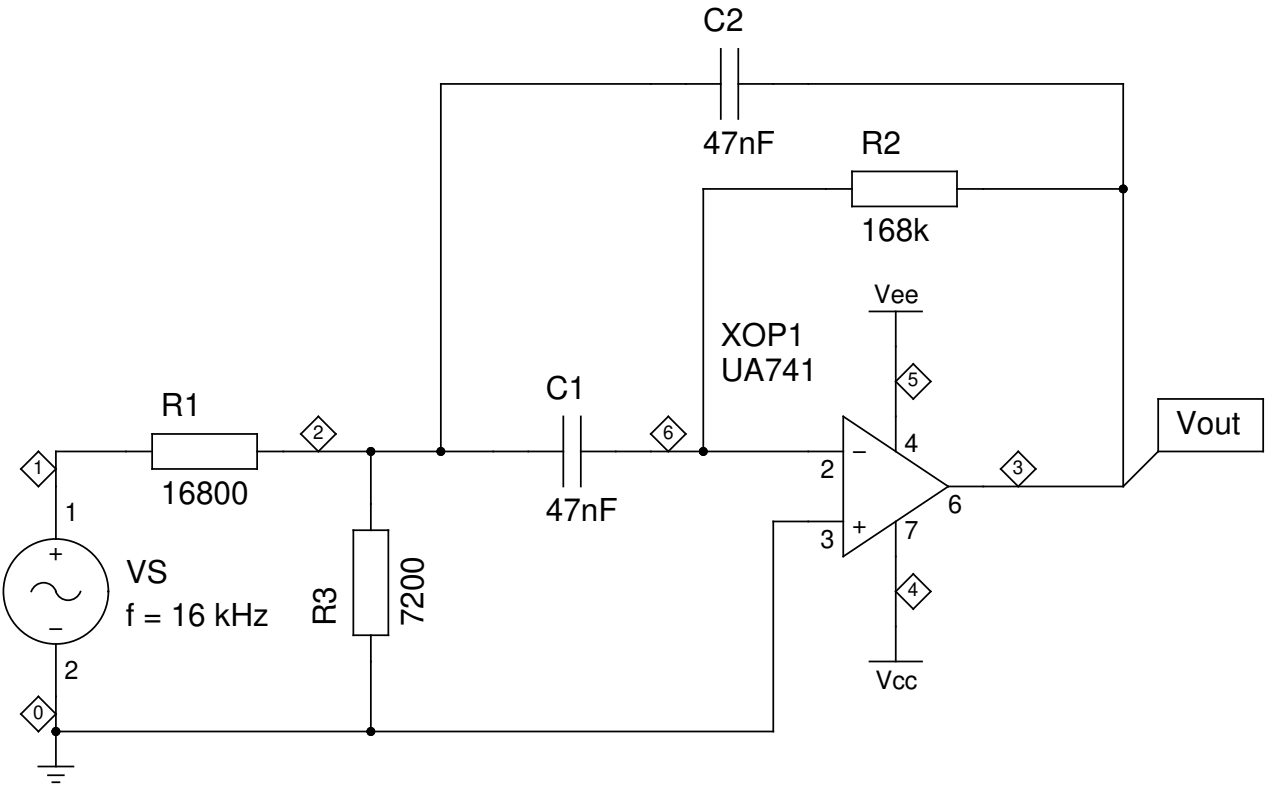

OCTAVE\_FILTER  
125 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.006.00.03.02.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 007: 125 HZ DETECTOR – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 1 125)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741


.PRINT OP Iter(0) V(3)

.PRINT AC VDB(3) VDB(9)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

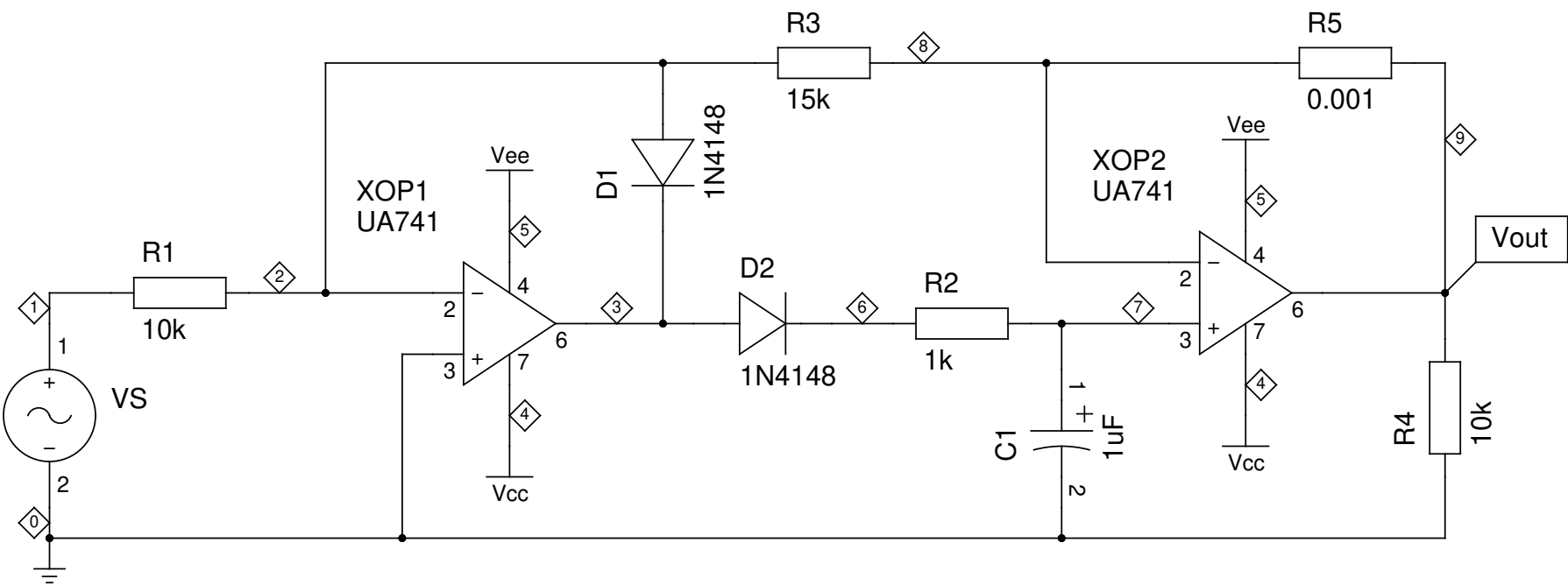

OCTAVE\_FILTER  
125 Hz Detector – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.007.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 007: 125 HZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1 125)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(9) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.4 0.00001

.END

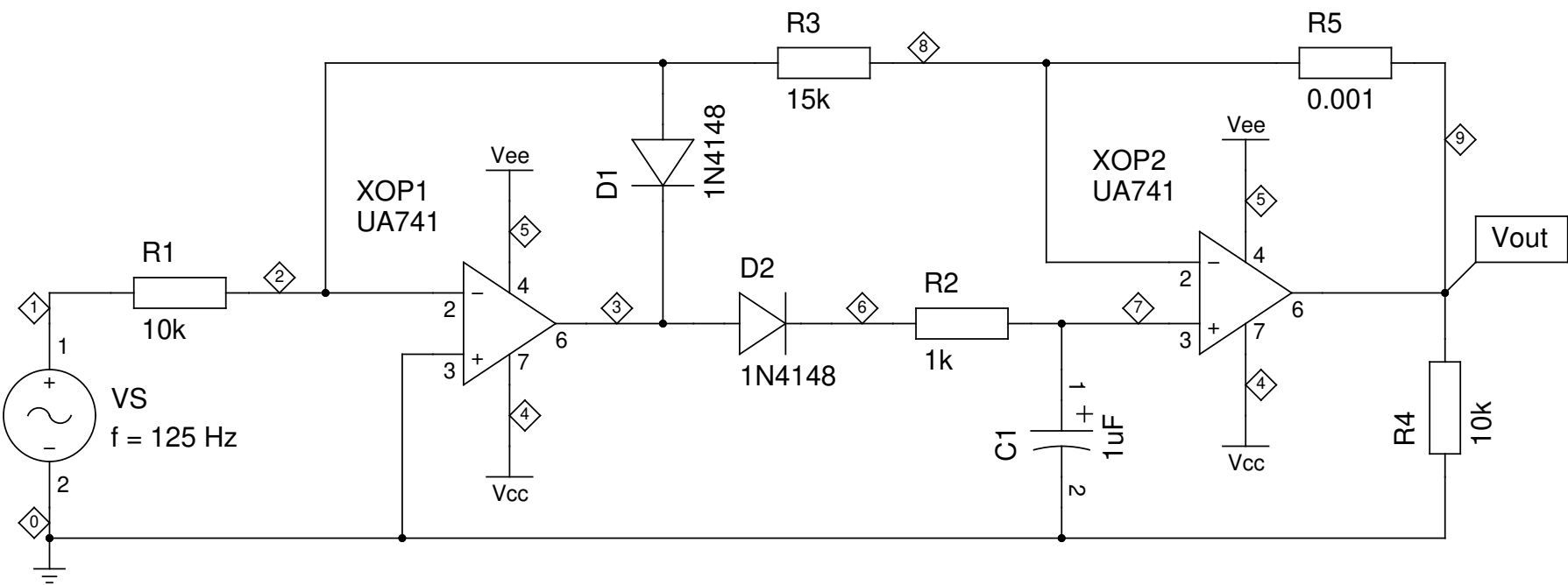

OCTAVE\_FILTER  
125 Hz Detector – Transient response (125 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.007.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 007: 125 HZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)



VS 1 0 AC 1 SIN(0 1.41 125)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iiter(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3) I(R4) I(R5) I(D1) I(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

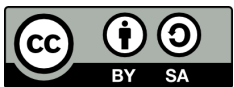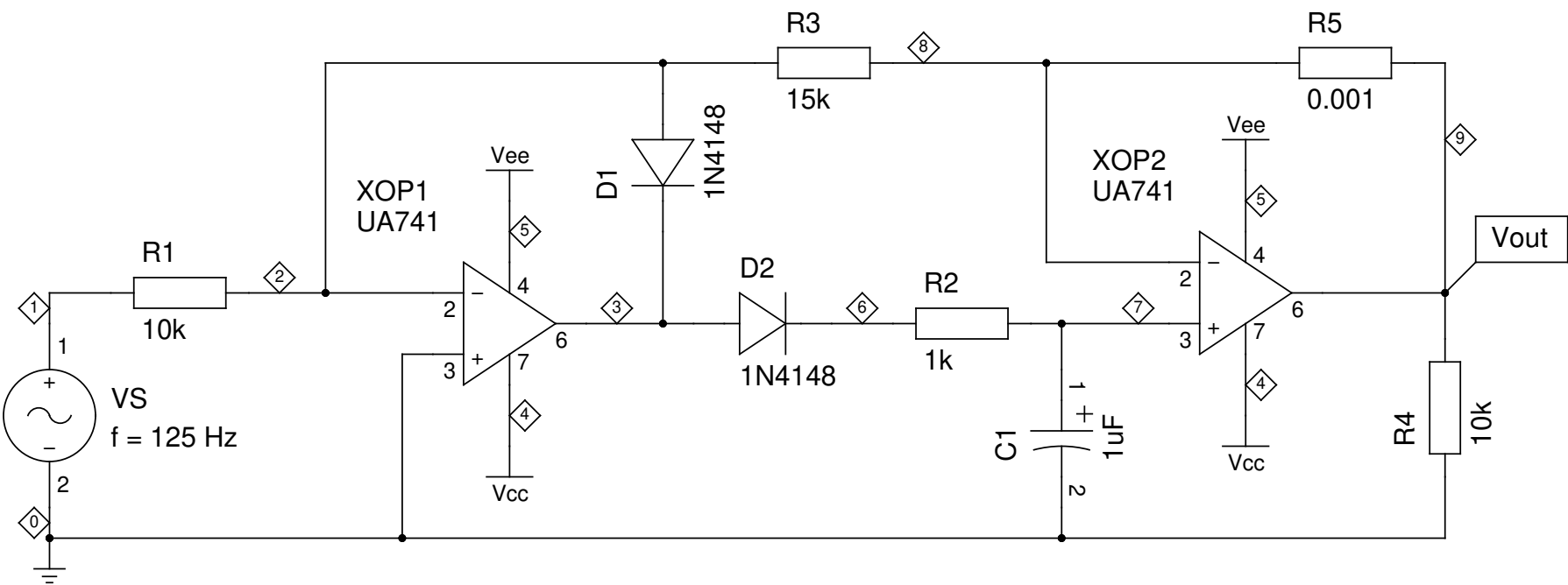

OCTAVE\_FILTER  
125 Hz Detector – Transient response (125 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.007.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 007: 125 HZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 125)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iiter(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3) P(R4) P(R5) P(D1) P(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

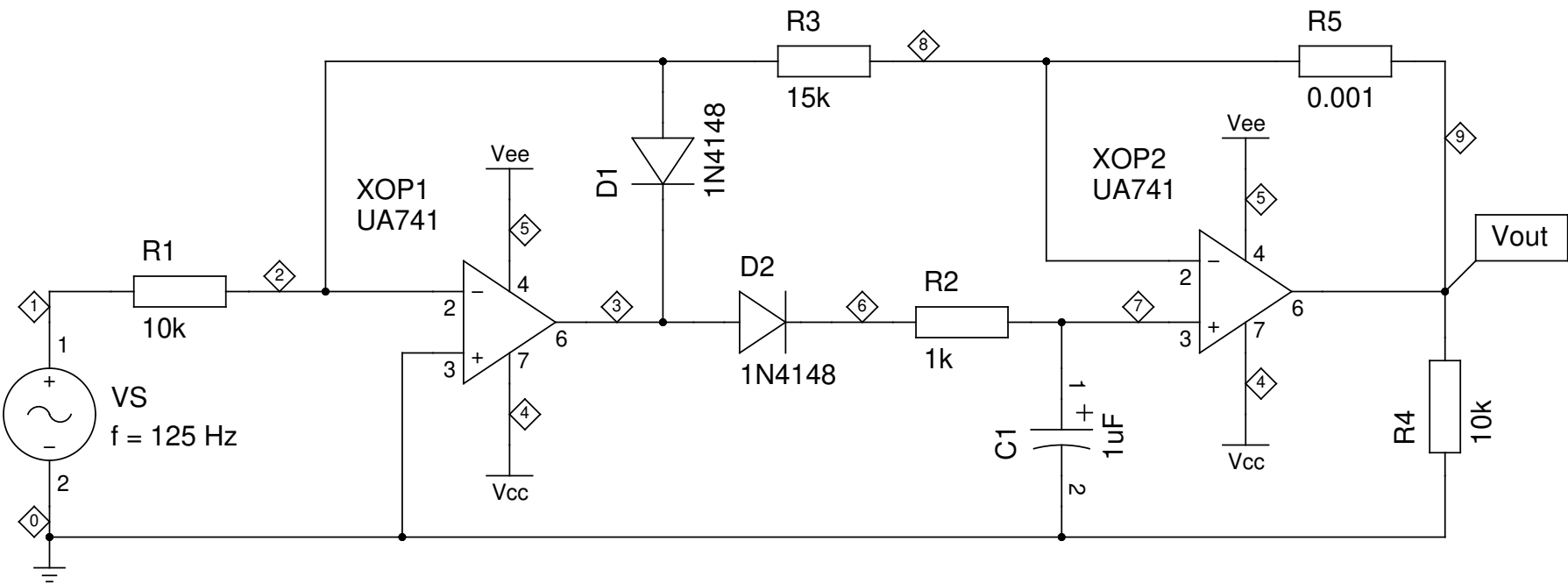

OCTAVE\_FILTER  
125 Hz Detector – Transient response (125 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.007.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

A3



.TITLE OCTAVE FILTER – FUNCTION 008: 250 HZ BAND–PASS FILTER – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 1 100)  
R1 1 2 18200  
R2 3 6 182K  
R3 0 2 7200  
C1 2 6 22nF  
C2 3 2 22nF  
XOP1 0 6 0 4 5 3 UA741


.PRINT OP Iter(0) V(3)

.PRINT AC VDB(3)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

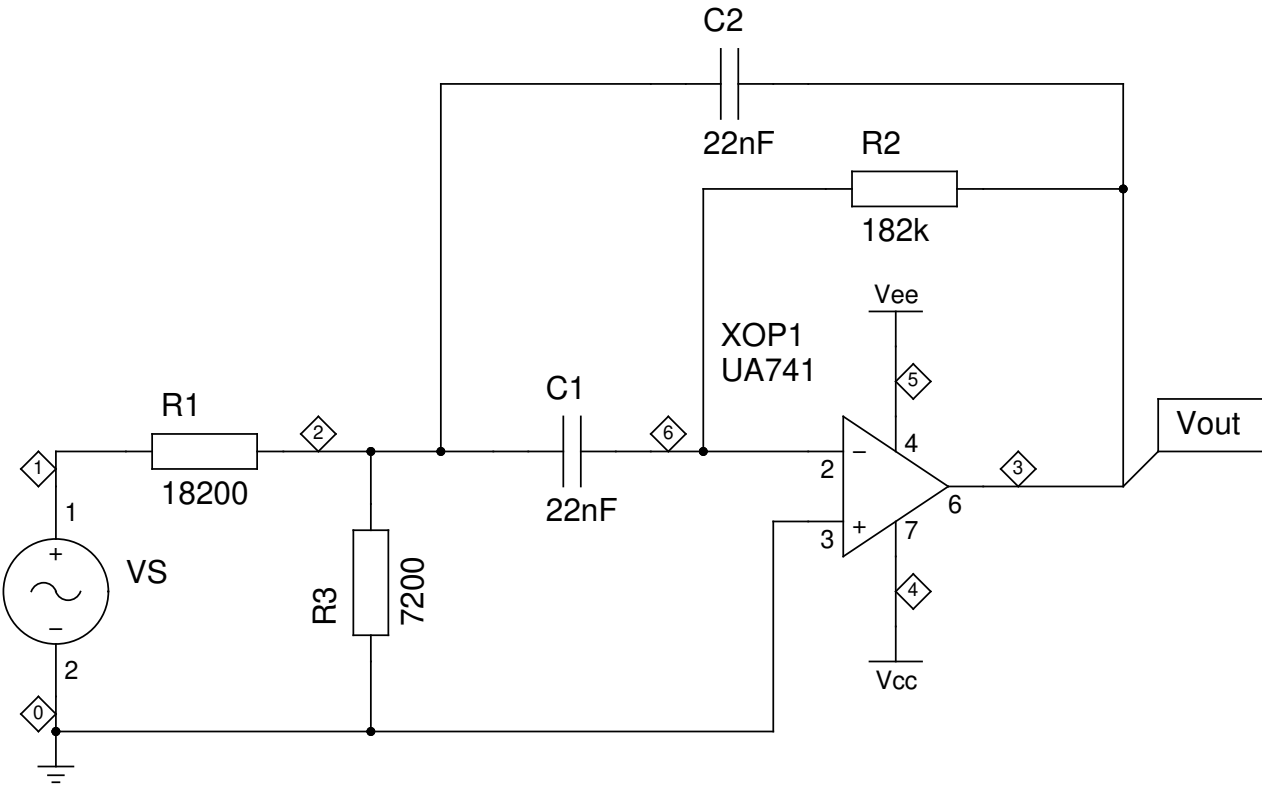

OCTAVE\_FILTER  
250 Hz Band-pass Filter – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.008.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 008: 250 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 250)  
R1 1 2 18200  
R2 3 6 182K  
R3 0 2 7200  
C1 2 6 22nF  
C2 3 2 22nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.05 0.00001 TRACE ALL

.END

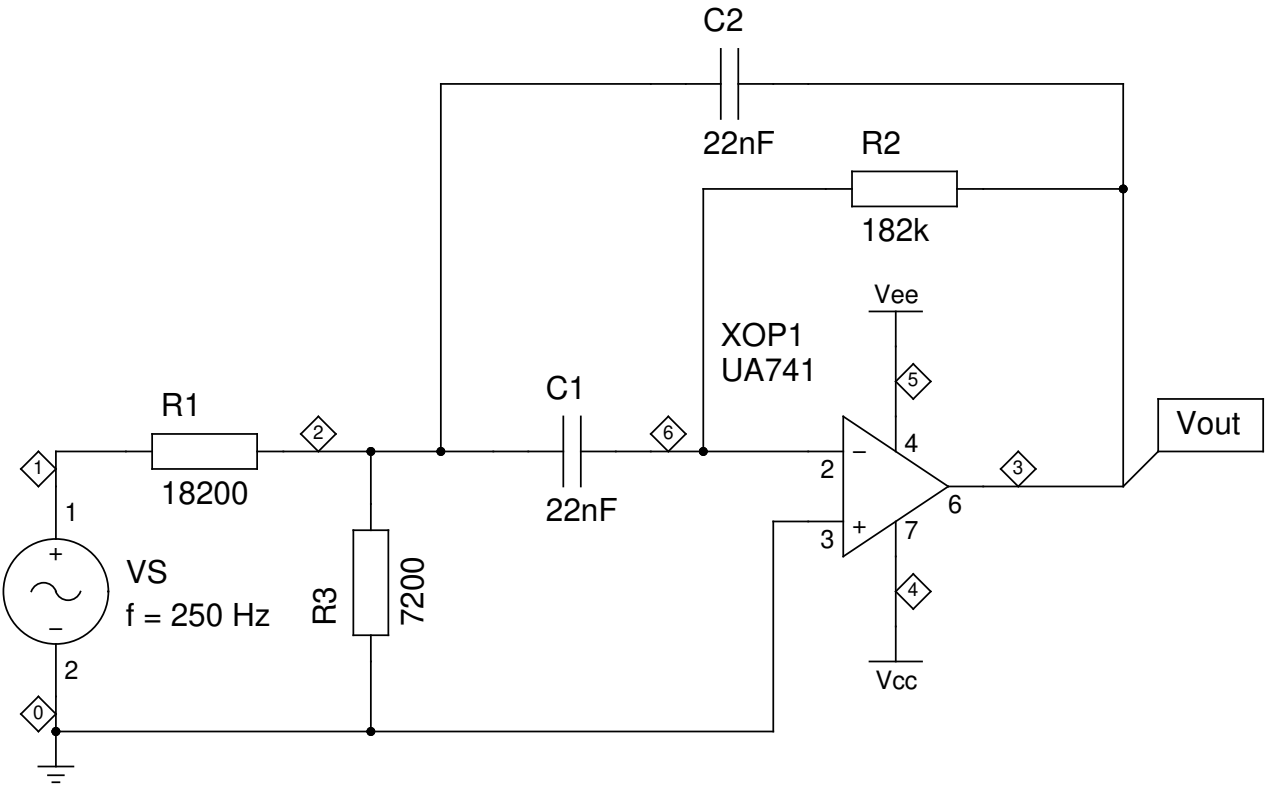

OCTAVE\_FILTER  
250 Hz Band-pass Filter – Transient response (250 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.008.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 008: 250 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 18200  
R2 3 6 182K  
R3 0 2 7200  
C1 2 6 22nF  
C2 3 2 22nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

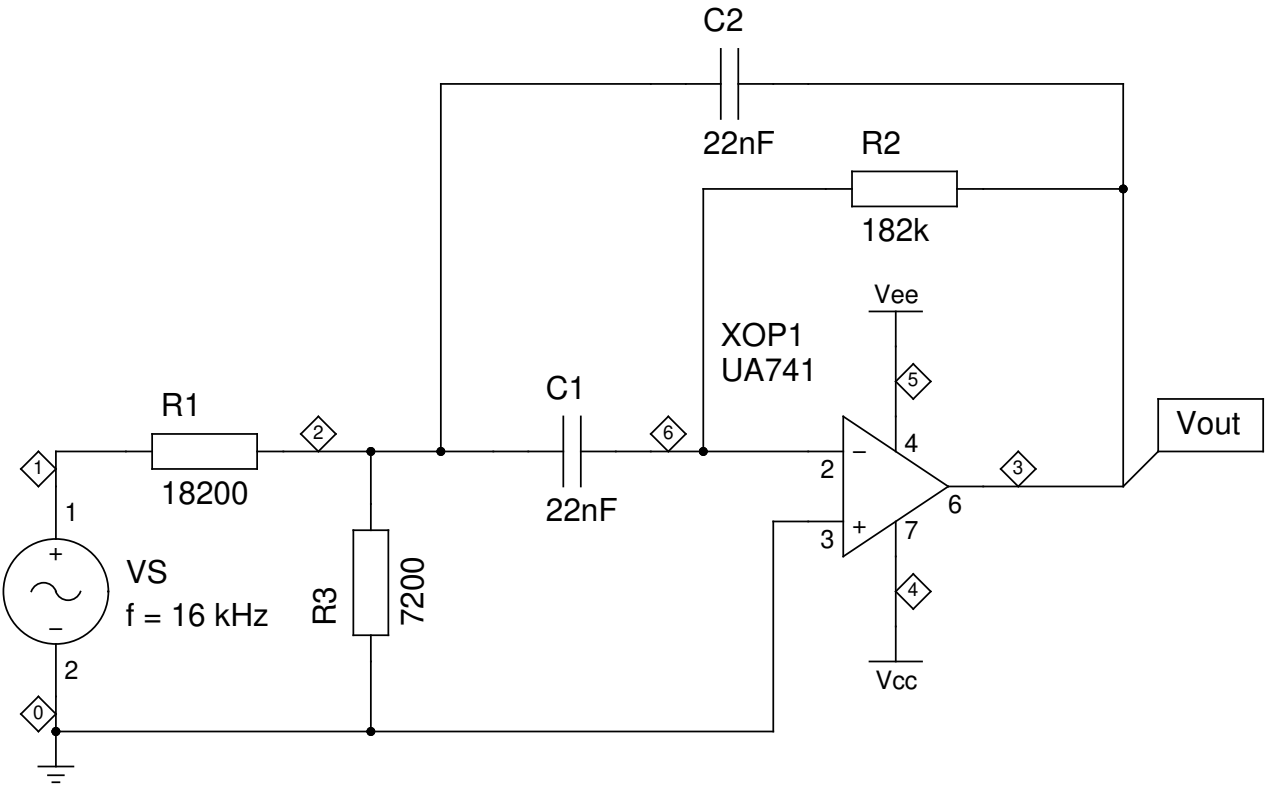

OCTAVE\_FILTER  
250 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.008.00.01.02.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 008: 250 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 250)  
R1 1 2 18200  
R2 3 6 182K  
R3 0 2 7200  
C1 2 6 22nF  
C2 3 2 22nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

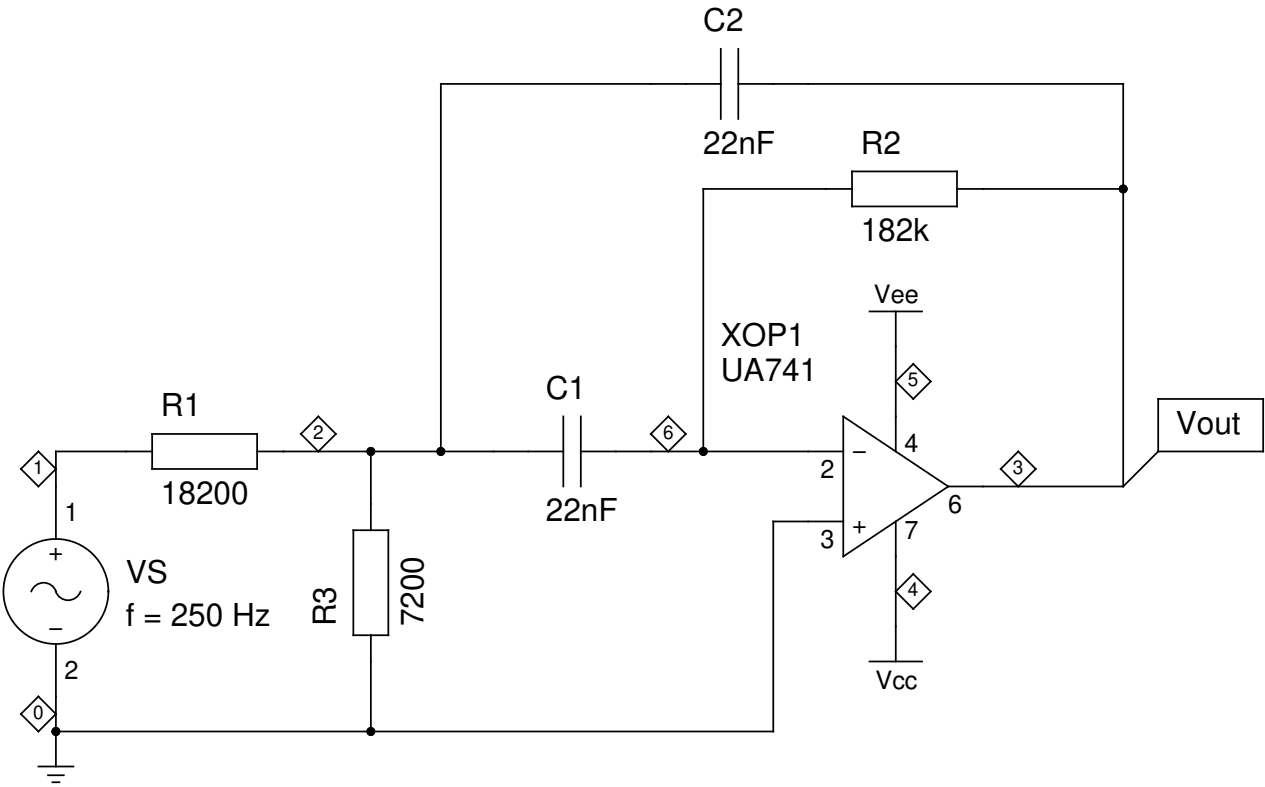

OCTAVE\_FILTER  
250 Hz Band-pass Filter – Transient response (250 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.008.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 008: 250 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 18200  
R2 3 6 182K  
R3 0 2 7200  
C1 2 6 22nF  
C2 3 2 22nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

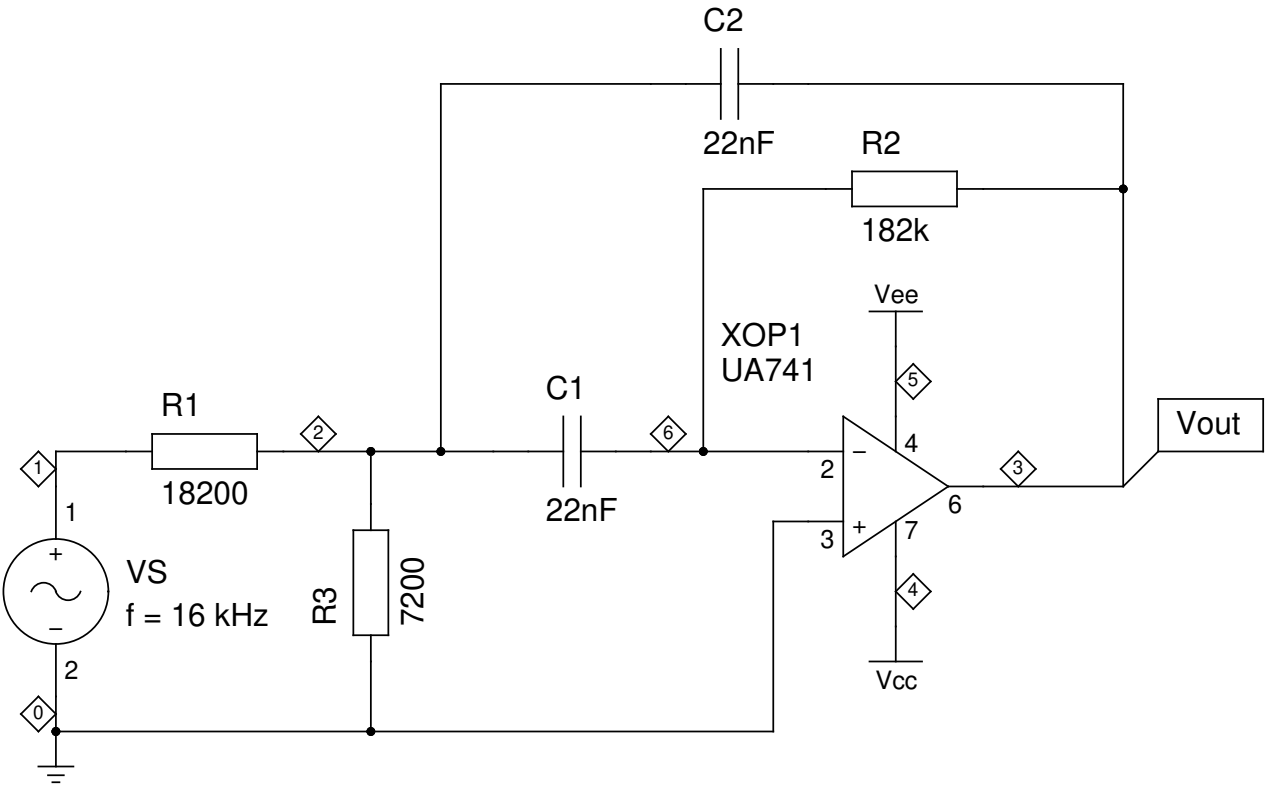

OCTAVE\_FILTER  
250 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.008.00.02.02.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 008: 250 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 250)  
R1 1 2 18200  
R2 3 6 182K  
R3 0 2 7200  
C1 2 6 22nF  
C2 3 2 22nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

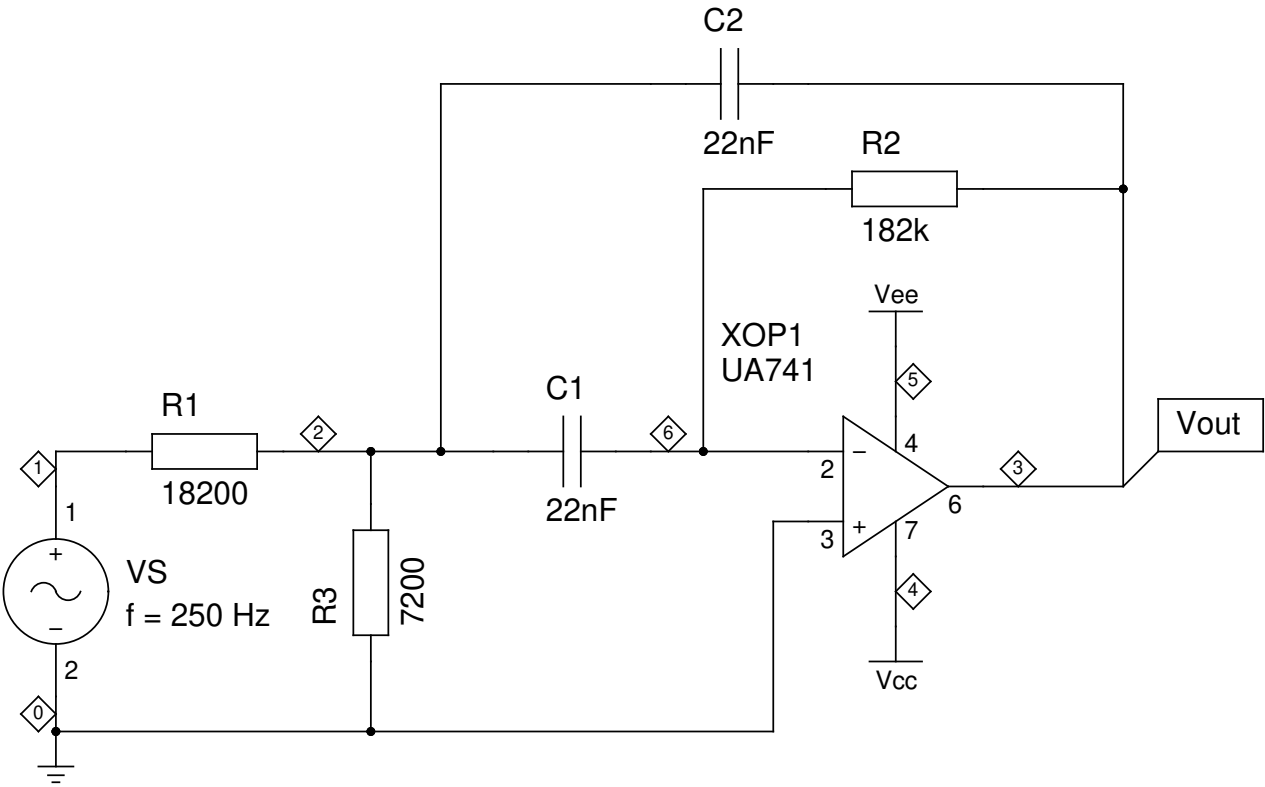


OCTAVE\_FILTER  
250 Hz Band-pass Filter – Transient response (250 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.008.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240525  
DRAWN BY: Bert Timmerman



.END

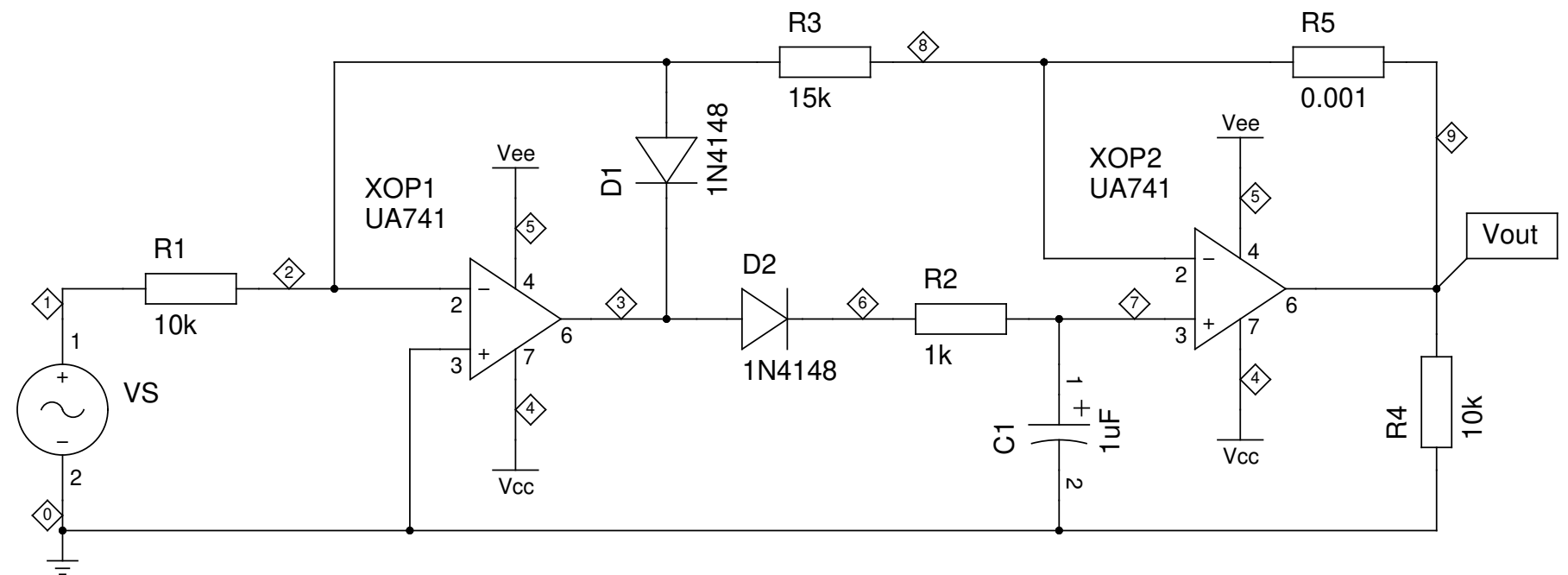

A3



.TITLE OCTAVE FILTER – FUNCTION 009: 250 HZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1 250)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(9) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.2 0.00001

.END

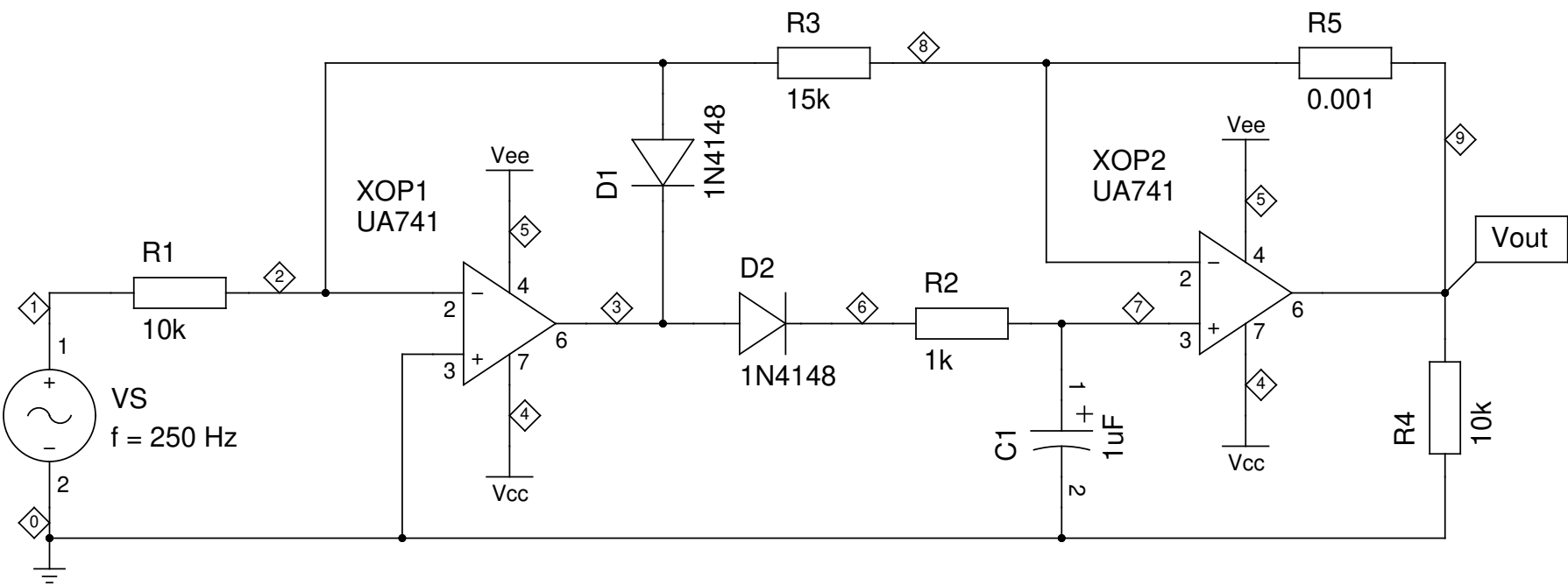

OCTAVE\_FILTER  
250 Hz Detector – Transient response (250 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.009.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240526  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 009: 250 HZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 250)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3) I(R4) I(R5) I(D1) I(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

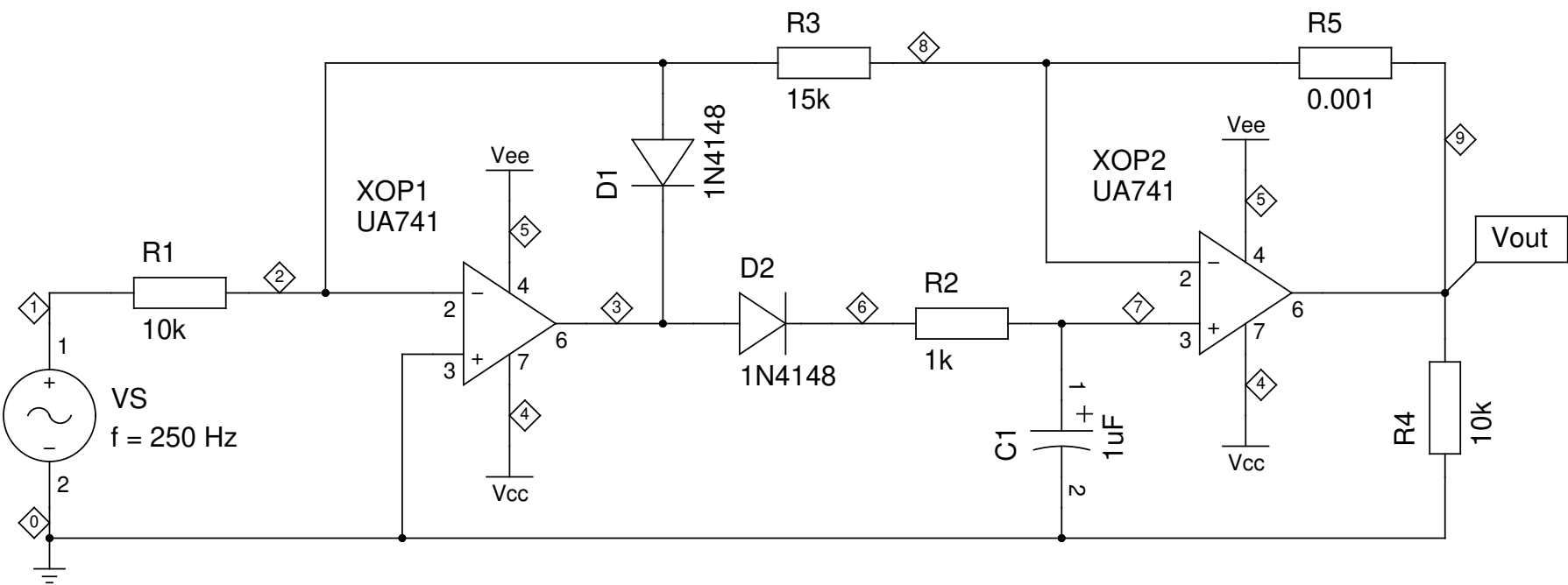

OCTAVE\_FILTER  
250 Hz Detector – Transient response (250 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.009.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240526  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 009: 250 HZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)



VS 1 0 AC 1 SIN(0 1.41 250)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iiter(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3) P(R4) P(R5) P(D1) P(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

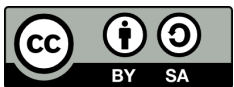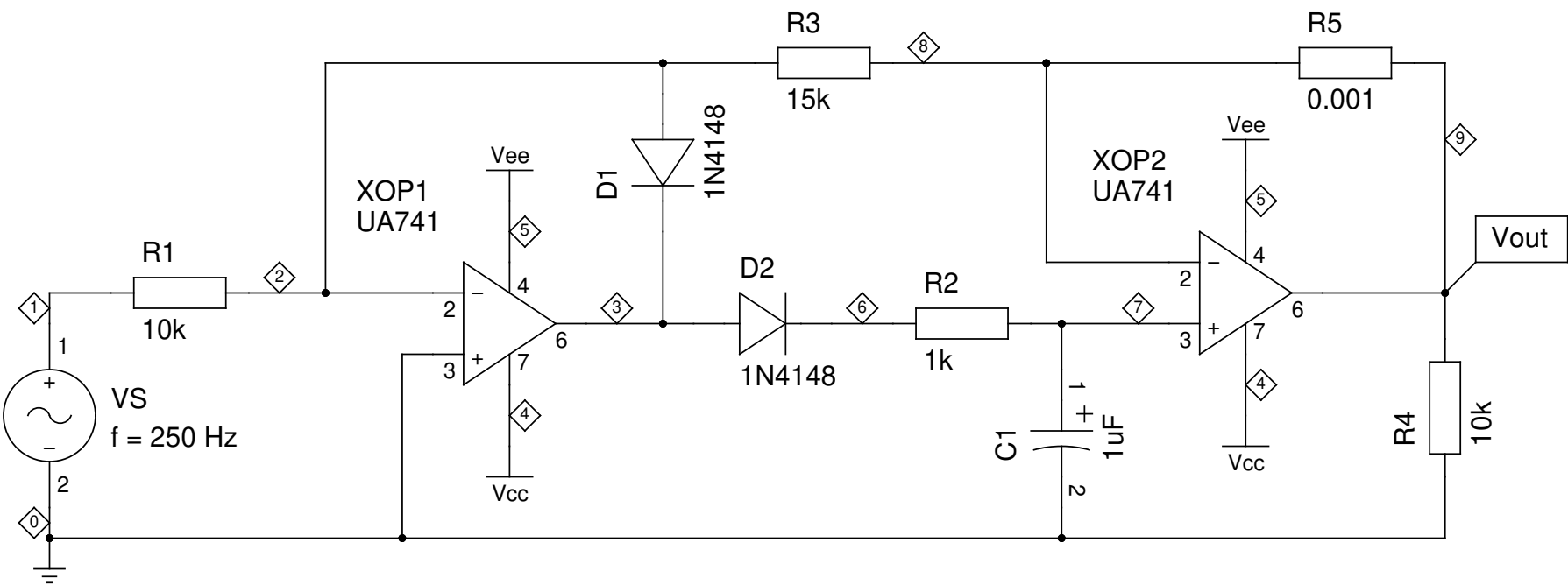

OCTAVE\_FILTER  
250 Hz Detector – Transient response (250 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.009.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240526  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 010: 500 HZ BAND–PASS FILTER – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 15  
VEE 5 0 –15

VS 1 0 AC 1 SIN(0 1.41 500)  
R1 1 2 20k  
R2 3 6 200K  
R3 0 2 8300  
C1 2 6 10nF  
C2 3 2 10nF  
XOP1 0 6 0 4 5 3 UA741


.PRINT OP Iter(0) V(3)

.PRINT AC VDB(3)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

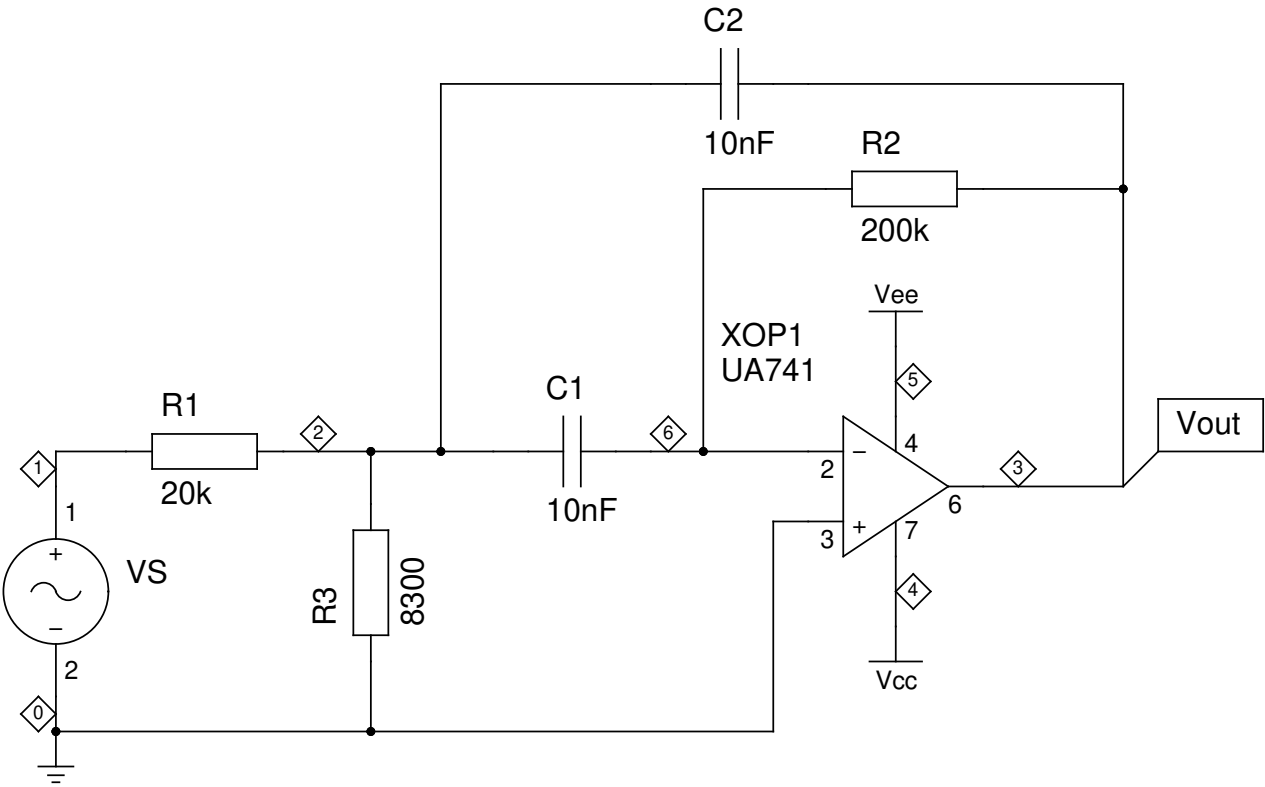

OCTAVE\_FILTER  
500 Hz Band-pass Filter – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.010.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240526  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 010: 500 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 500)  
R1 1 2 20k  
R2 3 6 200K  
R3 0 2 8300  
C1 2 6 10nF  
C2 3 2 10nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.05 0.00001 TRACE ALL

.END

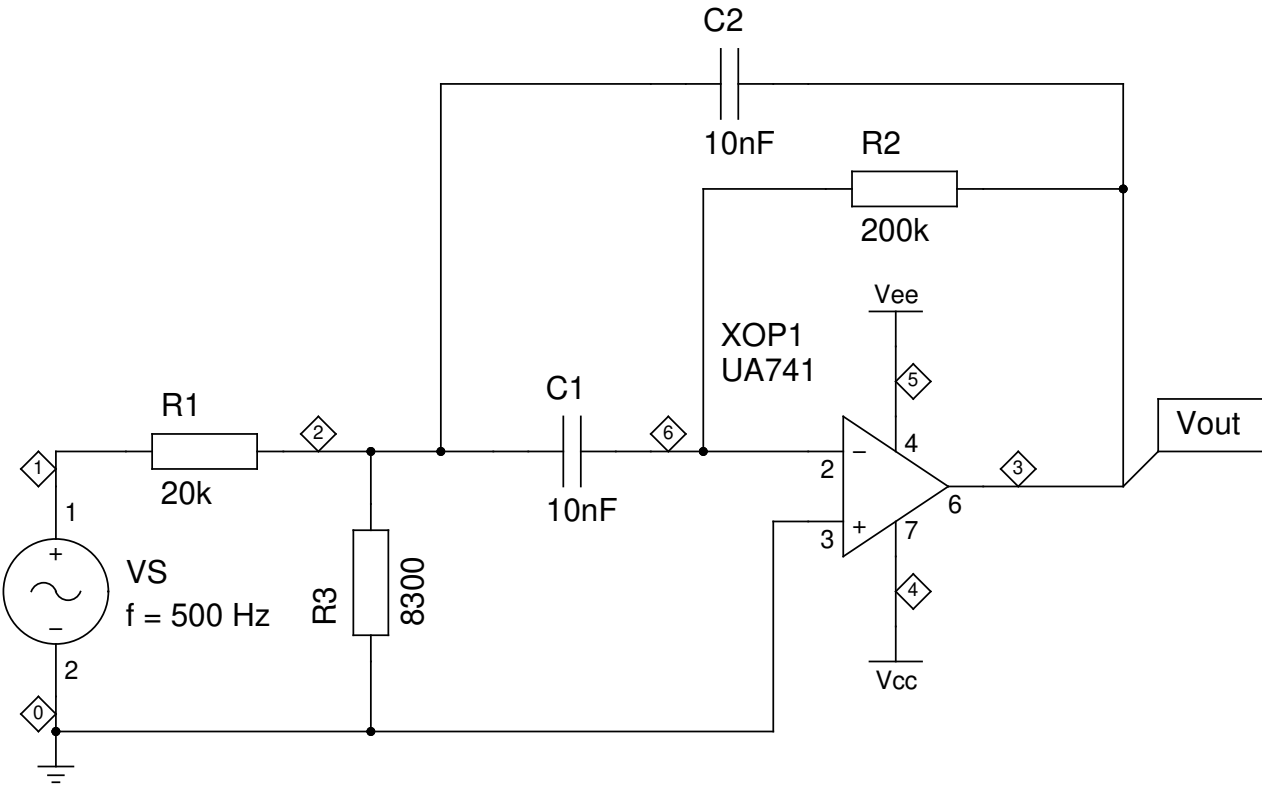

OCTAVE\_FILTER  
500 Hz Band-pass Filter – Transient response (500 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.010.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240526  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 010: 500 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 20k  
R2 3 6 200K  
R3 0 2 8300  
C1 2 6 10nF  
C2 3 2 10nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

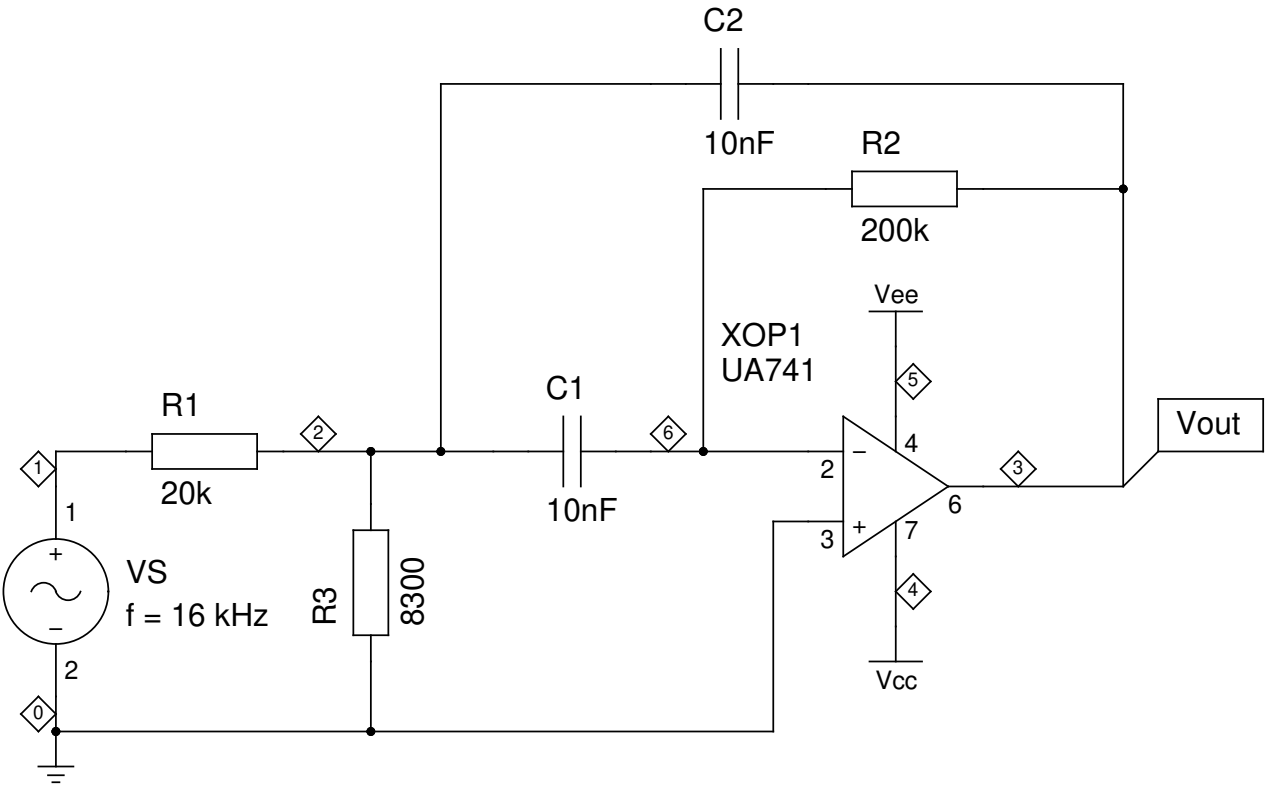

OCTAVE\_FILTER  
500 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.010.00.01.02.sch  
PAGE 01 OF 01

REVISION: 20240526  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 010: 500 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 500)  
R1 1 2 20k  
R2 3 6 200K  
R3 0 2 8300  
C1 2 6 10nF  
C2 3 2 10nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

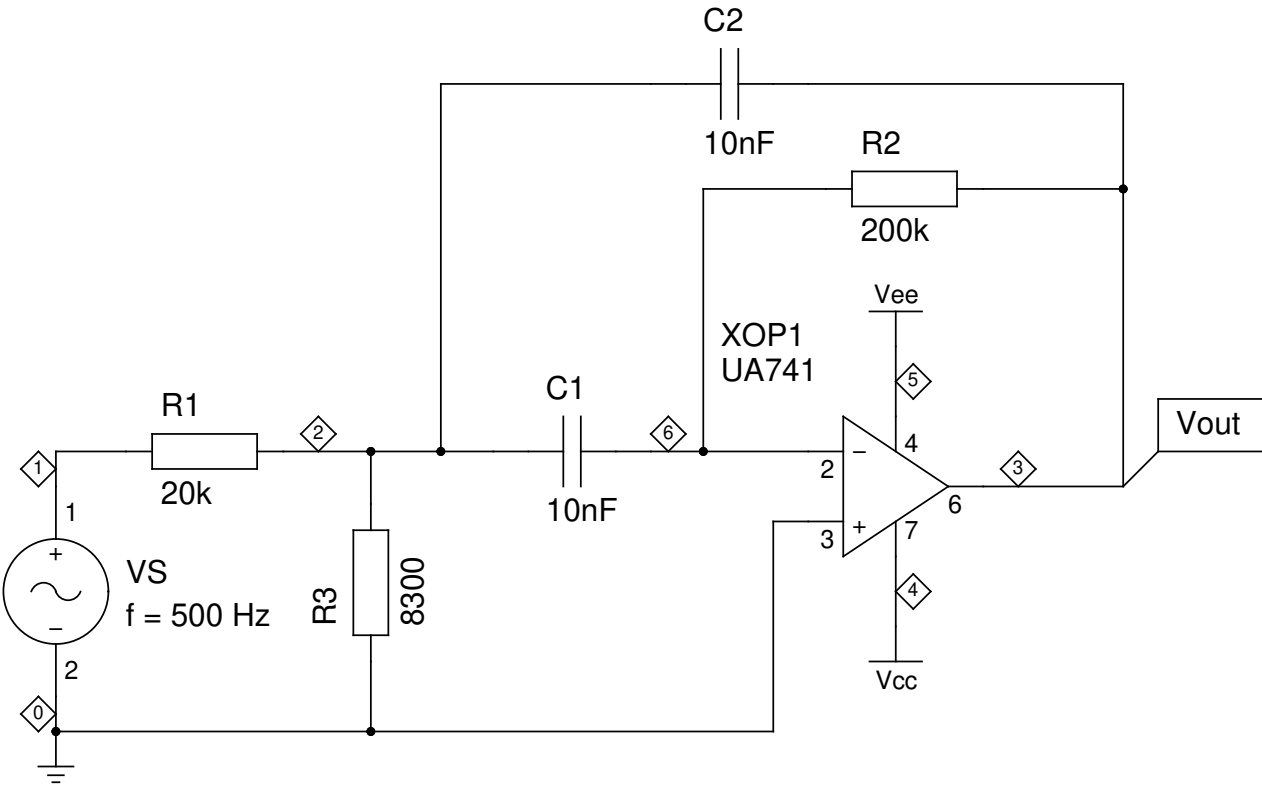

OCTAVE\_FILTER  
500 Hz Band-pass Filter – Transient response (500 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.010.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240526  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 010: 500 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 20k  
R2 3 6 200K  
R3 0 2 8300  
C1 2 6 10nF  
C2 3 2 10nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

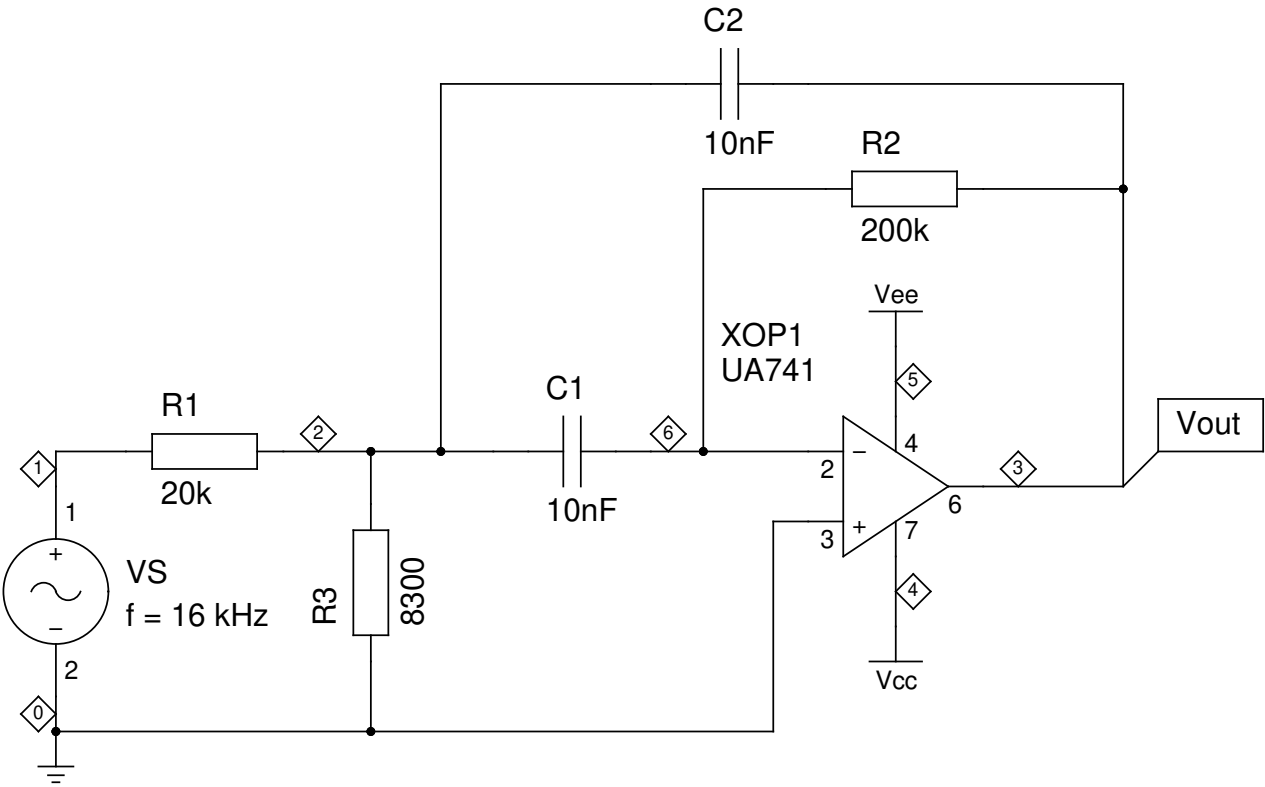

OCTAVE\_FILTER  
500 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.010.00.02.02.sch  
PAGE 01 OF 01

REVISION: 20240526  
DRAWN BY: Bert Timmerman



.TITLE OCTAVE FILTER – FUNCTION 010: 500 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 500)  
R1 1 2 20k  
R2 3 6 200K  
R3 0 2 8300  
C1 2 6 10nF  
C2 3 2 10nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

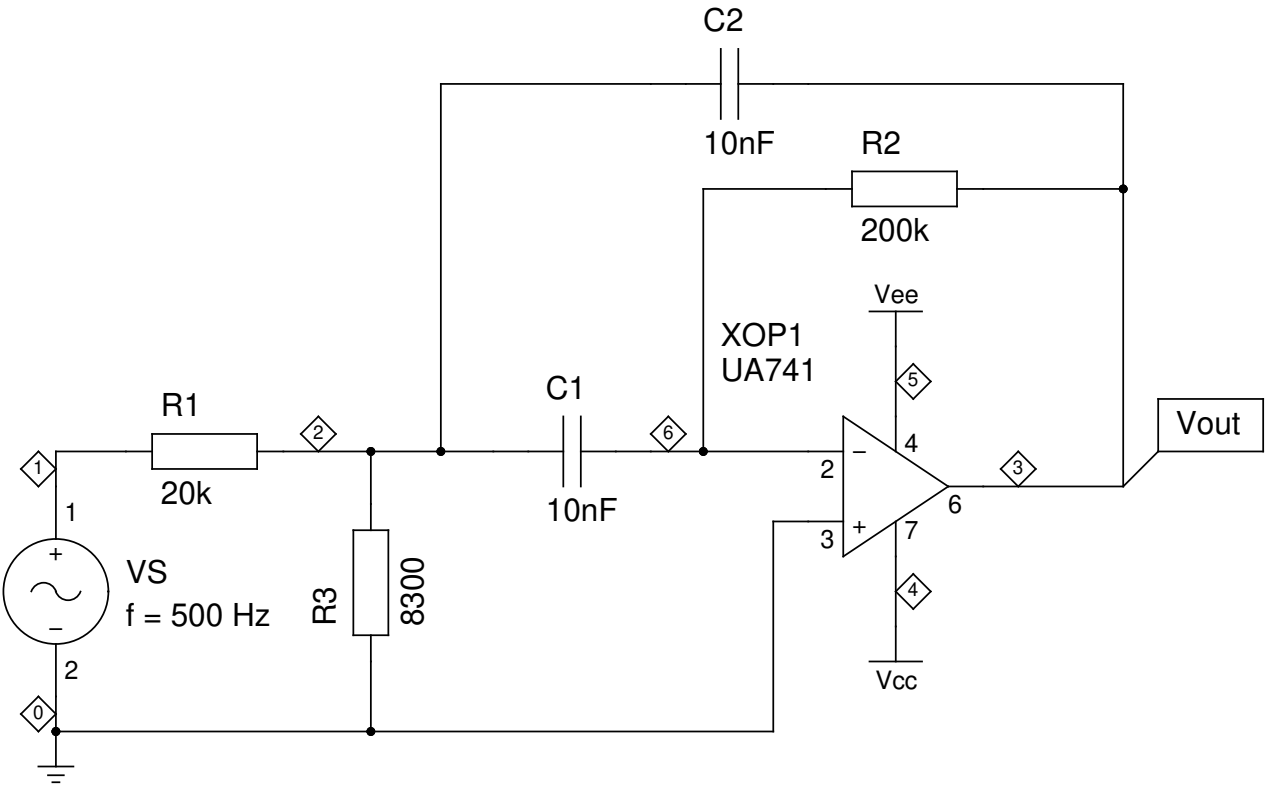

OCTAVE\_FILTER  
500 Hz Band-pass Filter – Transient response (500 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.010.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240527  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 010: 500 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 20k  
R2 3 6 200K  
R3 0 2 8300  
C1 2 6 10nF  
C2 3 2 10nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

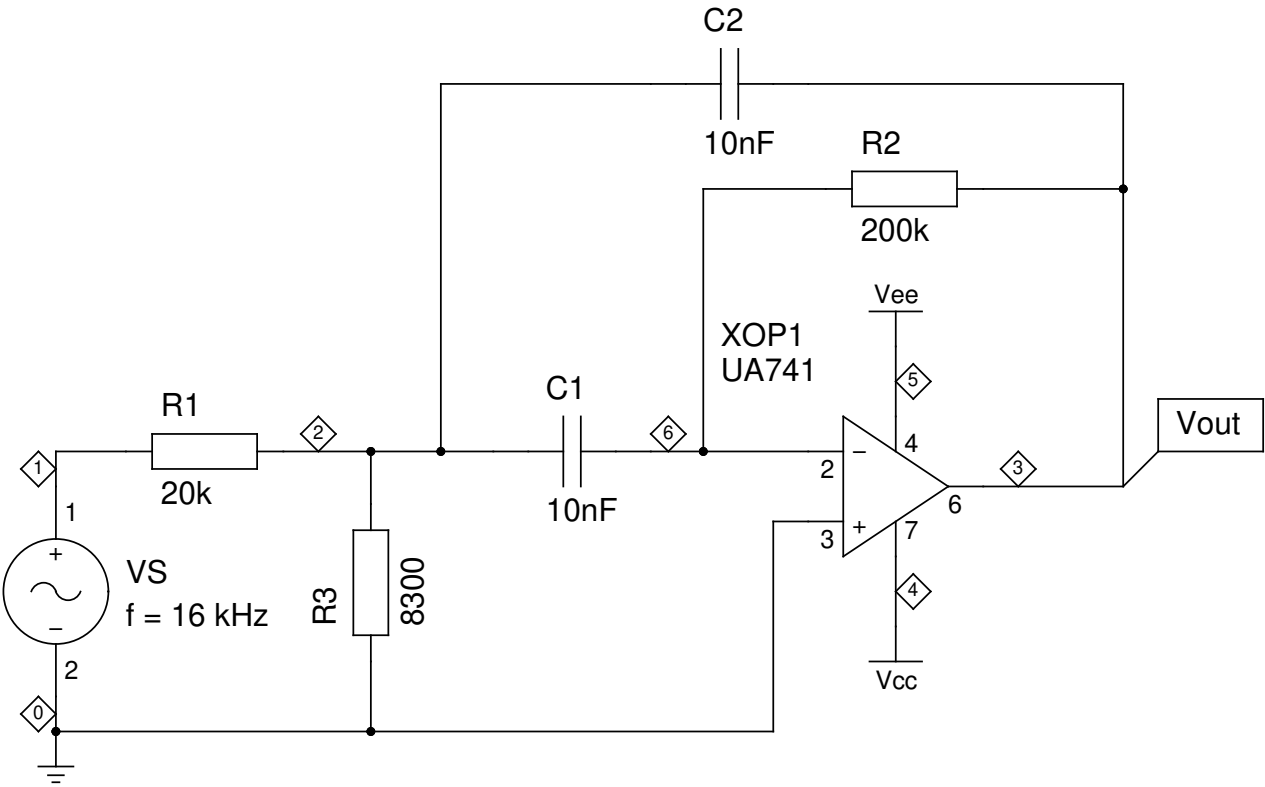

OCTAVE\_FILTER  
500 Hz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.010.00.03.02.sch  
PAGE 01 OF 01

REVISION: 20240527  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 011: 500 HZ DETECTOR – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 1 500)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741


.PRINT OP Iter(0) V(3)

.PRINT AC VDB(3) VDB(9)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

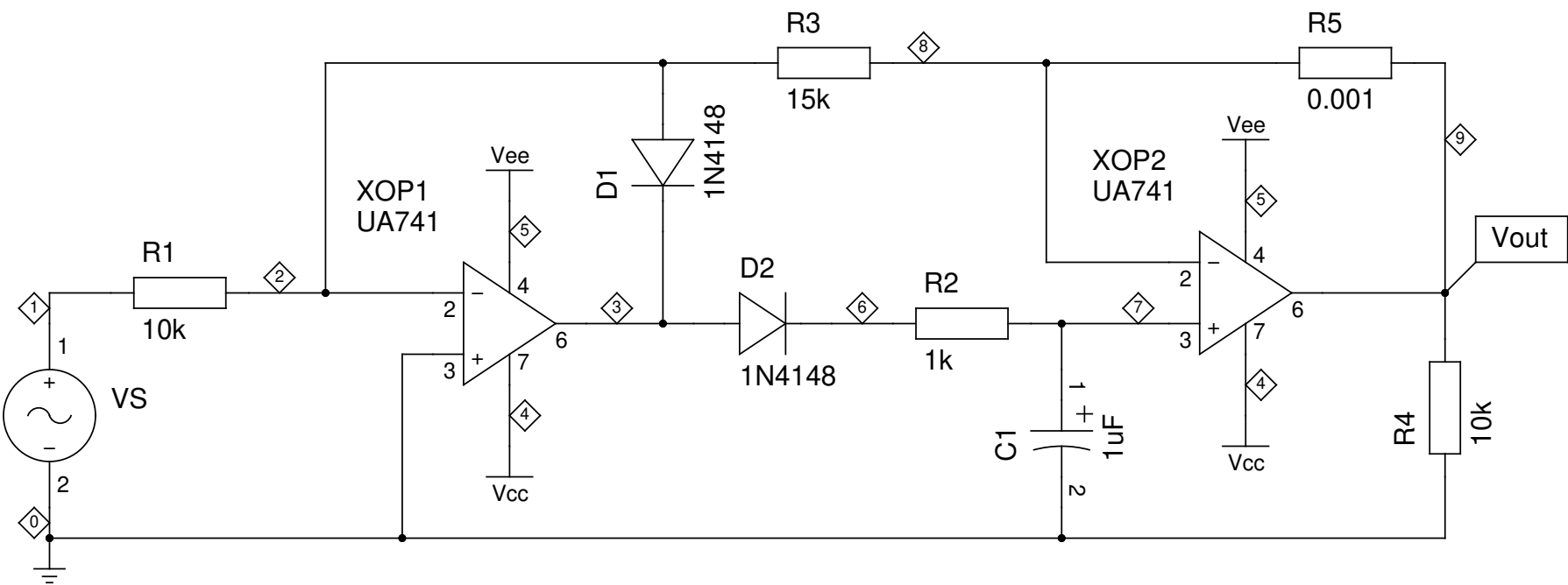

OCTAVE\_FILTER  
500 Hz Detector – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.011.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240527  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 011: 500 HZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)



VS 1 0 AC 1 SIN(0 1 500)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(9) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

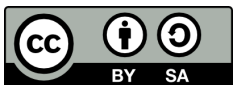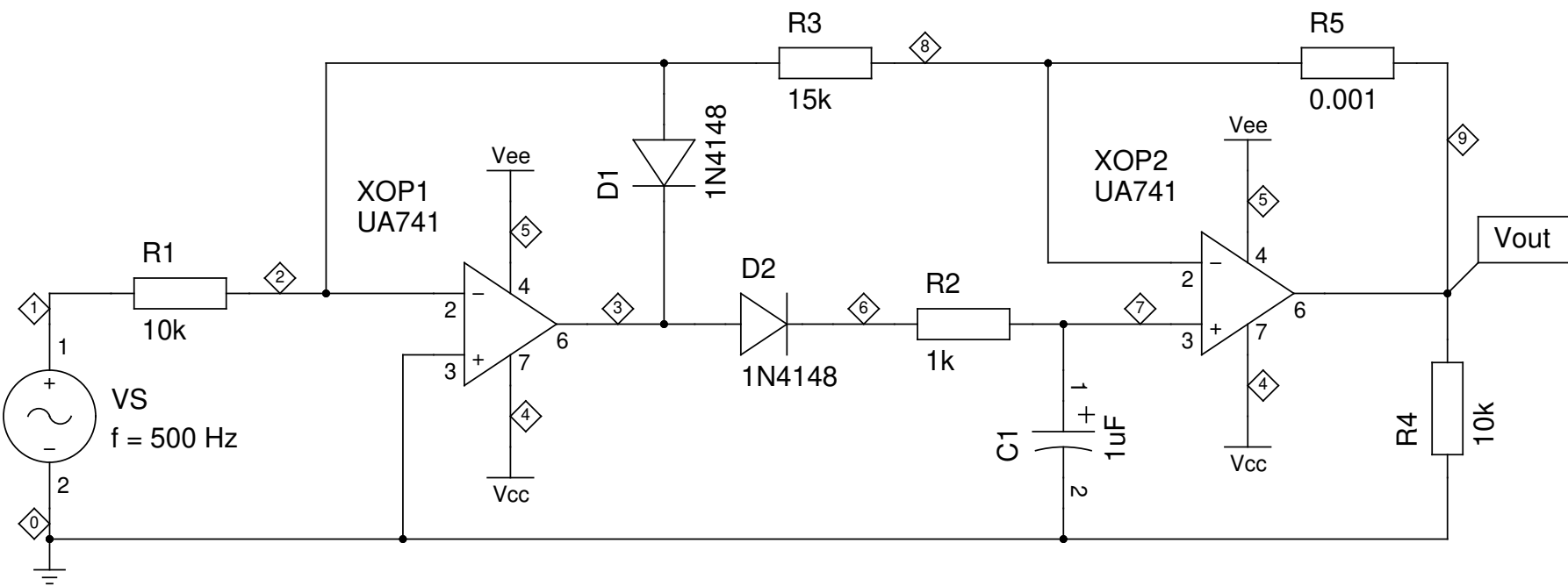

OCTAVE\_FILTER  
500 Hz Detector – Transient response (500 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.011.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240527  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 011: 500 HZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 500)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3) I(R4) I(R5) I(D1) I(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

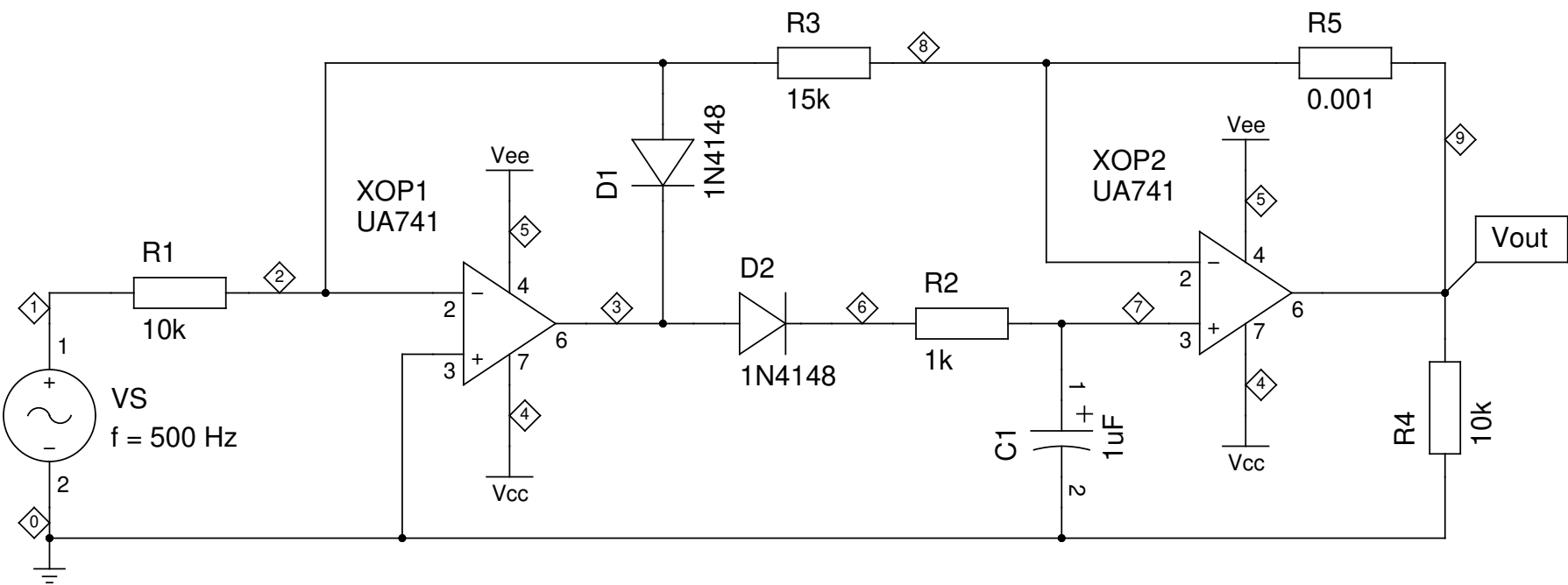

OCTAVE\_FILTER  
500 Hz Detector – Transient response (500 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.011.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240527  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 011: 500 HZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 500)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iiter(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3) P(R4) P(R5) P(D1) P(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

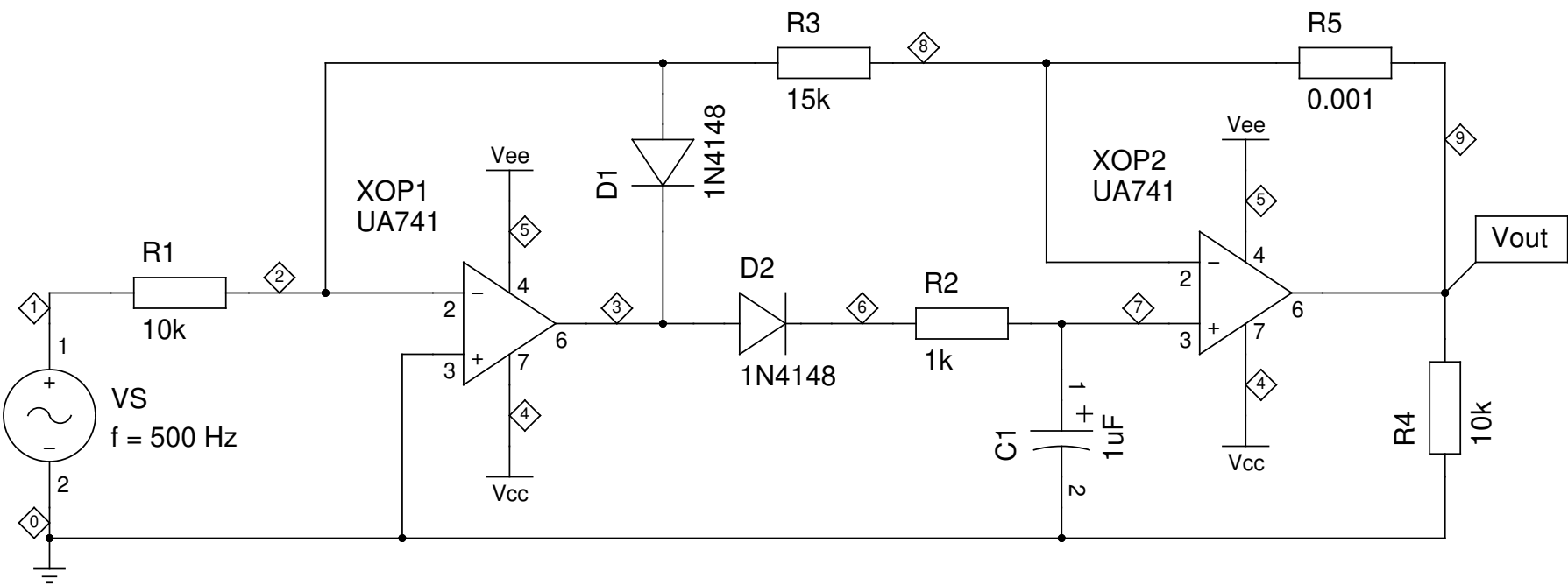

OCTAVE\_FILTER  
500 Hz Detector – Transient response (500 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.011.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240527  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 012: 1 kHz BAND-PASS FILTER – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 1.41 1k)  
R1 1 2 21.3k  
R2 3 6 213K  
R3 0 2 8300  
C1 2 6 4.7nF  
C2 3 2 4.7nF  
XOP1 0 6 0 4 5 3 UA741


.PRINT OP Iter(0) V(3)

.PRINT AC VDB(3)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

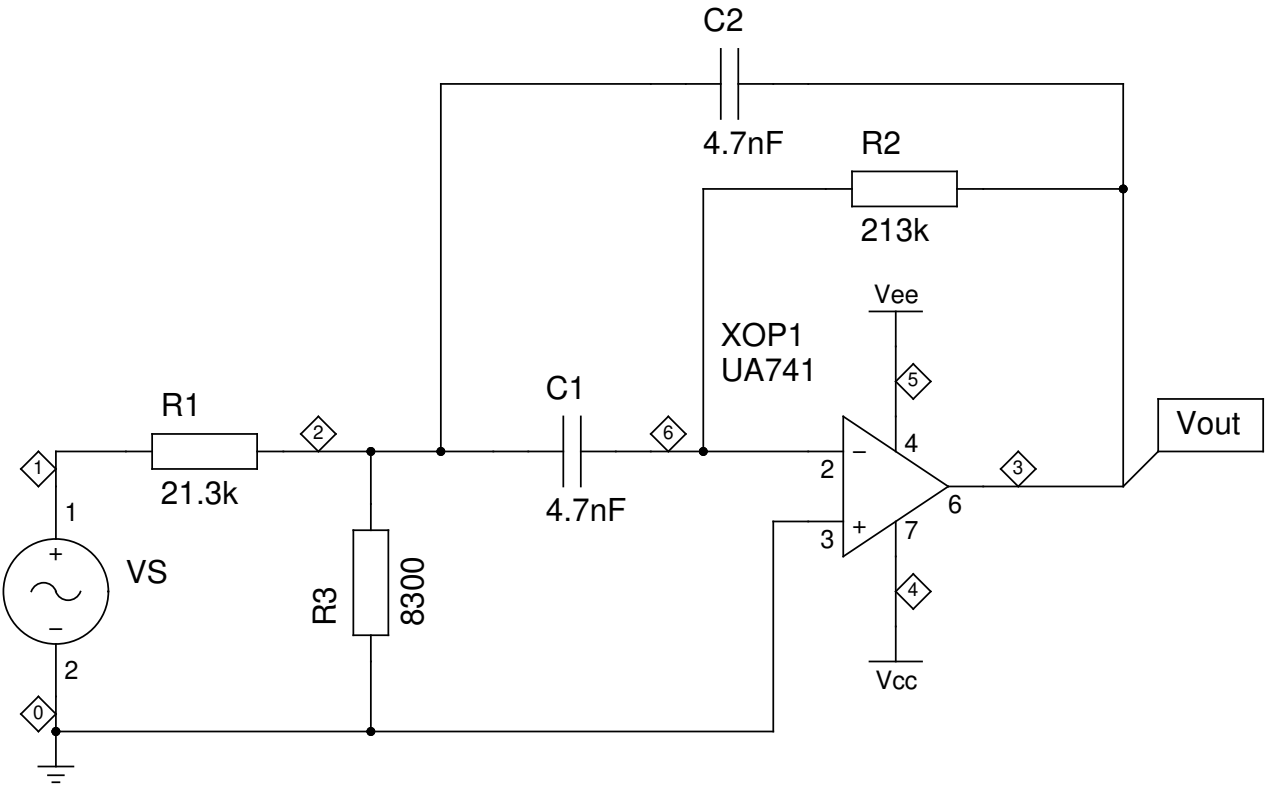

OCTAVE\_FILTER  
1 kHz Band-pass Filter – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.012.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240528  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 012: 1 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 1k)  
R1 1 2 21.3k  
R2 3 6 213K  
R3 0 2 8300  
C1 2 6 4.7nF  
C2 3 2 4.7nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.05 0.00001 TRACE ALL

.END

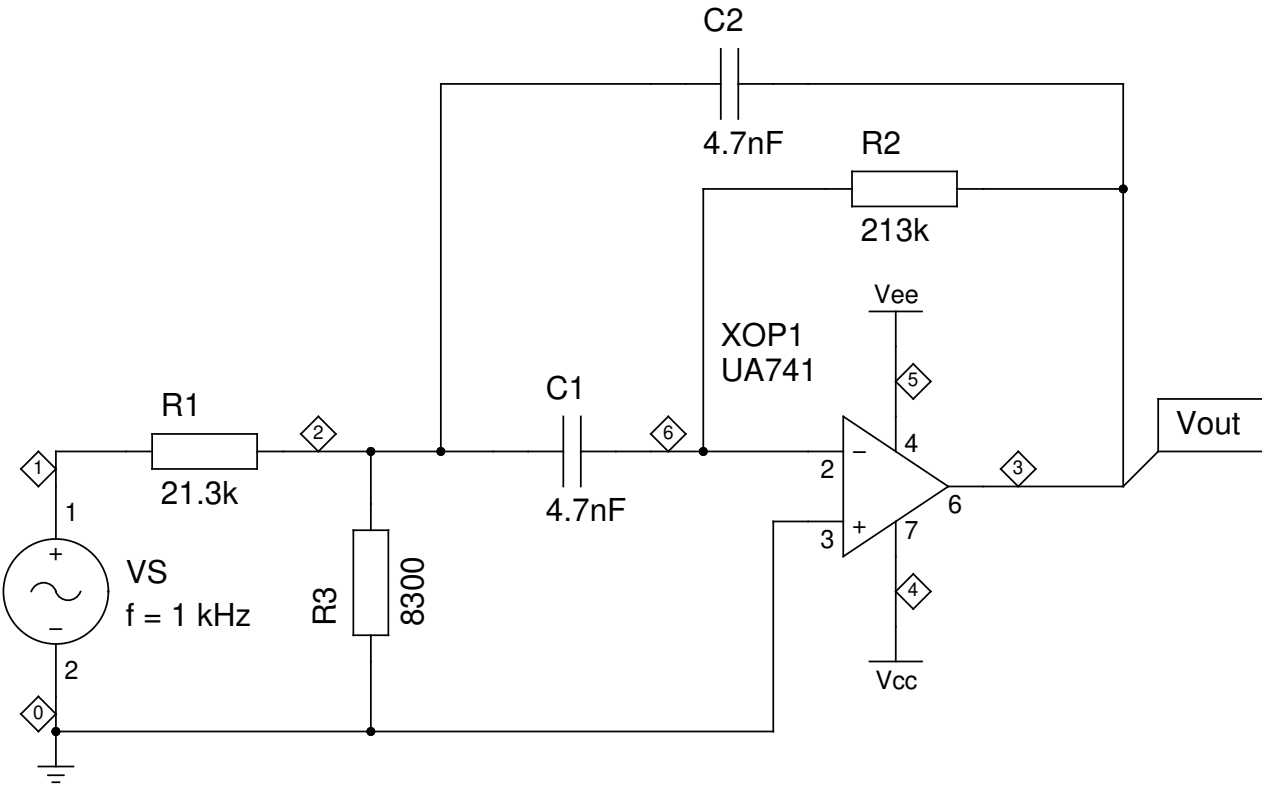

OCTAVE\_FILTER  
1 kHz Band-pass Filter – Transient response (1 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.012.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240528  
DRAWN BY: Bert Timmerman



.TITLE OCTAVE FILTER – FUNCTION 012: 1 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 21.3k  
R2 3 6 213K  
R3 0 2 8300  
C1 2 6 4.7nF  
C2 3 2 4.7nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

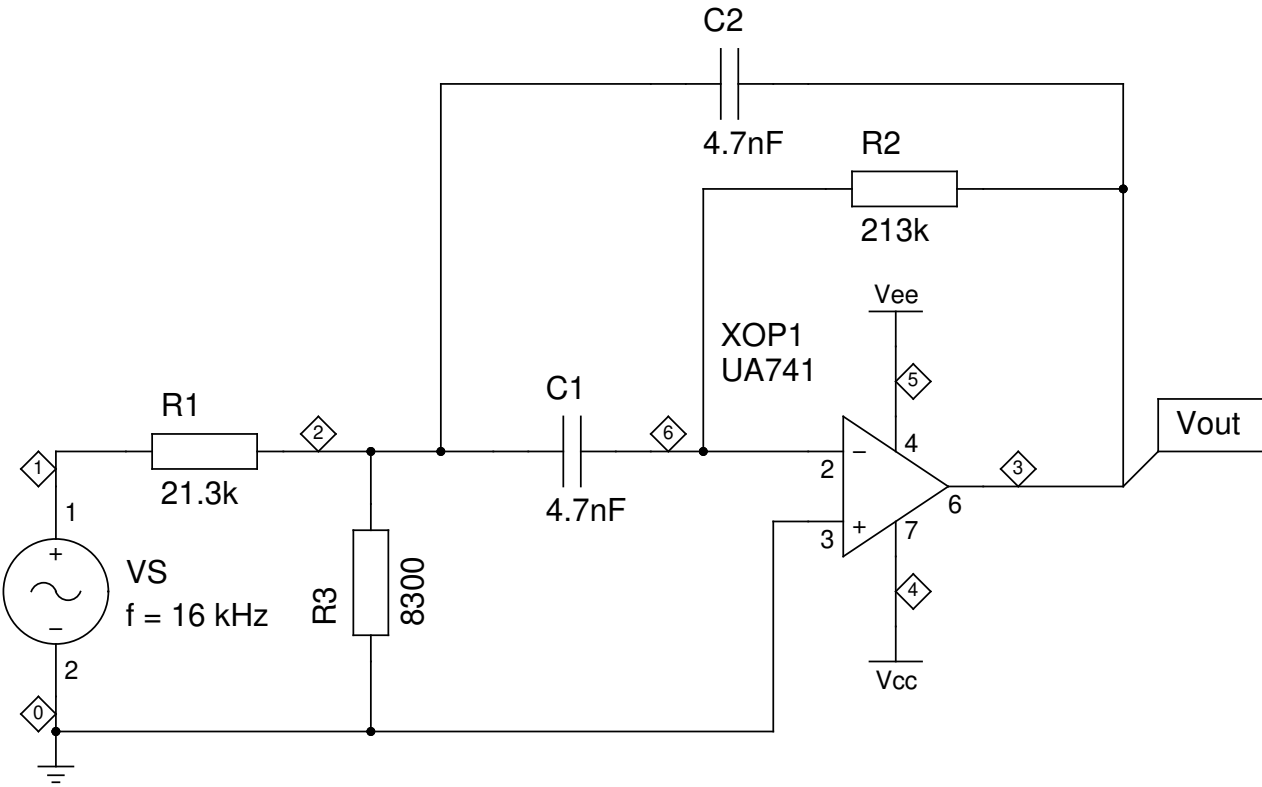

OCTAVE\_FILTER  
1 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.012.00.01.02.sch  
PAGE 01 OF 01

REVISION: 20240528  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 012: 1 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 21.3k  
R2 3 6 213K  
R3 0 2 8300  
C1 2 6 4.7nF  
C2 3 2 4.7nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

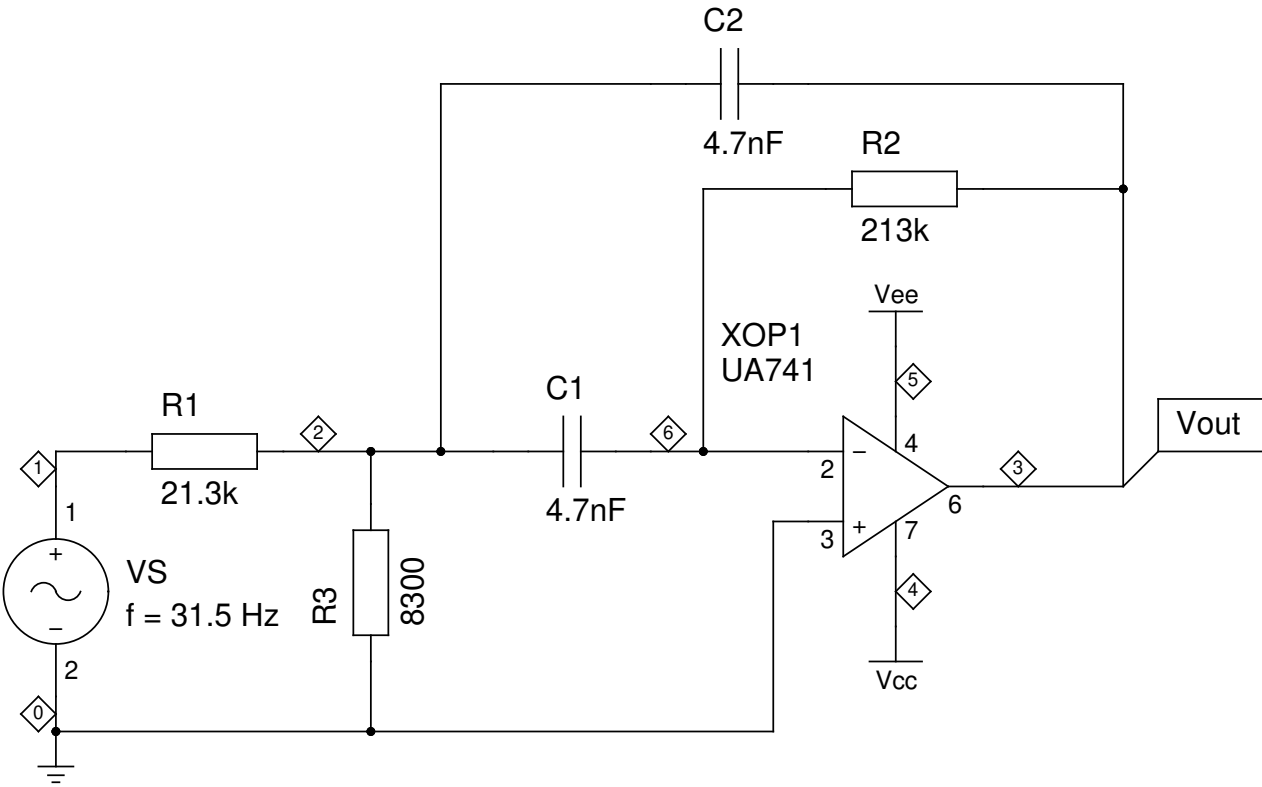

OCTAVE\_FILTER  
1 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.012.00.01.03.sch  
PAGE 01 OF 01

REVISION: 20240528  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 012: 1 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 1k)  
R1 1 2 21.3k  
R2 3 6 213K  
R3 0 2 8300  
C1 2 6 4.7nF  
C2 3 2 4.7nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

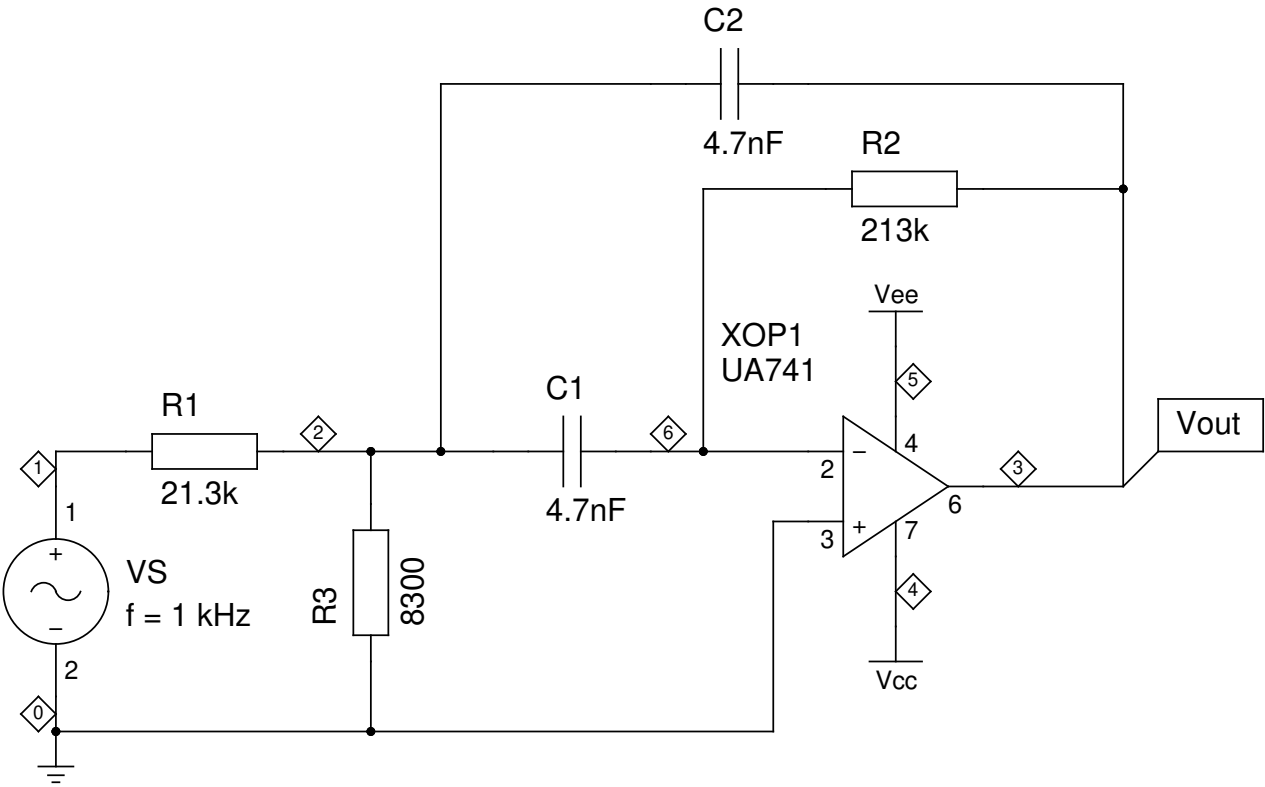

OCTAVE\_FILTER  
1 kHz Band-pass Filter – Transient response (1 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.012.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240528  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 012: 1 KHZ BAND-PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 21.3k  
R2 3 6 213K  
R3 0 2 8300  
C1 2 6 4.7nF  
C2 3 2 4.7nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

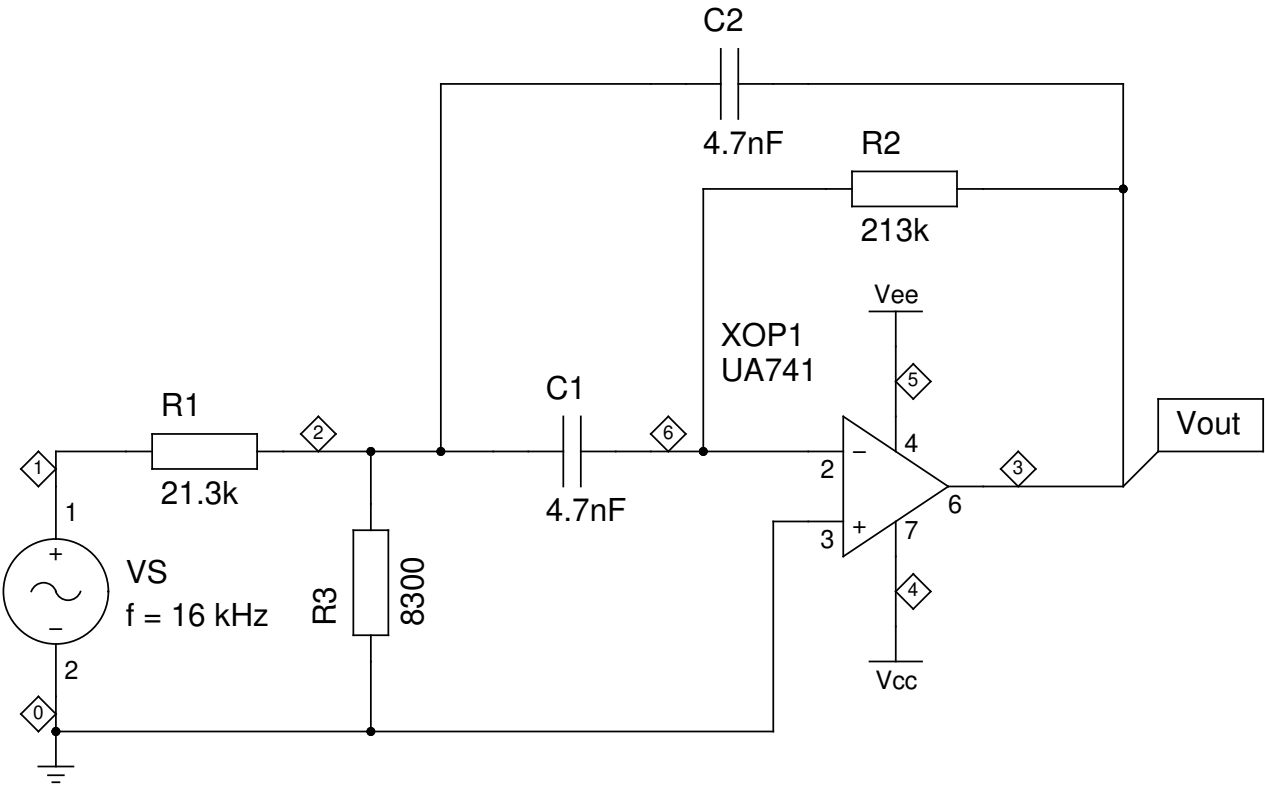

OCTAVE\_FILTER  
1 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.012.00.02.02.sch  
PAGE 01 OF 01

REVISION: 20240529  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 012: 1 KHZ BAND-PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 21.3k  
R2 3 6 213K  
R3 0 2 8300  
C1 2 6 4.7nF  
C2 3 2 4.7nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

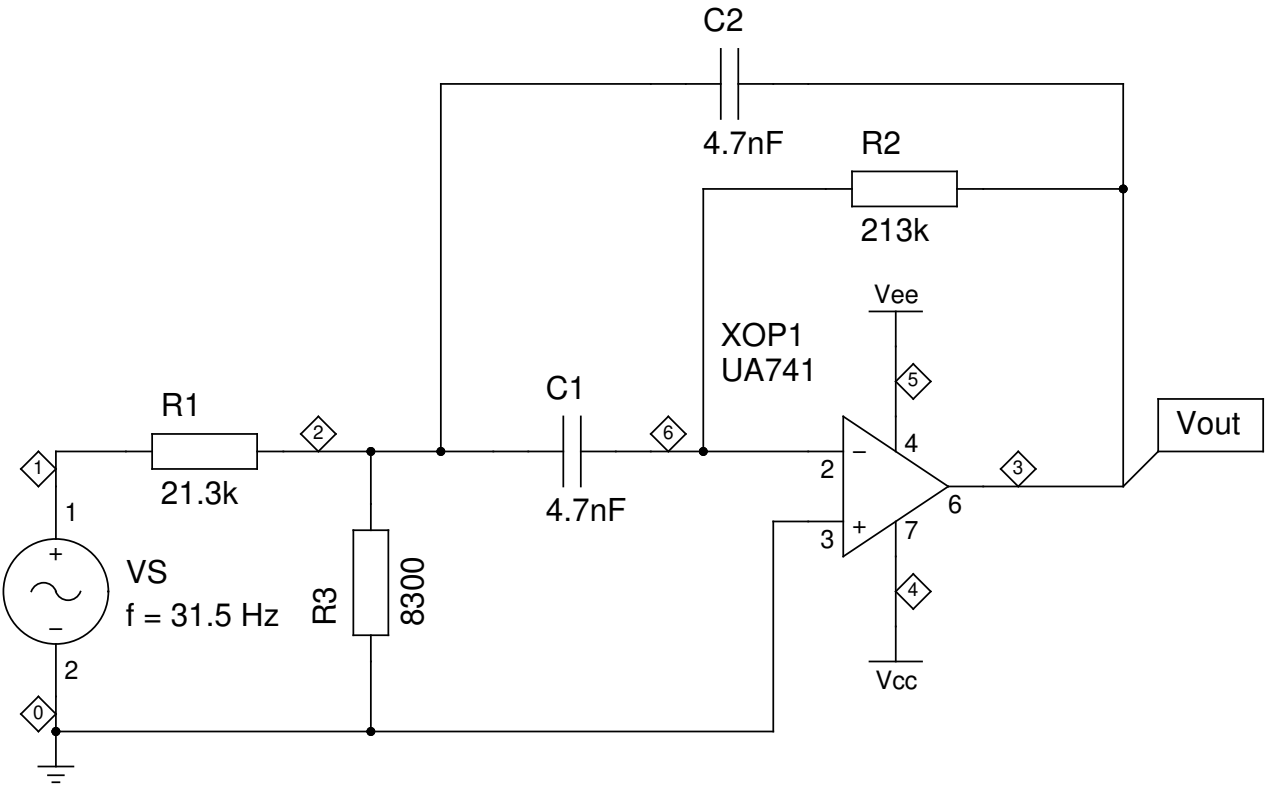

OCTAVE\_FILTER  
1 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.012.00.02.03.sch  
PAGE 01 OF 01

REVISION: 20240529  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 012: 1 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 1k)  
R1 1 2 21.3k  
R2 3 6 213K  
R3 0 2 8300  
C1 2 6 4.7nF  
C2 3 2 4.7nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

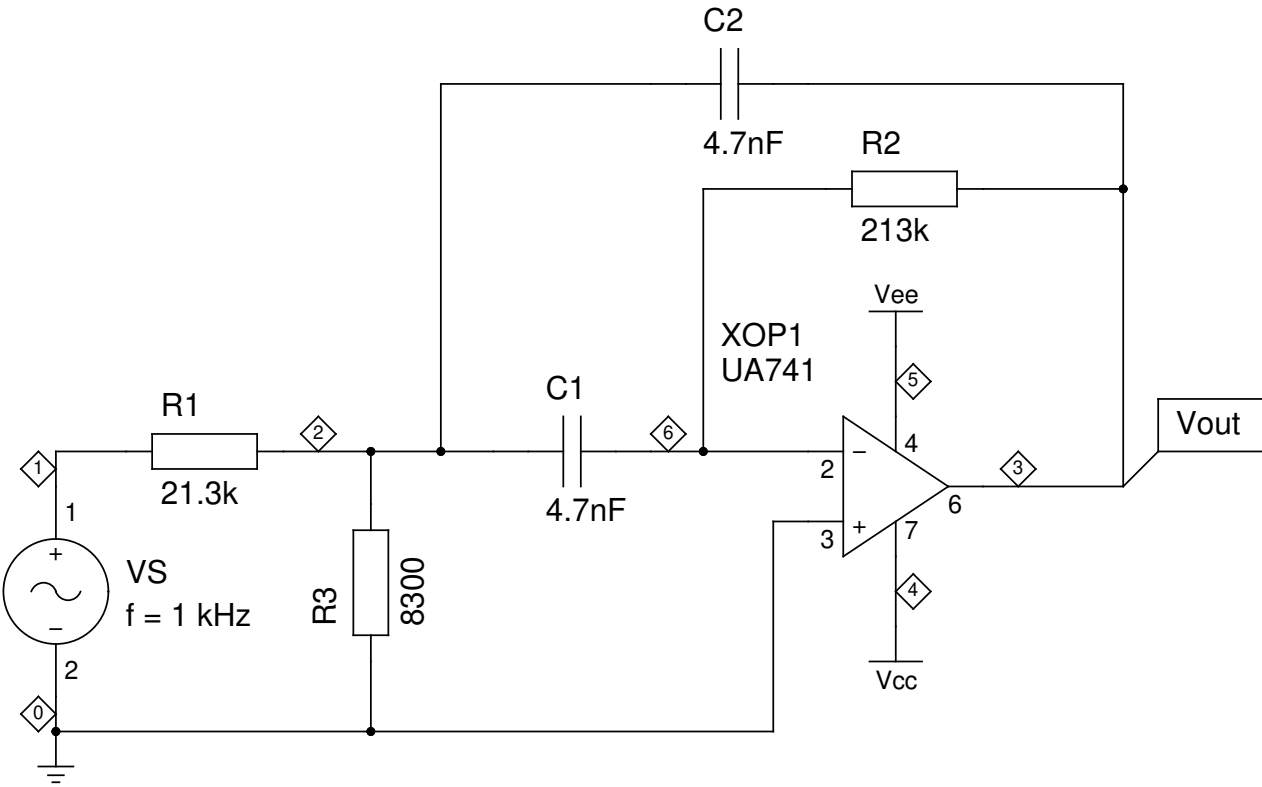

OCTAVE\_FILTER  
1 kHz Band-pass Filter – Transient response (1 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.012.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240529  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 012: 1 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 21.3k  
R2 3 6 213K  
R3 0 2 8300  
C1 2 6 4.7nF  
C2 3 2 4.7nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

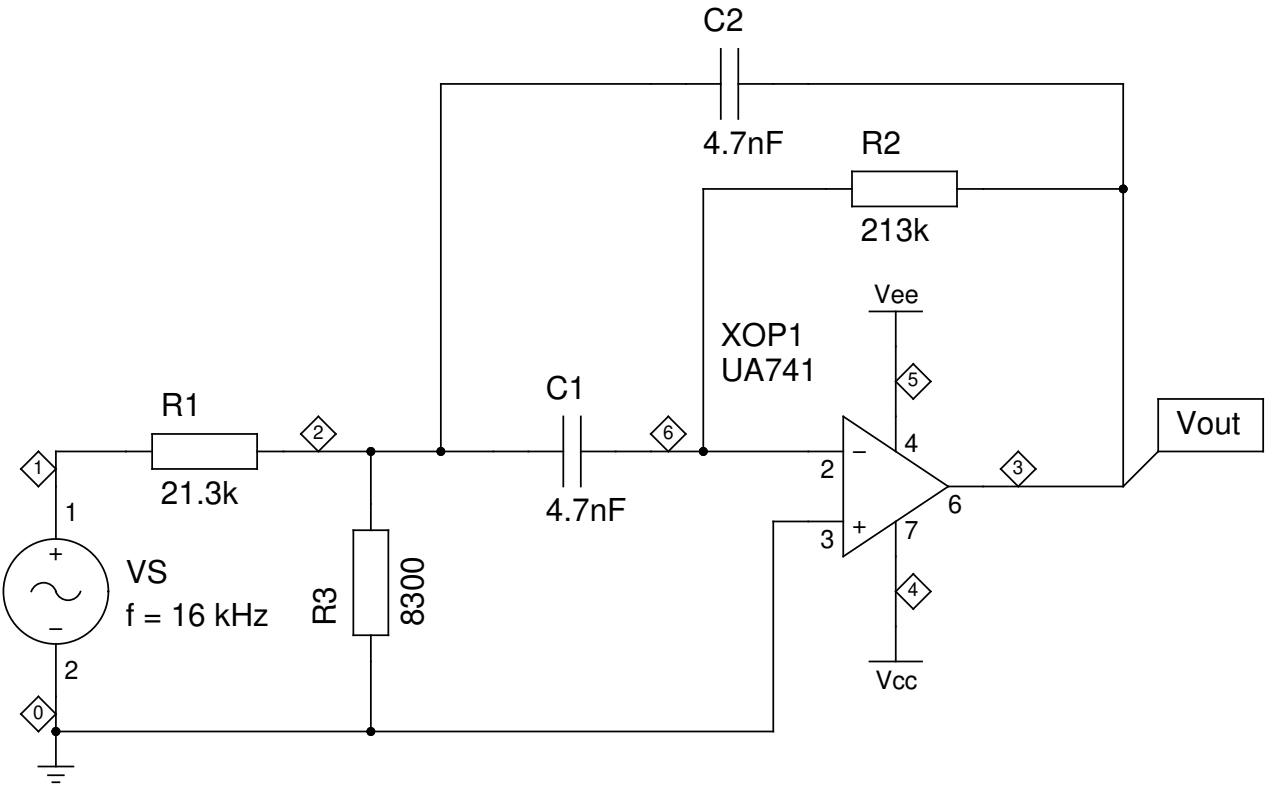

OCTAVE\_FILTER  
1 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.012.00.03.02.sch  
PAGE 01 OF 01

REVISION: 20240529  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 010: 500 HZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 21.3k  
R2 3 6 213K  
R3 0 2 8300  
C1 2 6 4.7nF  
C2 3 2 4.7nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

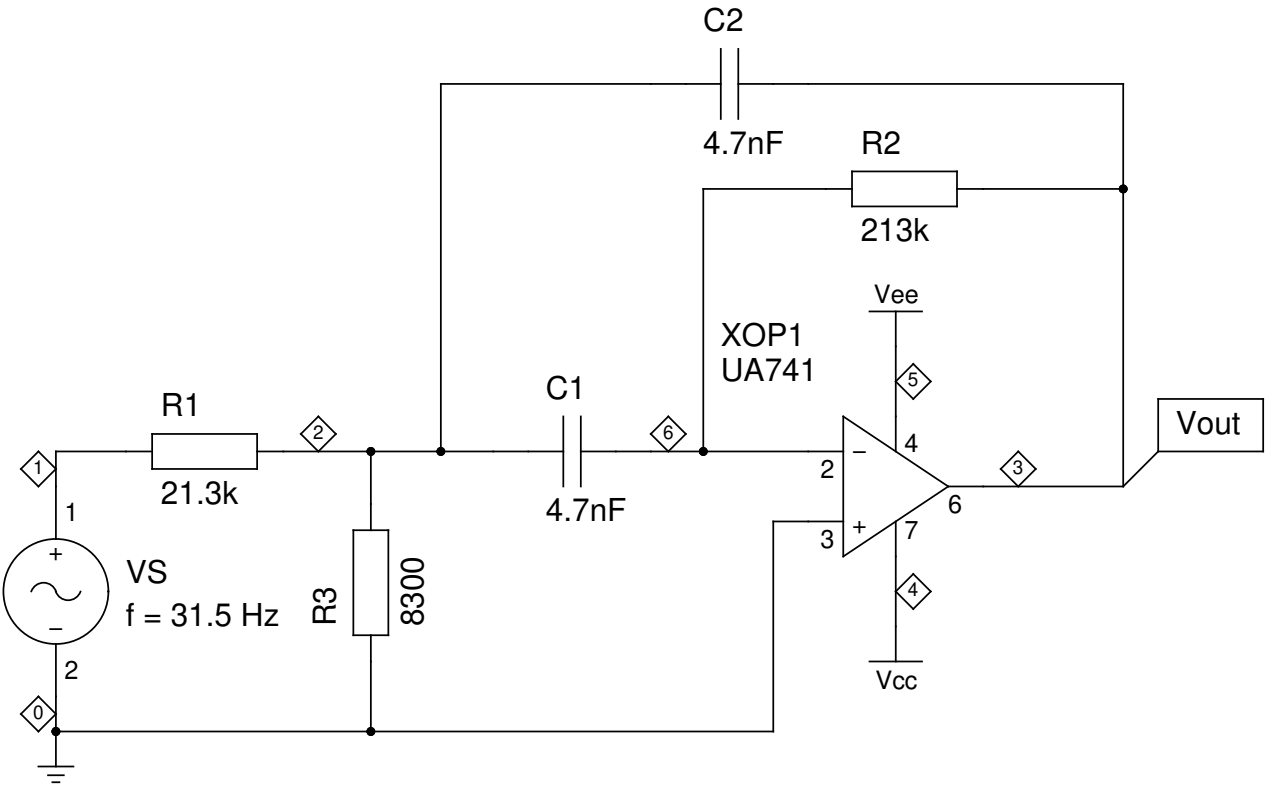

OCTAVE\_FILTER  
1 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.012.00.03.03.sch  
PAGE 01 OF 01

REVISION: 20240529  
DRAWN BY: Bert Timmerman



.TITLE OCTAVE FILTER – FUNCTION 013: 1 KHZ DETECTOR – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 1 1k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741



.PRINT OP Iiter(0) V(3)

.PRINT AC VDB(3) VDB(9)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

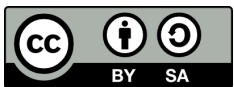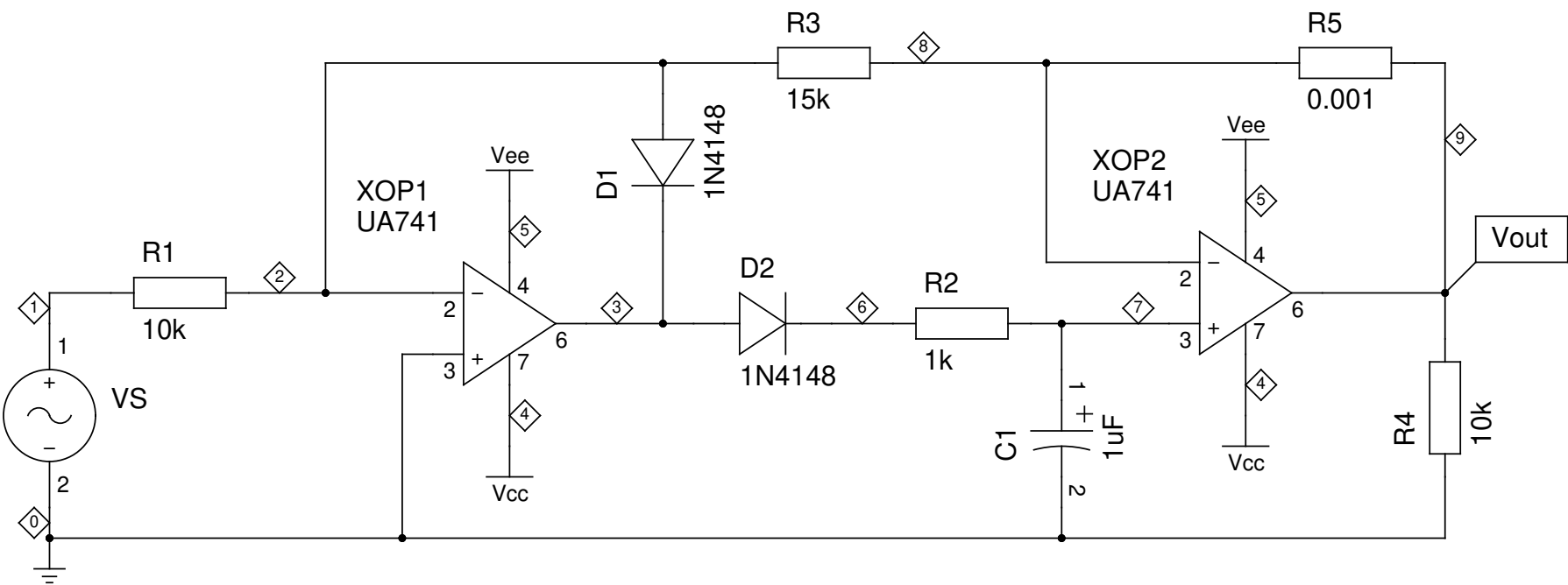

OCTAVE\_FILTER  
1 kHz Detector – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.013.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240529  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 013: 1 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1 1k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(9) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

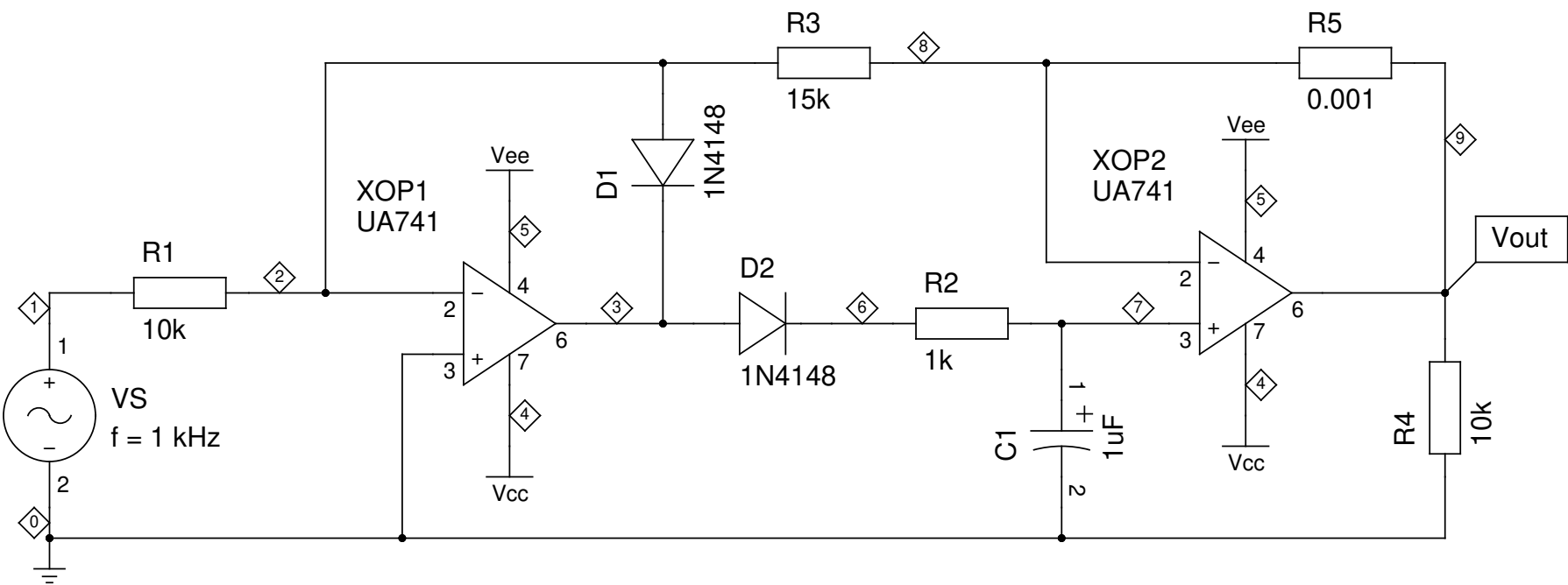

OCTAVE\_FILTER  
1 kHz Detector – Transient response (1 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.013.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240529  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 013: 1 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)



VS 1 0 AC 1 SIN(0 1.41 1k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3) I(R4) I(R5) I(D1) I(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

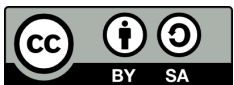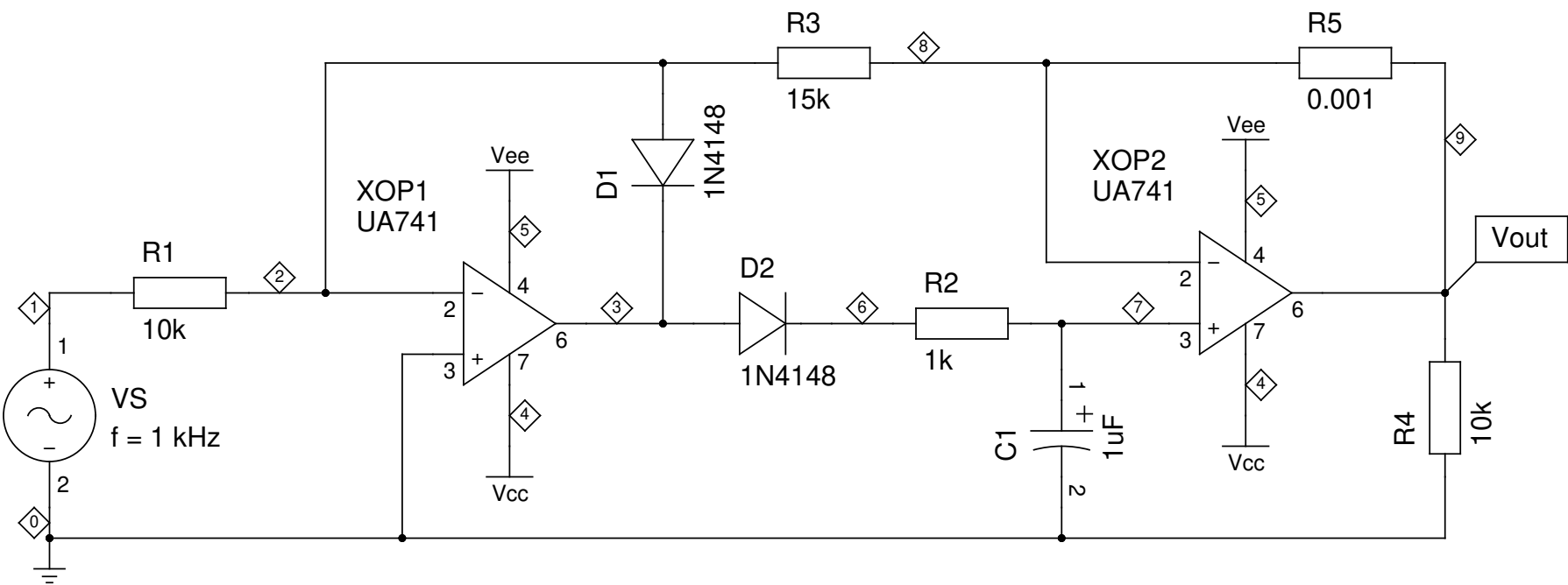

OCTAVE\_FILTER  
1 kHz Detector – Transient response (1 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.013.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240529  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 013: 1 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 1k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iiter(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3) P(R4) P(R5) P(D1) P(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

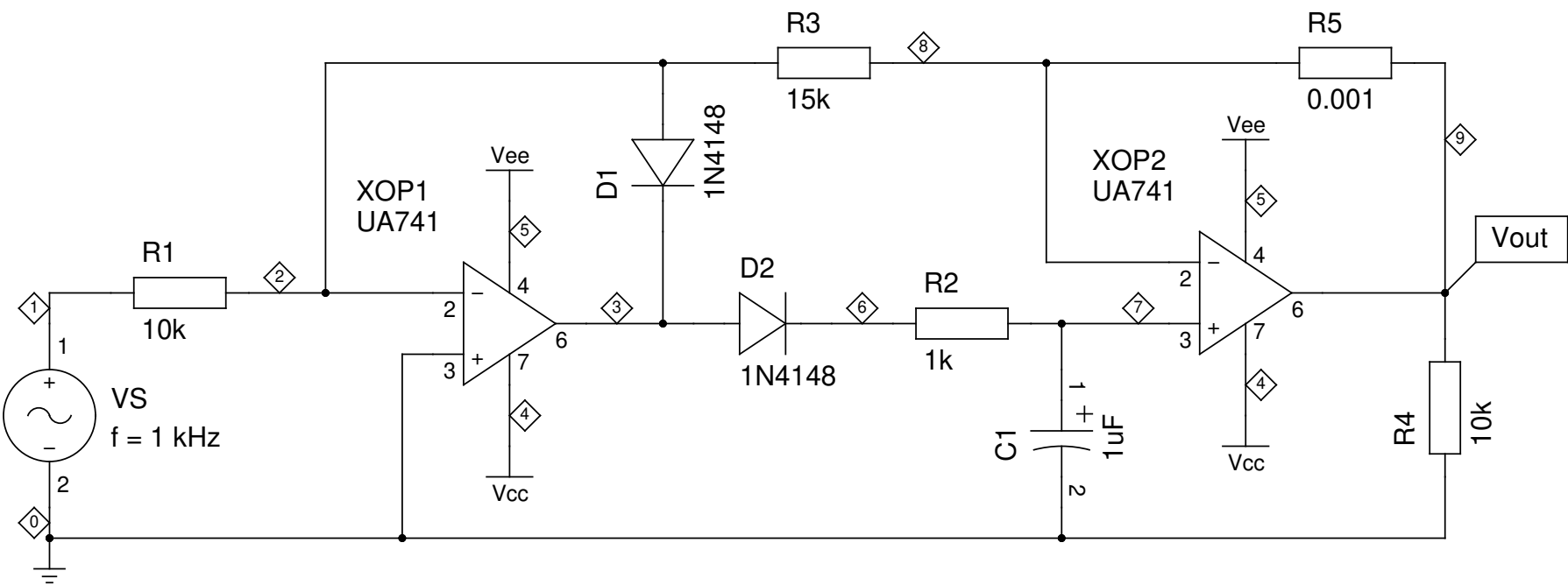

OCTAVE\_FILTER  
1 kHz Detector – Transient response (1 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.013.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240529  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 014: 2 kHz BAND-PASS FILTER – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 1.41 2k)  
R1 1 2 22.7k  
R2 3 6 227K  
R3 0 2 8900  
C1 2 6 2.2nF  
C2 3 2 2.2nF  
XOP1 0 6 0 4 5 3 UA741


.PRINT OP Iter(0) V(3)

.PRINT AC VDB(3)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

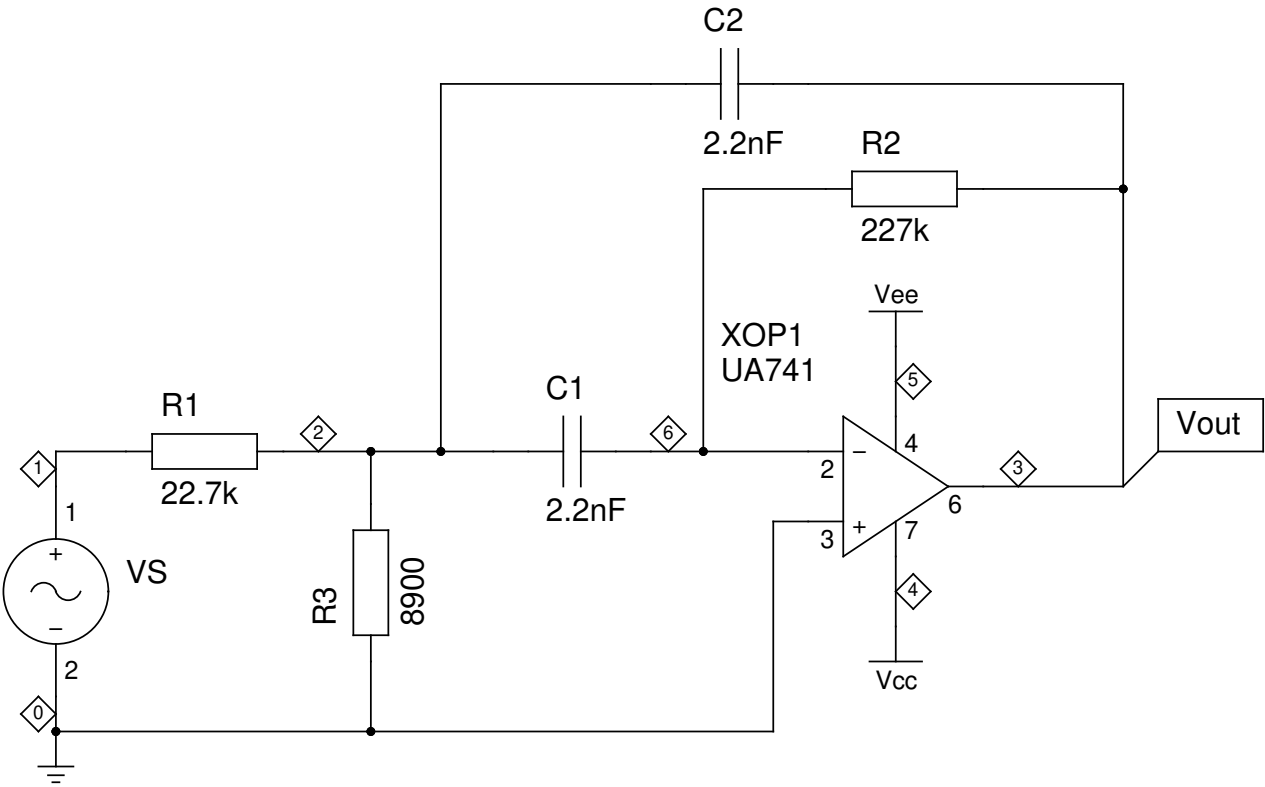

OCTAVE\_FILTER  
2 kHz Band-pass Filter – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.014.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240530  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 014: 2 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 2k)  
R1 1 2 22.7k  
R2 3 6 227K  
R3 0 2 8900  
C1 2 6 2.2nF  
C2 3 2 2.2nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.05 0.00001 TRACE ALL

.END

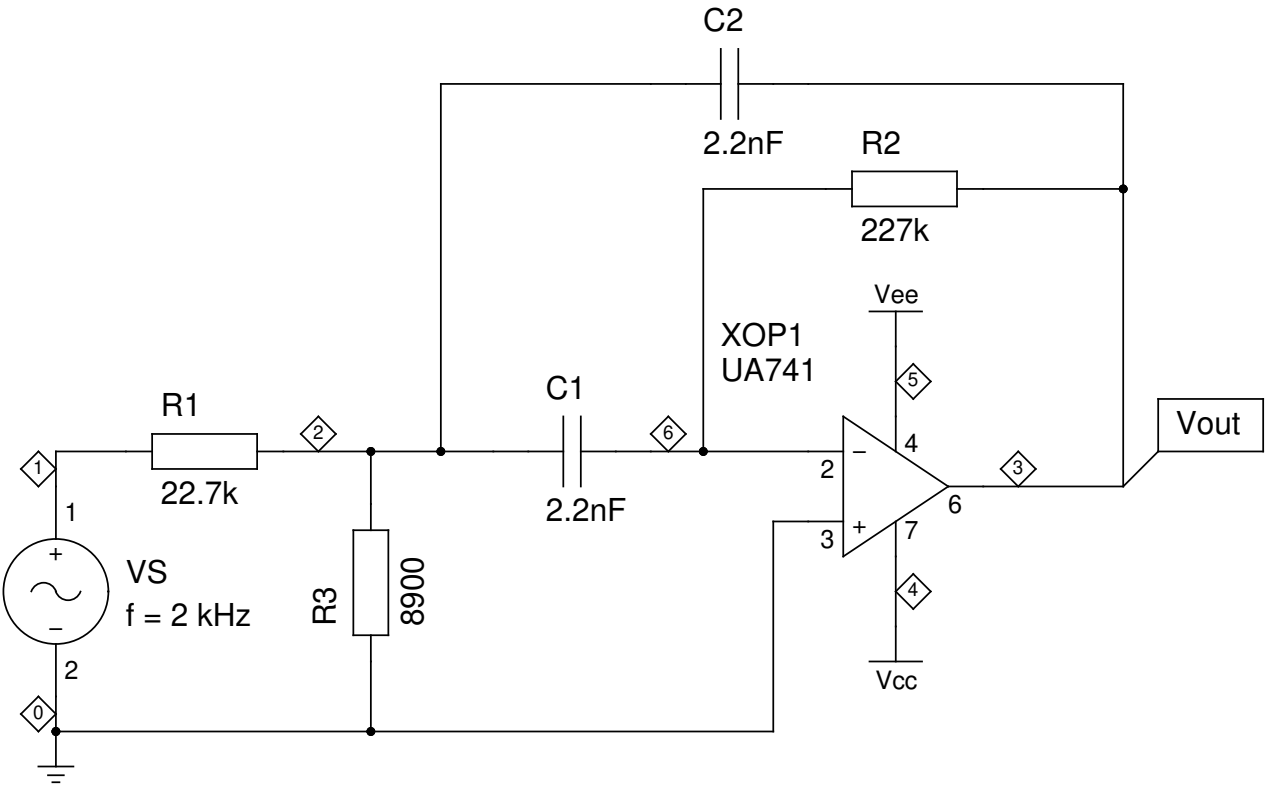

OCTAVE\_FILTER  
2 kHz Band-pass Filter – Transient response (2 kHz)  
TITLE Schematic (DFS)

FILE: gnucap/26.014.00.01.01.sch

PAGE 01 OF 01

REVISION: 20240530

DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 014: 2 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 22.7k  
R2 3 6 227K  
R3 0 2 8900  
C1 2 6 2.2nF  
C2 3 2 2.2nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

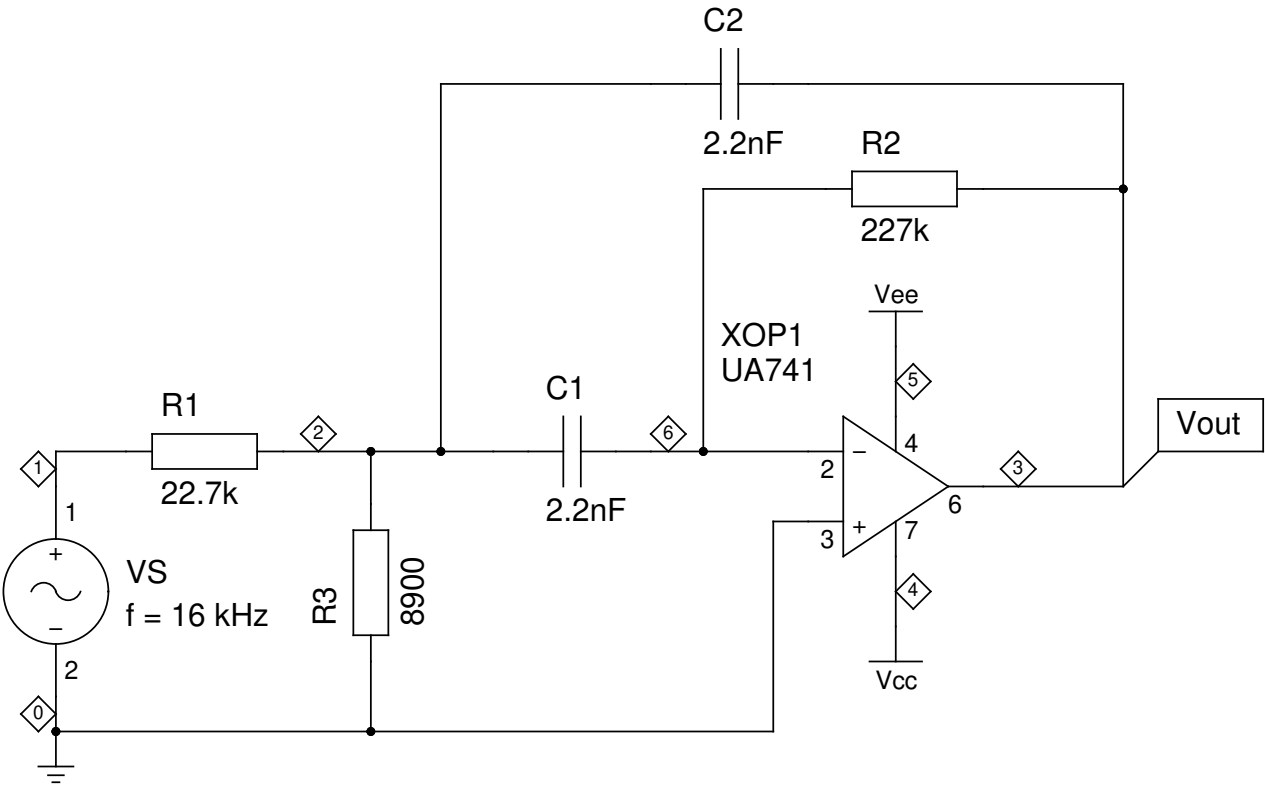

OCTAVE\_FILTER  
2 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.014.00.01.02.sch  
PAGE 01 OF 01

REVISION: 20240531  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 014: 2 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 22.7k  
R2 3 6 227K  
R3 0 2 8900  
C1 2 6 2.2nF  
C2 3 2 2.2nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

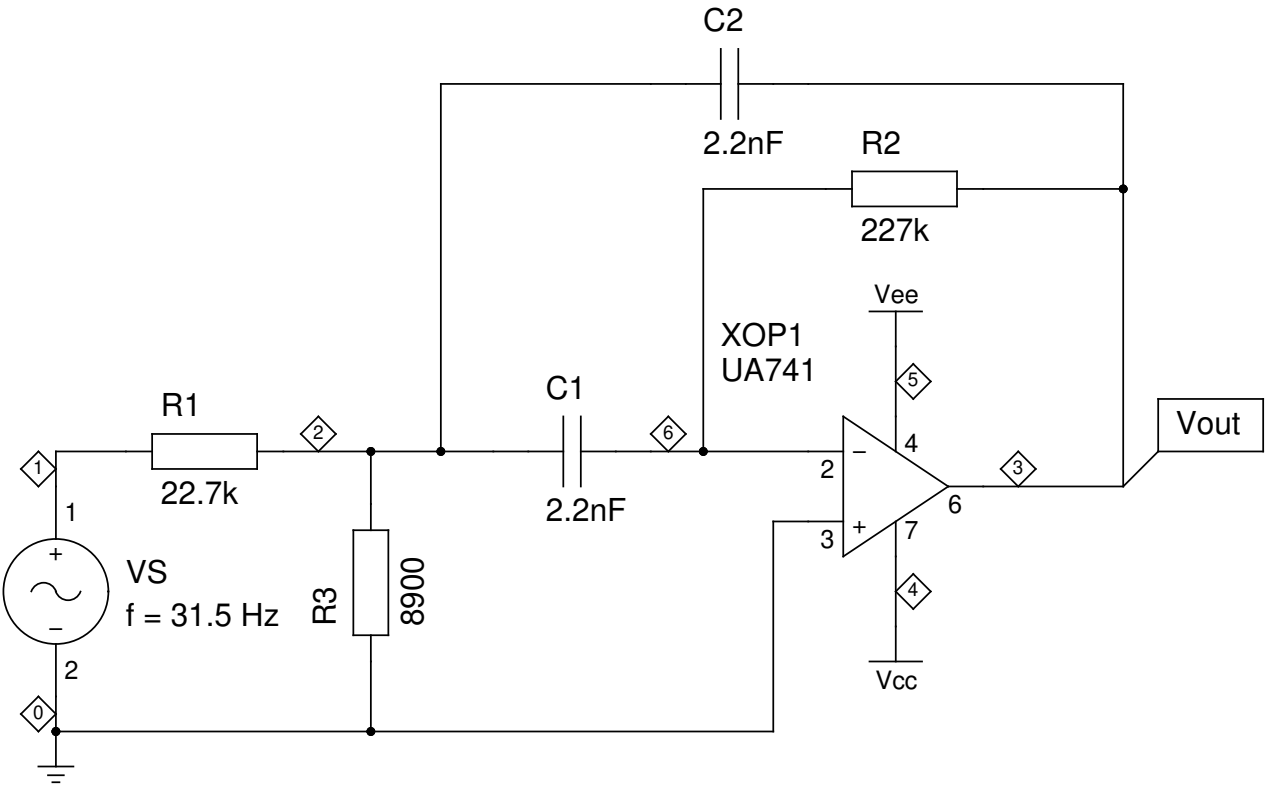

OCTAVE\_FILTER  
2 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.014.00.01.03.sch  
PAGE 01 OF 01

REVISION: 20240531  
DRAWN BY: Bert Timmerman



.TITLE OCTAVE FILTER – FUNCTION 014: 2 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 2k)  
R1 1 2 22.7k  
R2 3 6 227K  
R3 0 2 8900  
C1 2 6 2.2nF  
C2 3 2 2.2nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

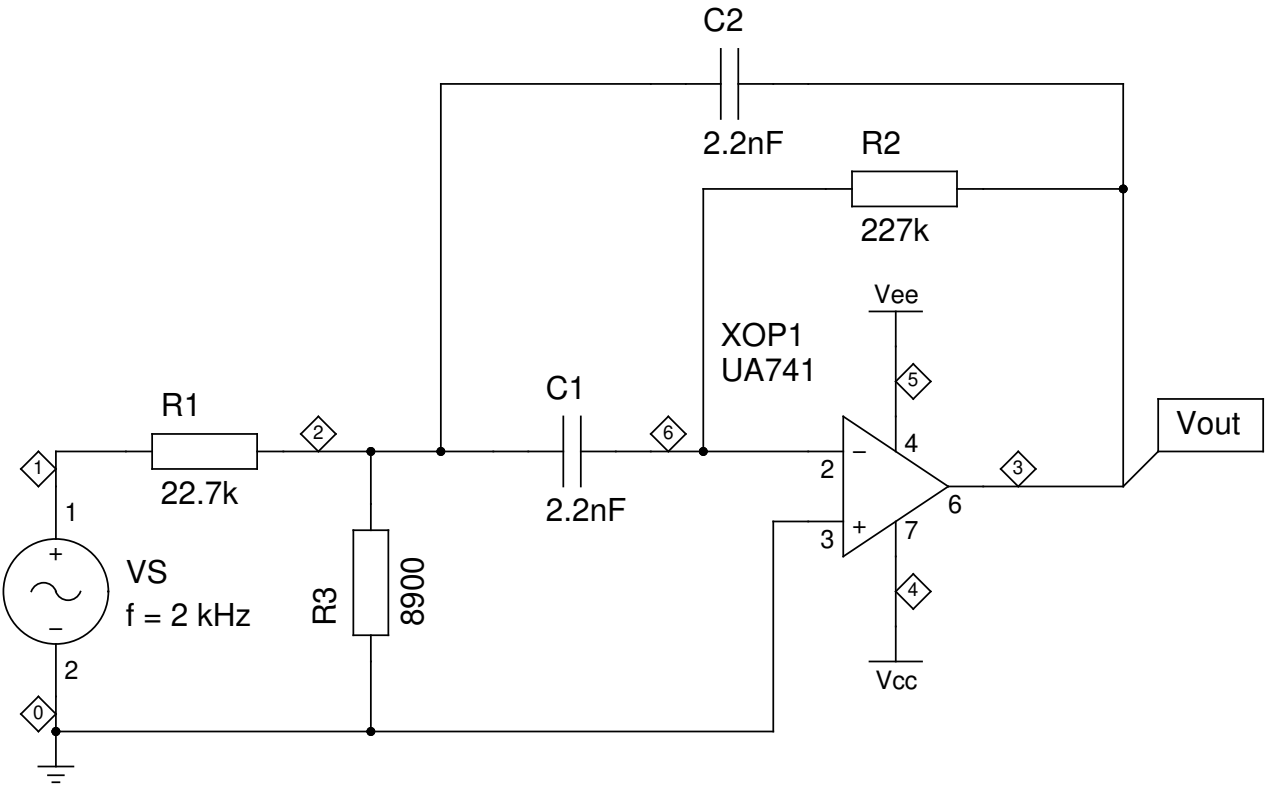

OCTAVE\_FILTER  
2 kHz Band-pass Filter – Transient response (2 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.014.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240531  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 014: 2 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 22.7k  
R2 3 6 227K  
R3 0 2 8900  
C1 2 6 2.2nF  
C2 3 2 2.2nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

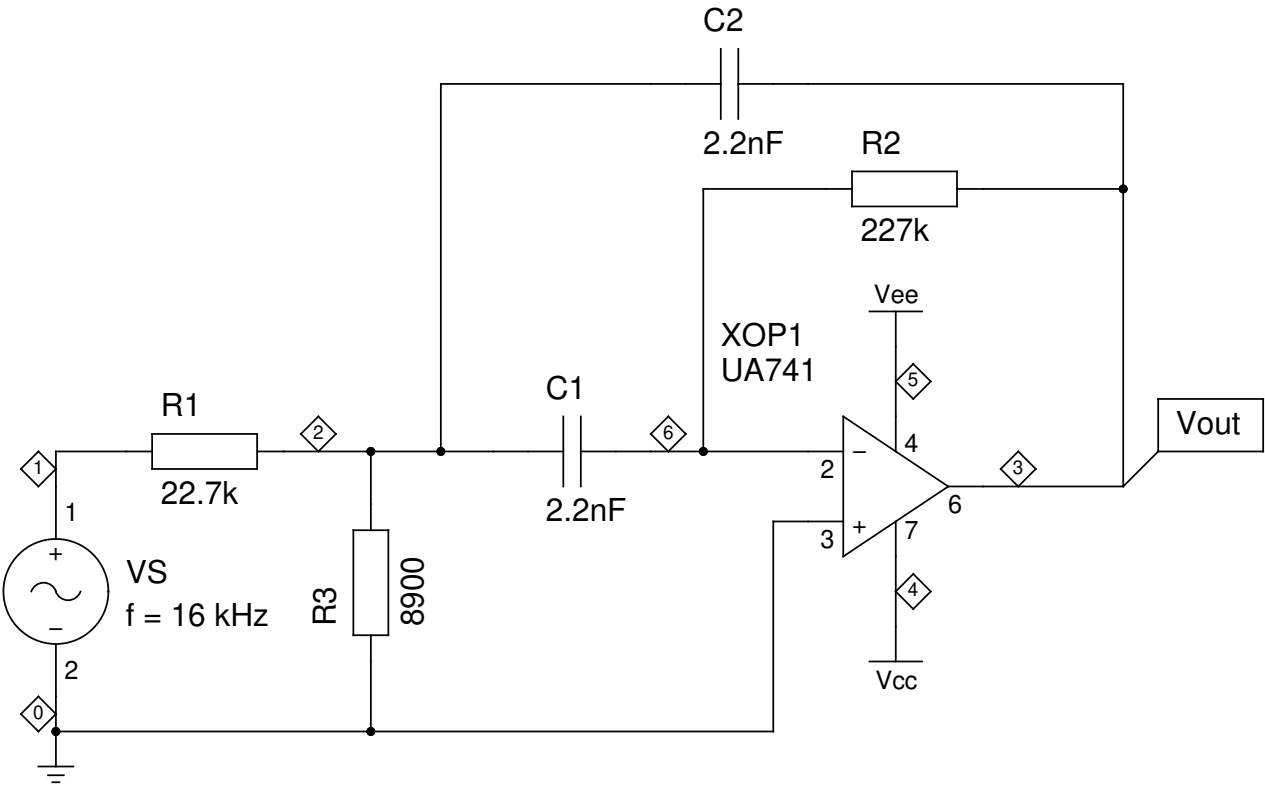

OCTAVE\_FILTER  
2 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.014.00.02.02.sch  
PAGE 01 OF 01

REVISION: 20240531  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 014: 2 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 22.7k  
R2 3 6 227K  
R3 0 2 8900  
C1 2 6 2.2nF  
C2 3 2 2.2nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

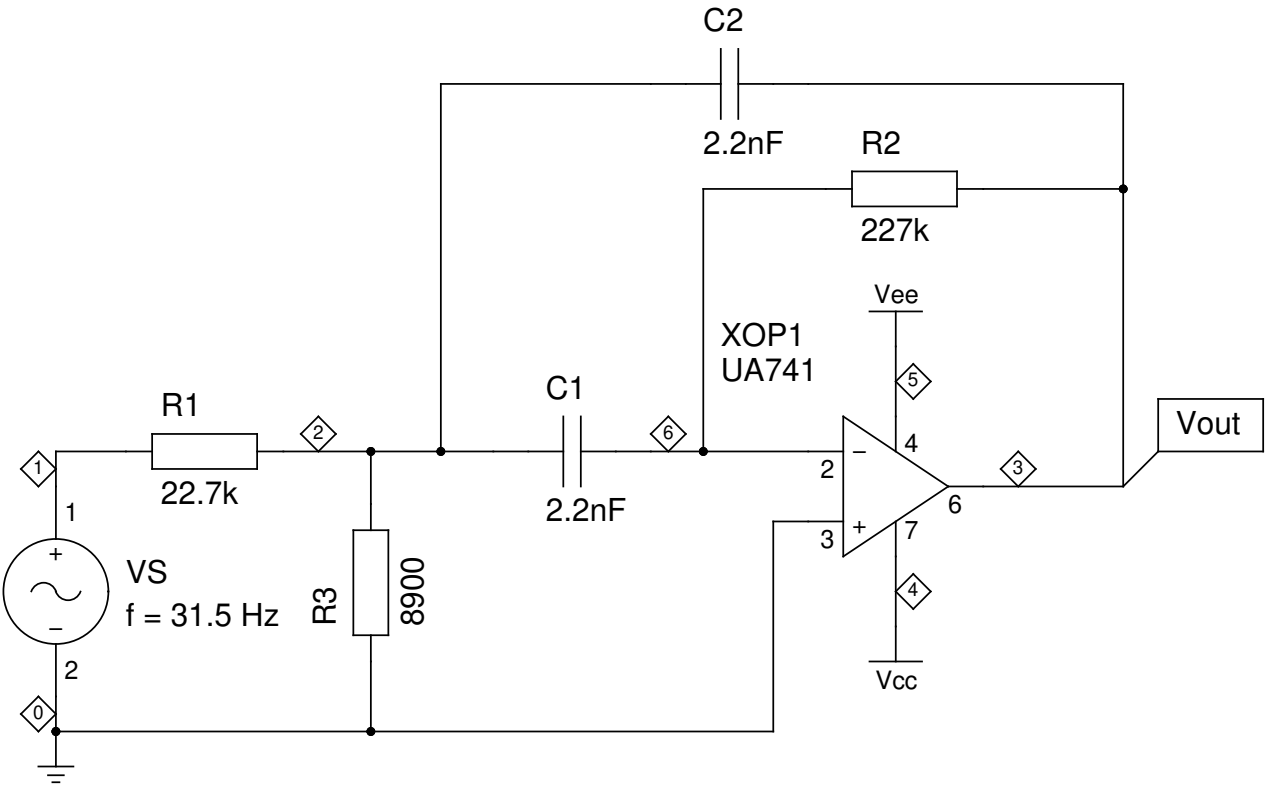

OCTAVE\_FILTER  
2 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.014.00.02.03.sch  
PAGE 01 OF 01

REVISION: 20240531  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 014: 2 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 2k)  
R1 1 2 22.7k  
R2 3 6 227K  
R3 0 2 8900  
C1 2 6 2.2nF  
C2 3 2 2.2nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

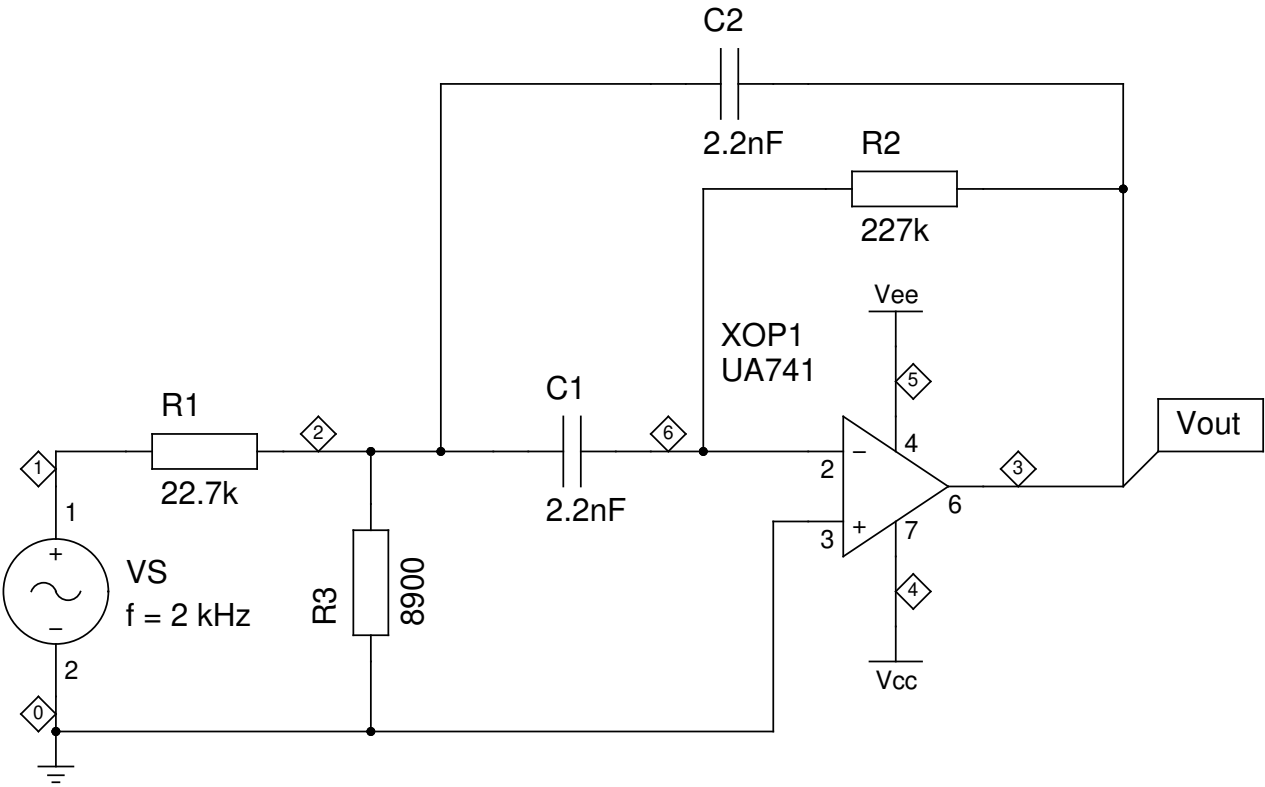

OCTAVE\_FILTER  
2 kHz Band-pass Filter – Transient response (2 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.014.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240601  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 014: 2 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 22.7k  
R2 3 6 227K  
R3 0 2 8900  
C1 2 6 2.2nF  
C2 3 2 2.2nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

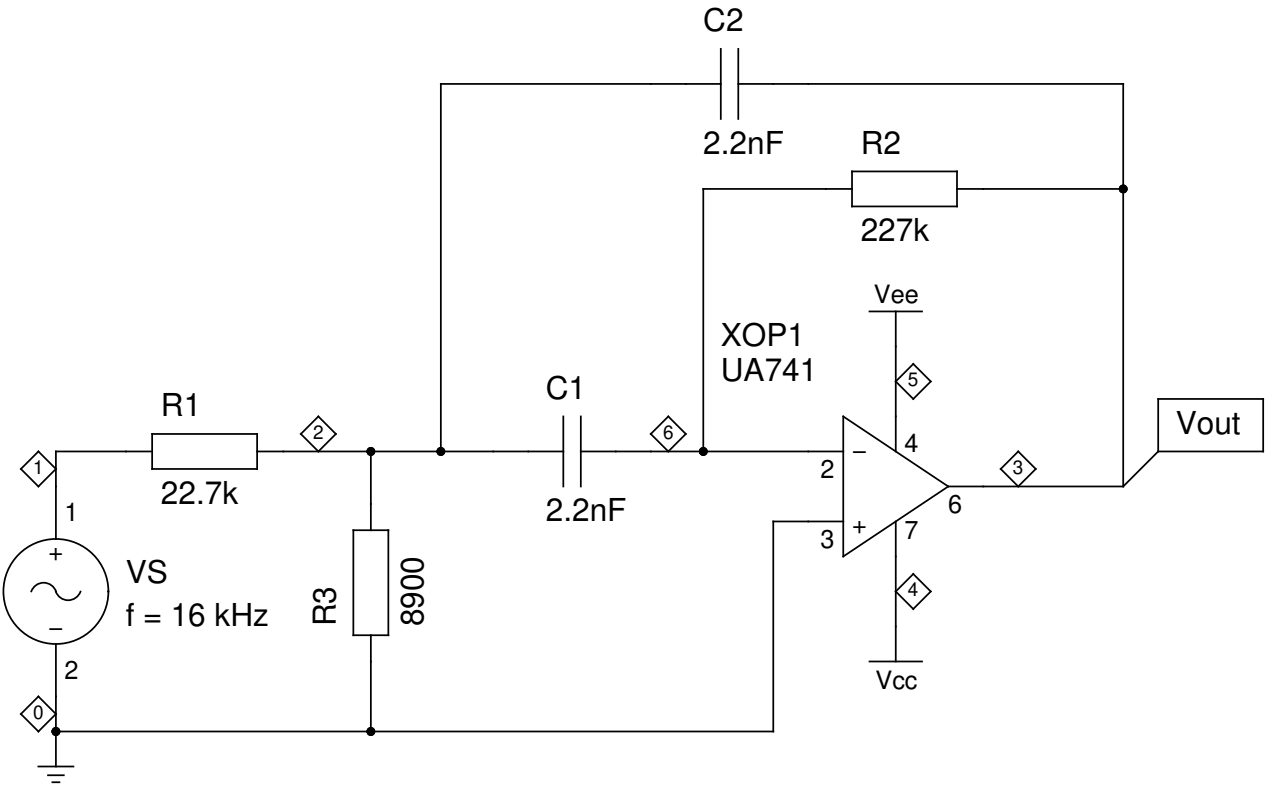

OCTAVE\_FILTER  
2 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.014.00.03.02.sch  
PAGE 01 OF 01

REVISION: 20240601  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 014: 2 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 22.7k  
R2 3 6 227K  
R3 0 2 8900  
C1 2 6 2.2nF  
C2 3 2 2.2nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

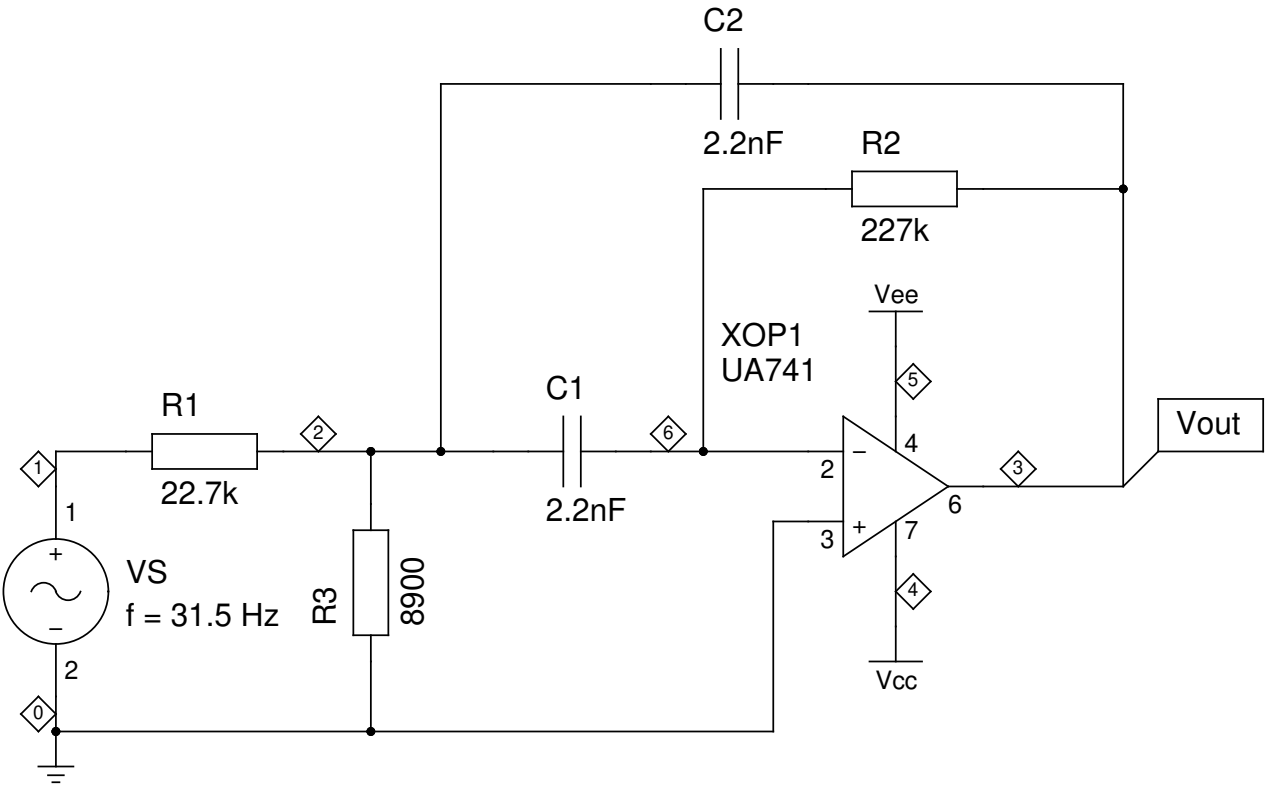

OCTAVE\_FILTER  
2 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.014.00.03.03.sch  
PAGE 01 OF 01

REVISION: 20240604  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 015: 2 KHZ DETECTOR – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 1 2k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741


.PRINT OP Iiter(0) V(3)

.PRINT AC VDB(3) VDB(9)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

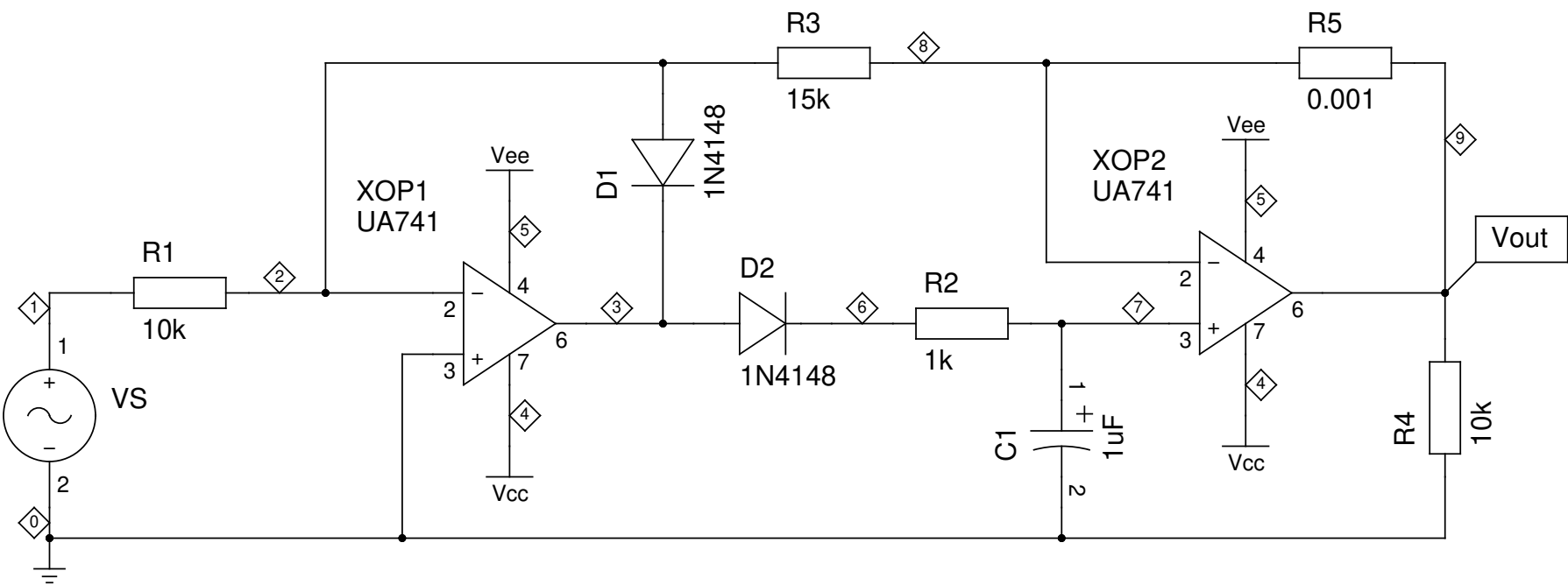

OCTAVE\_FILTER  
2 kHz Detector – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.015.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240604  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 015: 2 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)



VS 1 0 AC 1 SIN(0 1 2k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(9) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

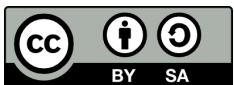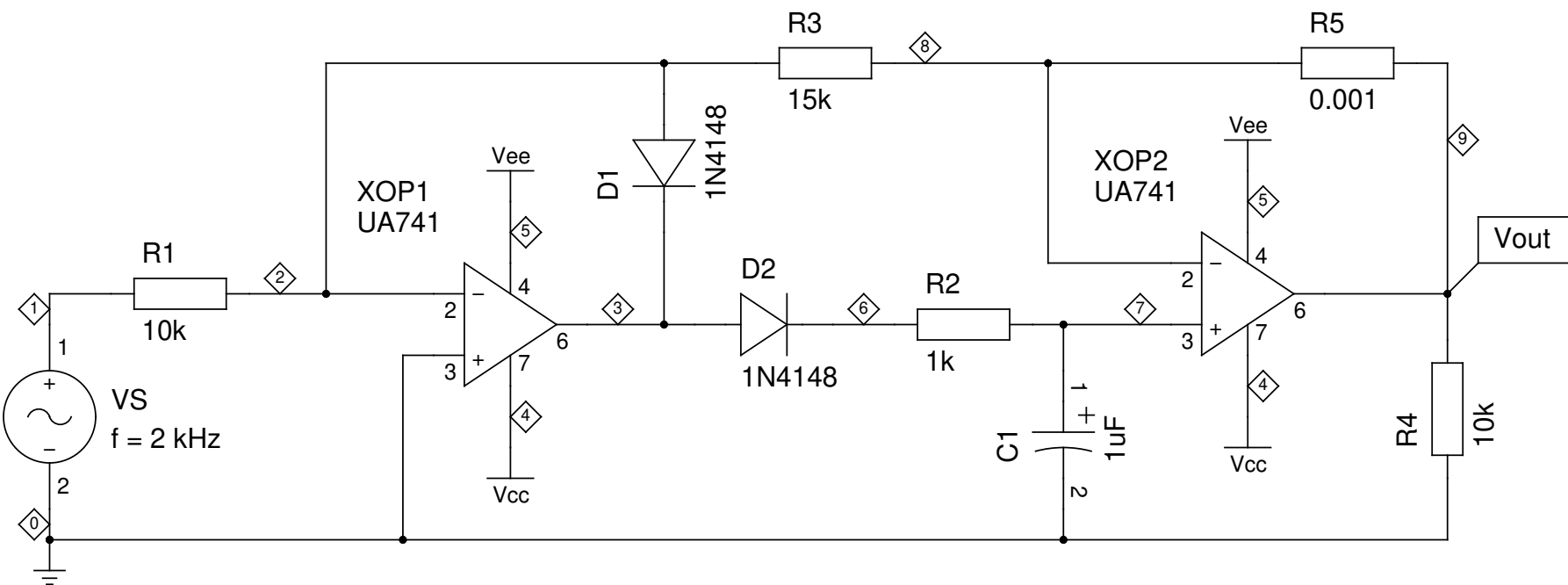

OCTAVE\_FILTER  
2 kHz Detector – Transient response (2 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.015.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240604  
DRAWN BY: Bert Timmerman

A3



.TITLE OCTAVE FILTER – FUNCTION 015: 2 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 2k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3) I(R4) I(R5) I(D1) I(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

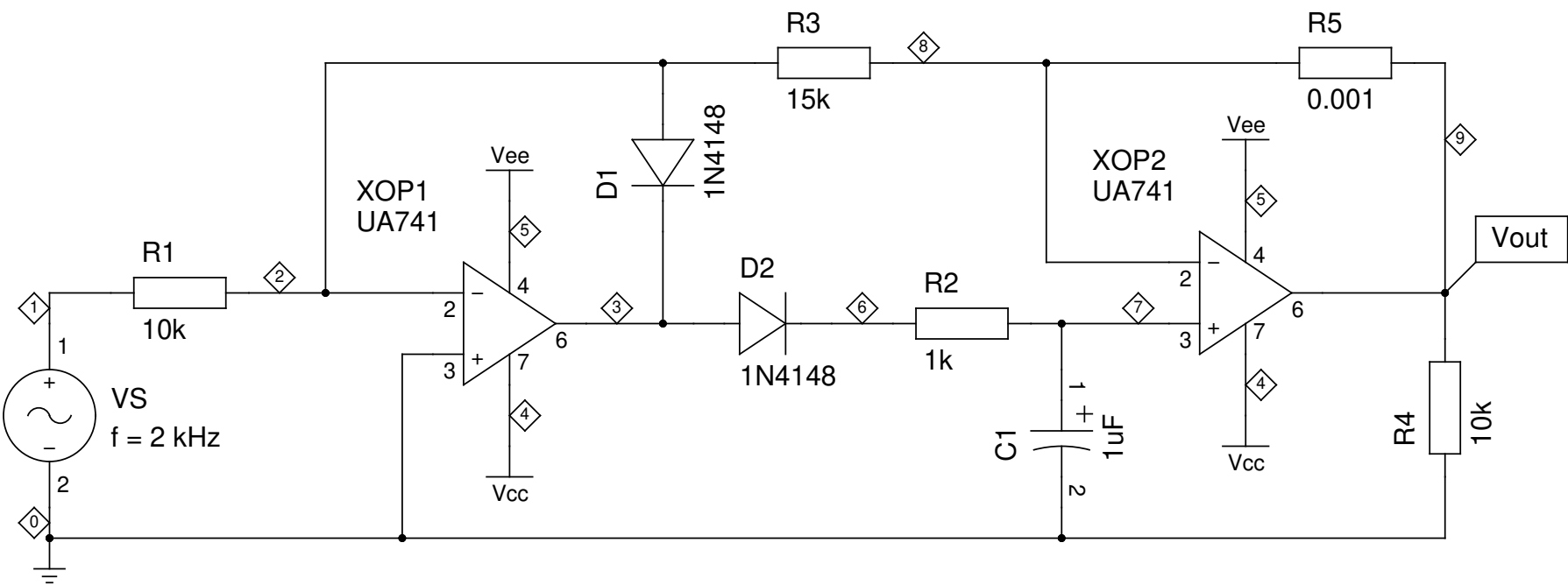

OCTAVE\_FILTER  
2 kHz Detector – Transient response (2 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.015.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240604  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 016: 4 kHz BAND-PASS FILTER – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 1.41 4k)  
R1 1 2 25k  
R2 3 6 250K  
R3 0 2 13300  
C1 2 6 1nF  
C2 3 2 1nF  
XOP1 0 6 0 4 5 3 UA741


.PRINT OP Iiter(0) V(3)

.PRINT AC VDB(3)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

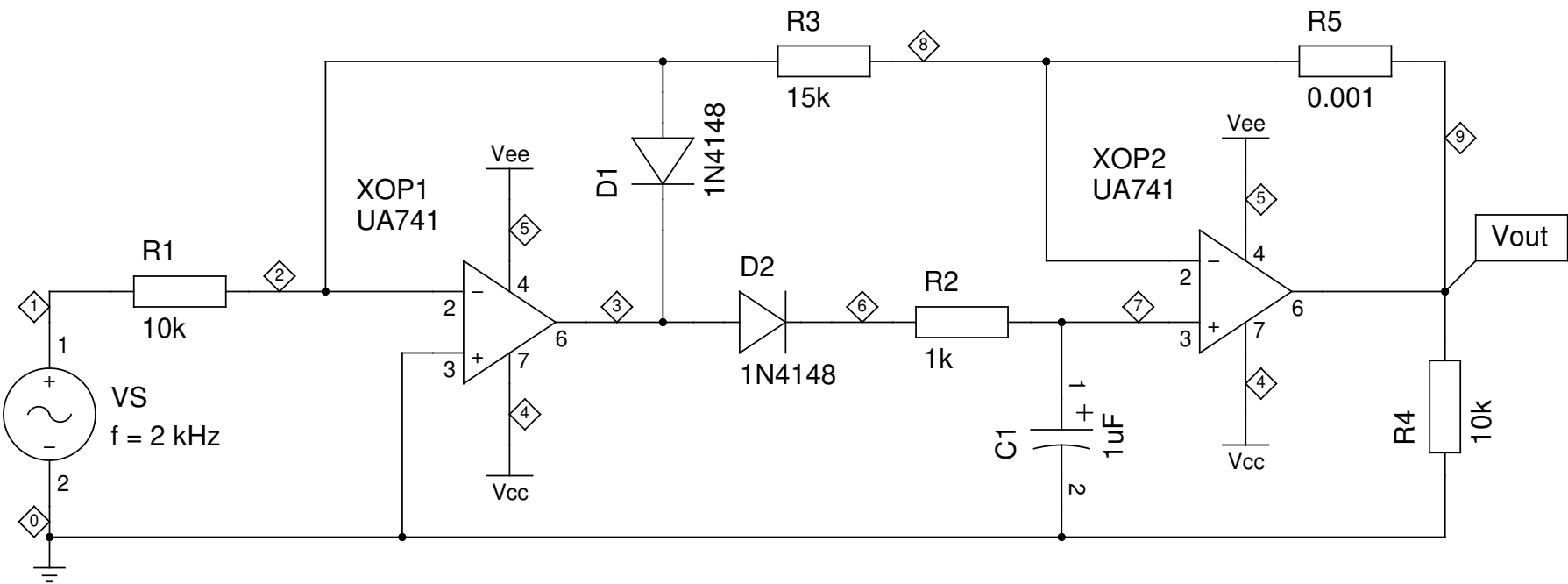

OCTAVE\_FILTER  
2 kHz Detector – Transient response (2 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.015.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240605  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 016: 4 kHz BAND-PASS FILTER – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 1.41 4k)  
R1 1 2 25k  
R2 3 6 250K  
R3 0 2 13300  
C1 2 6 1nF  
C2 3 2 1nF  
XOP1 0 6 0 4 5 3 UA741


.PRINT OP Iter(0) V(3)

.PRINT AC VDB(3)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

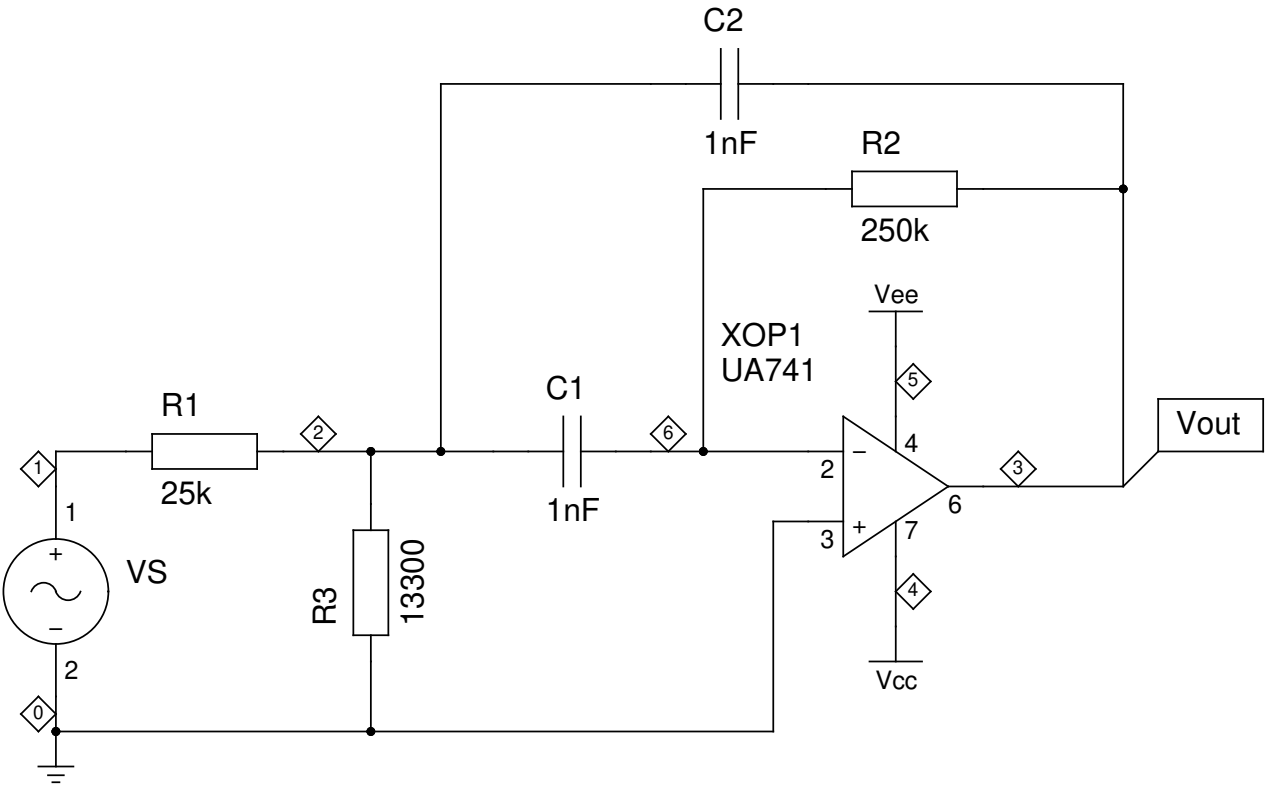

OCTAVE\_FILTER  
4 kHz Band-pass Filter – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.016.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240605  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 016: 4 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 4k)  
R1 1 2 25k  
R2 3 6 250K  
R3 0 2 13300  
C1 2 6 1nF  
C2 3 2 1nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.05 0.00001 TRACE ALL

.END

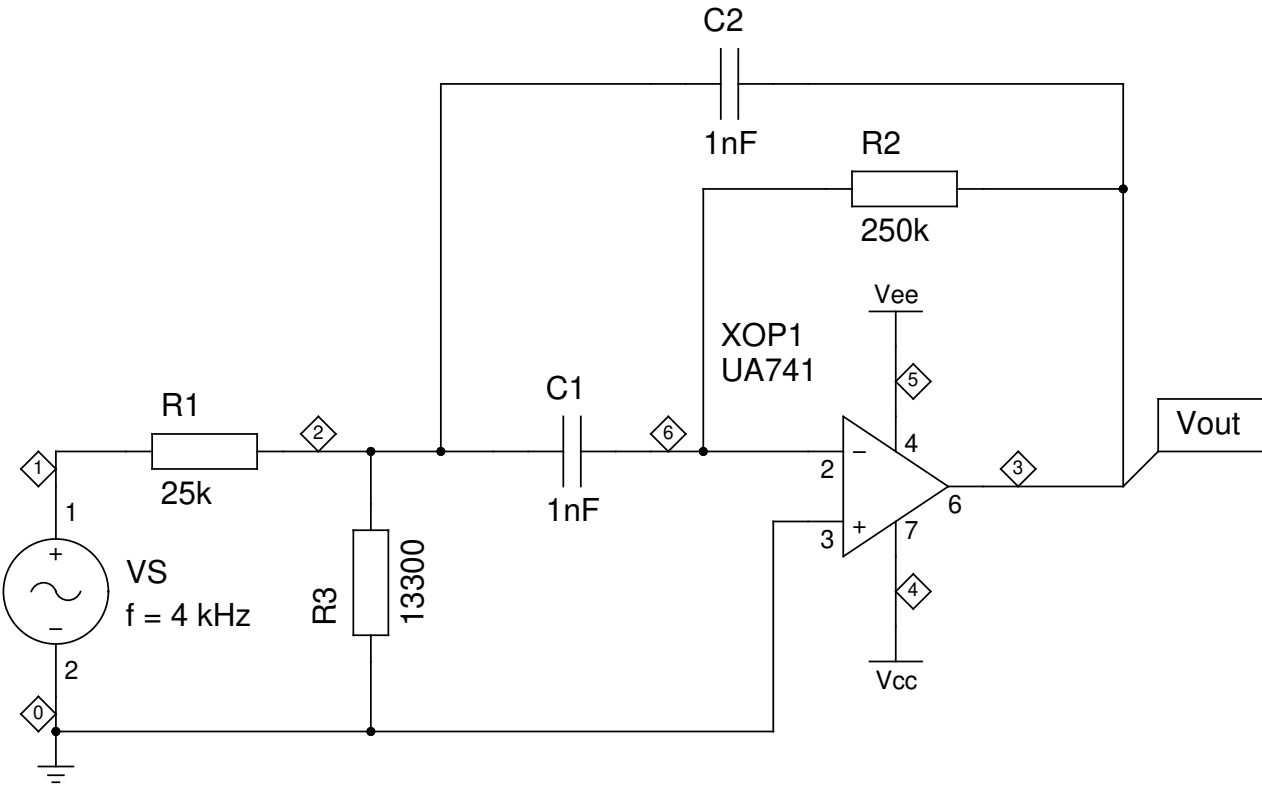

OCTAVE\_FILTER  
4 kHz Band-pass Filter – Transient response (4 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.016.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240605  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 016: 4 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 25k  
R2 3 6 250K  
R3 0 2 13300  
C1 2 6 1nF  
C2 3 2 1nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

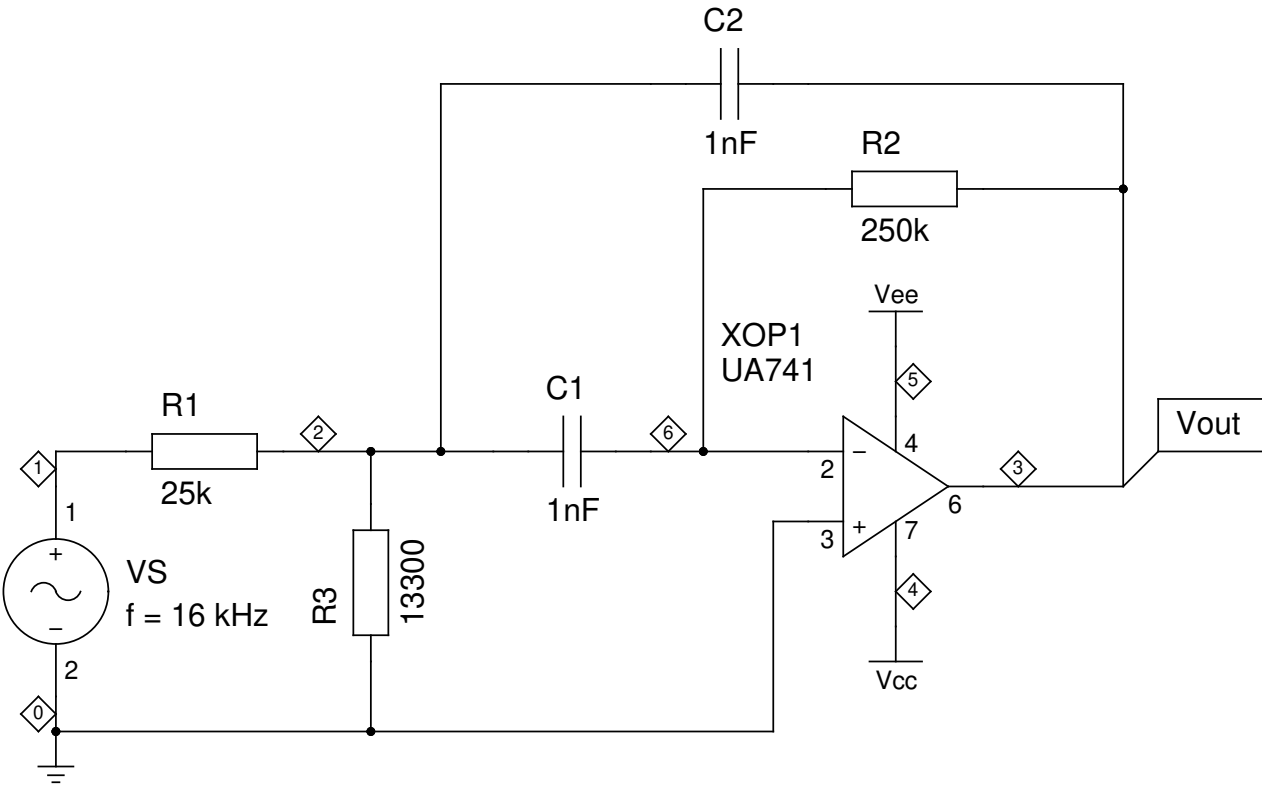

OCTAVE\_FILTER  
4 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.016.00.01.02.sch  
PAGE 01 OF 01

REVISION: 20240605  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 016: 4 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 25k  
R2 3 6 250K  
R3 0 2 13300  
C1 2 6 1nF  
C2 3 2 1nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

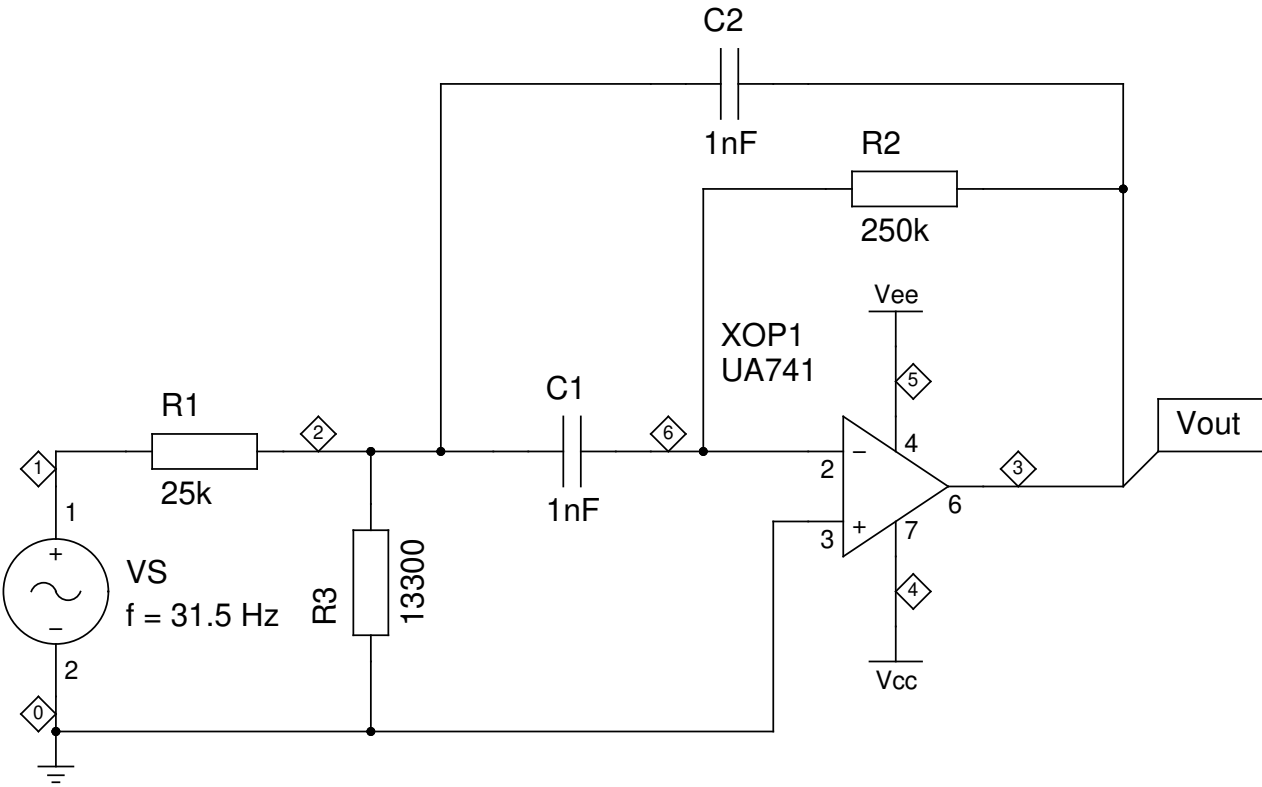

OCTAVE\_FILTER  
4 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.016.00.01.03.sch  
PAGE 01 OF 01

REVISION: 20240605  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 016: 4 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 4k)  
R1 1 2 25k  
R2 3 6 250K  
R3 0 2 13300  
C1 2 6 1nF  
C2 3 2 1nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

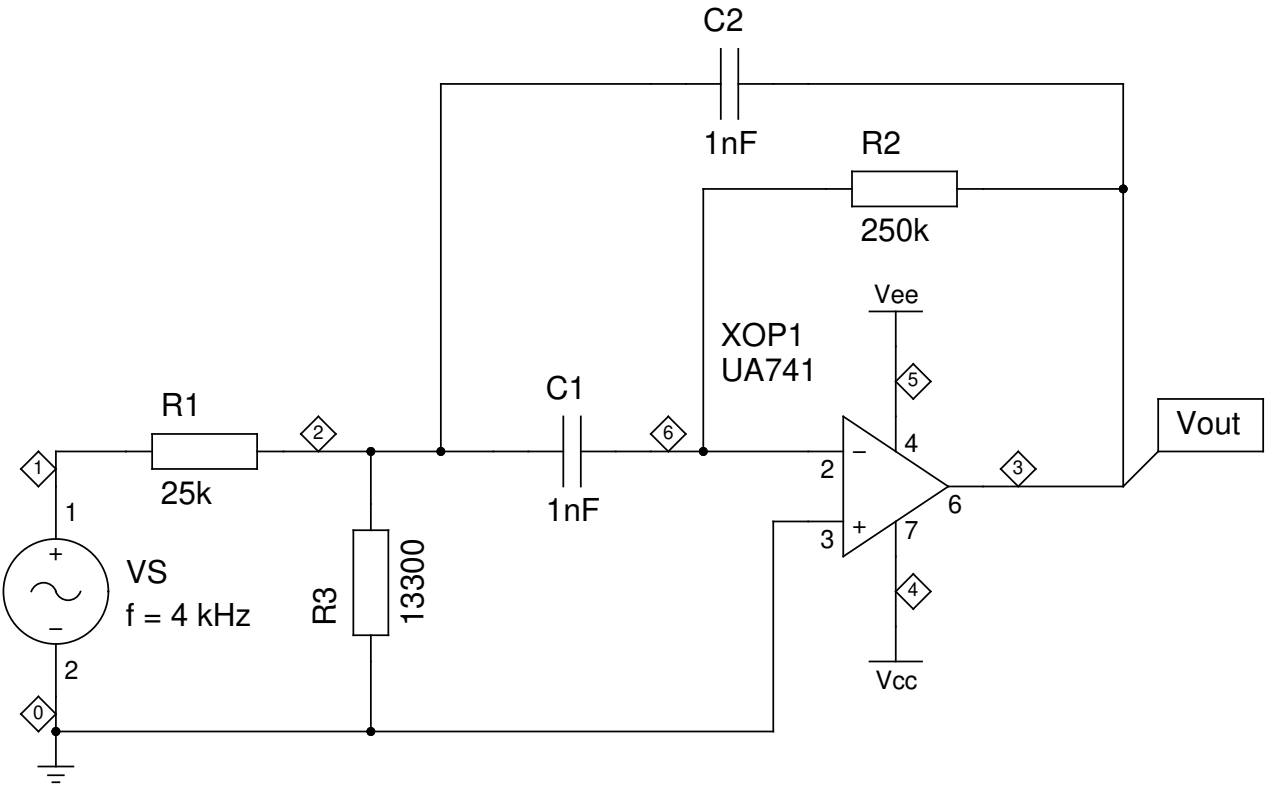

OCTAVE\_FILTER  
4 kHz Band-pass Filter – Transient response (4 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.016.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240605  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 016: 4 KHZ BAND-PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 25k  
R2 3 6 250K  
R3 0 2 13300  
C1 2 6 1nF  
C2 3 2 1nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

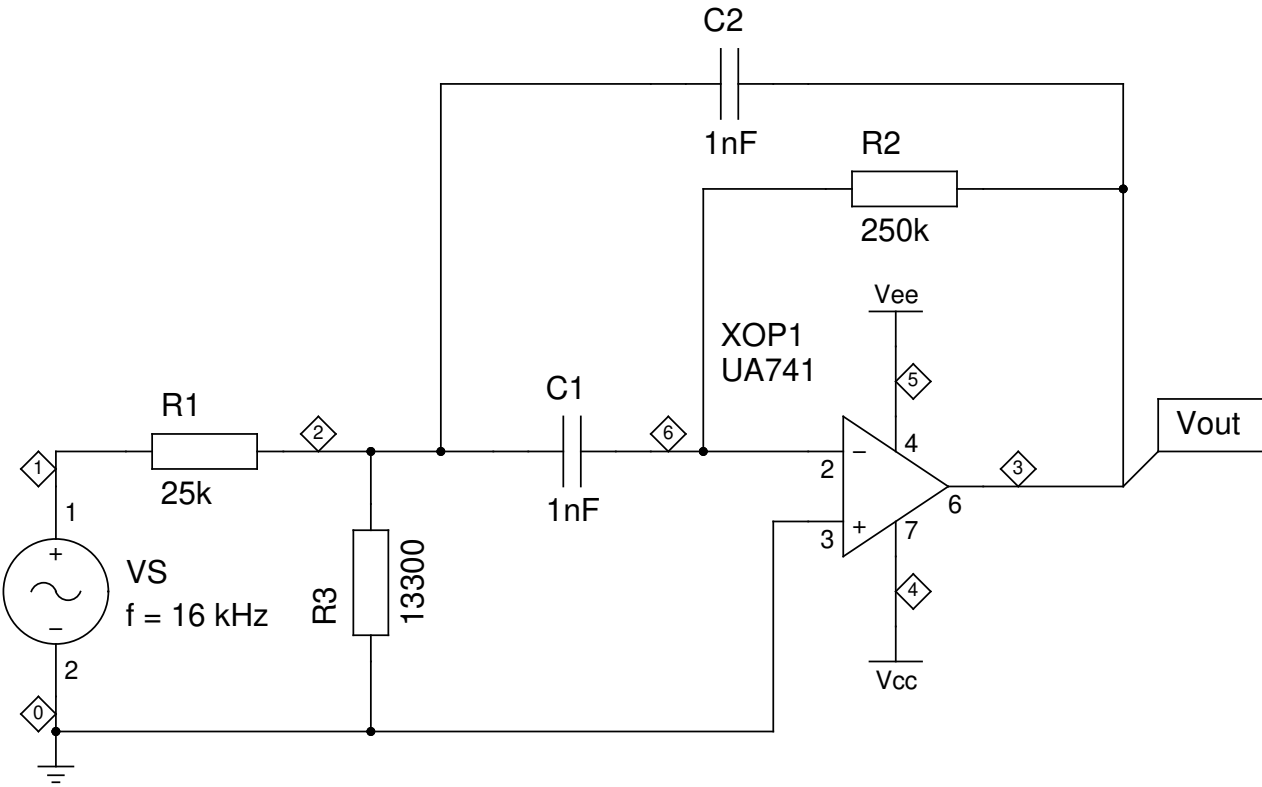

OCTAVE\_FILTER  
4 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.016.00.02.02.sch  
PAGE 01 OF 01

REVISION: 20240605  
DRAWN BY: Bert Timmerman



.TITLE OCTAVE FILTER – FUNCTION 016: 4 KHZ BAND-PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 25k  
R2 3 6 250K  
R3 0 2 13300  
C1 2 6 1nF  
C2 3 2 1nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

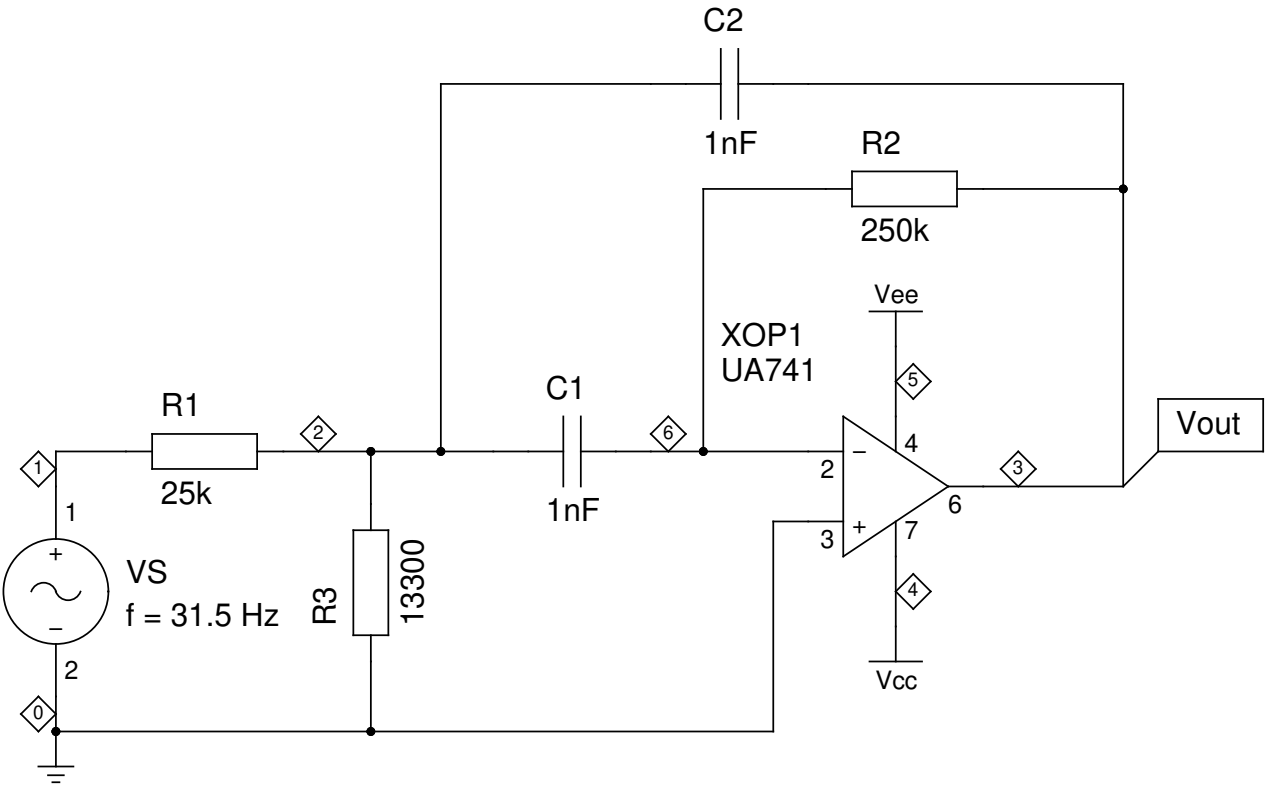

OCTAVE\_FILTER  
4 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.016.00.02.03.sch  
PAGE 01 OF 01

REVISION: 20240605  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 016: 4 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 4k)  
R1 1 2 25k  
R2 3 6 250K  
R3 0 2 13300  
C1 2 6 1nF  
C2 3 2 1nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

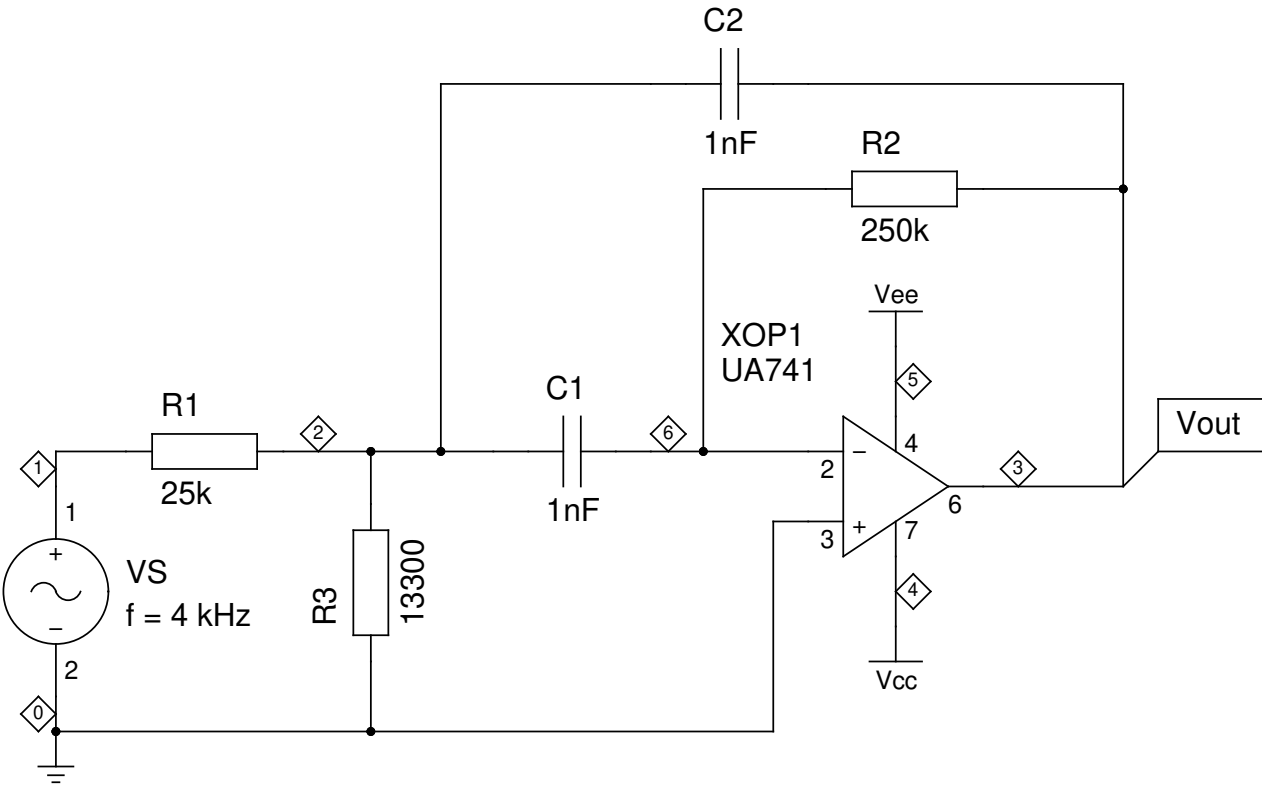

OCTAVE\_FILTER  
4 kHz Band-pass Filter – Transient response (4 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.016.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240607  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 016: 4 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 25k  
R2 3 6 250K  
R3 0 2 13300  
C1 2 6 1nF  
C2 3 2 1nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

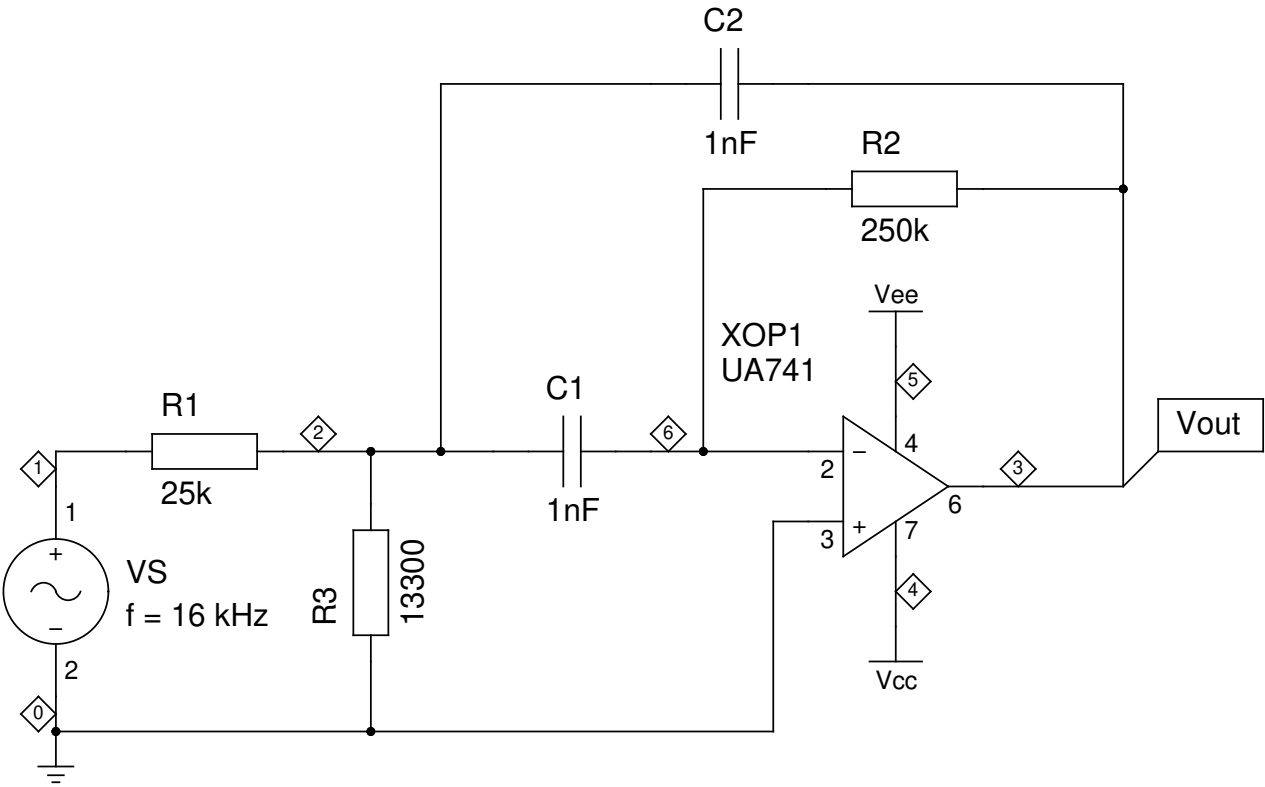

OCTAVE\_FILTER  
4 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.016.00.03.02.sch  
PAGE 01 OF 01

REVISION: 20240607  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 016: 4 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 25k  
R2 3 6 250K  
R3 0 2 13300  
C1 2 6 1nF  
C2 3 2 1nF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

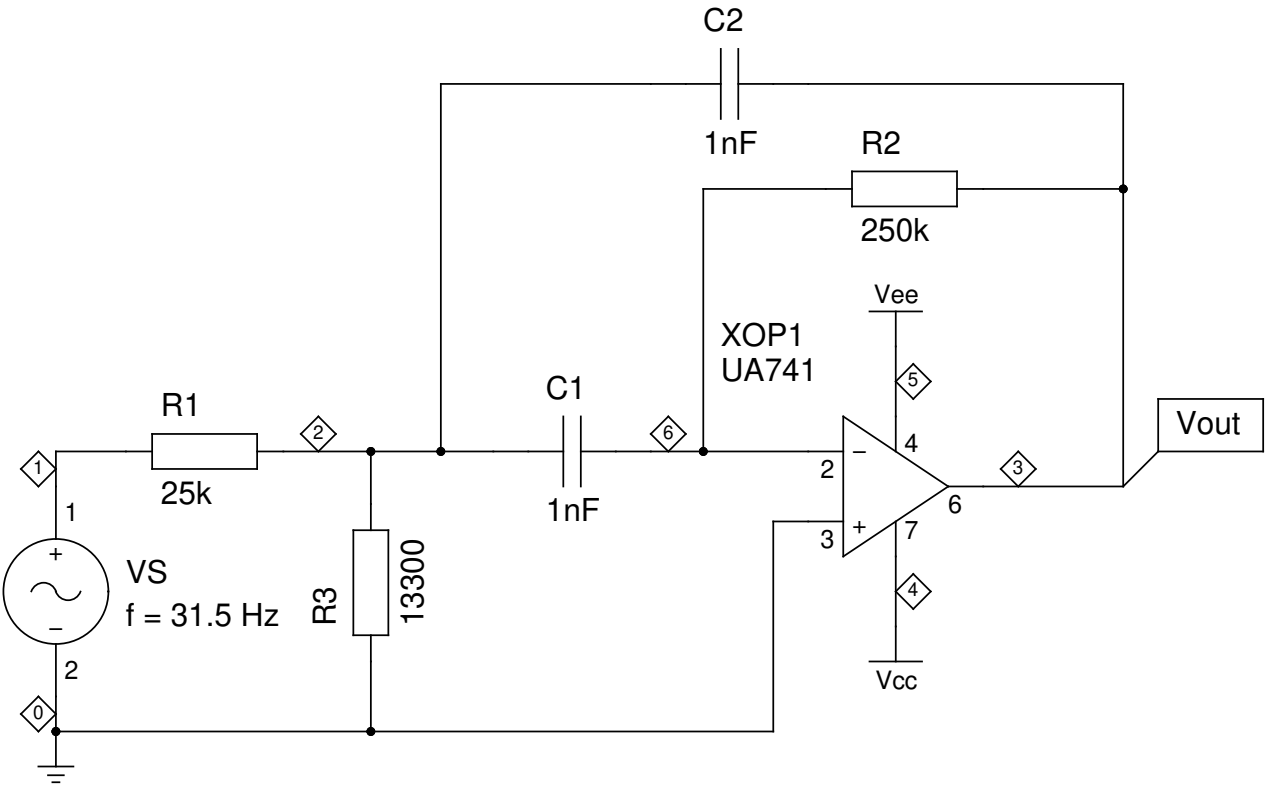

OCTAVE\_FILTER  
4 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.016.00.03.03.sch  
PAGE 01 OF 01

REVISION: 20240607  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 017: 4 KHZ DETECTOR – FREQUENCY RESPONSE

```
.INCLUDE UA741.subckt
```

```
.MODEL 1N4148 D IS=2e-14
```

VCC 4 0 15  
VEE 5 0 -15

```
VS 1 0 AC 1 SIN(0 1 4k)
C1 0 7 1uF
D1 2 3 1N4148
D2 3 6 1N4148
R1 1 2 10000
R2 6 7 1000
R3 8 2 15000
R4 0 9 10000
R5 8 9 .001
XOP1 0 2 0 4 5 3 UA741
XOP2 7 8 0 4 5 9 UA741
```


```
.PRINT OP Iter(0) V(3)
```

```
.PRINT AC VDB(3) VDB(9)
```

```
* FROM TO STEP
.TRAN 0.00001 0.2 0.0001
```

```
*      #STEPS/DECADE FROM  TO
.AC DEC 20      0.1  100k
```

.END

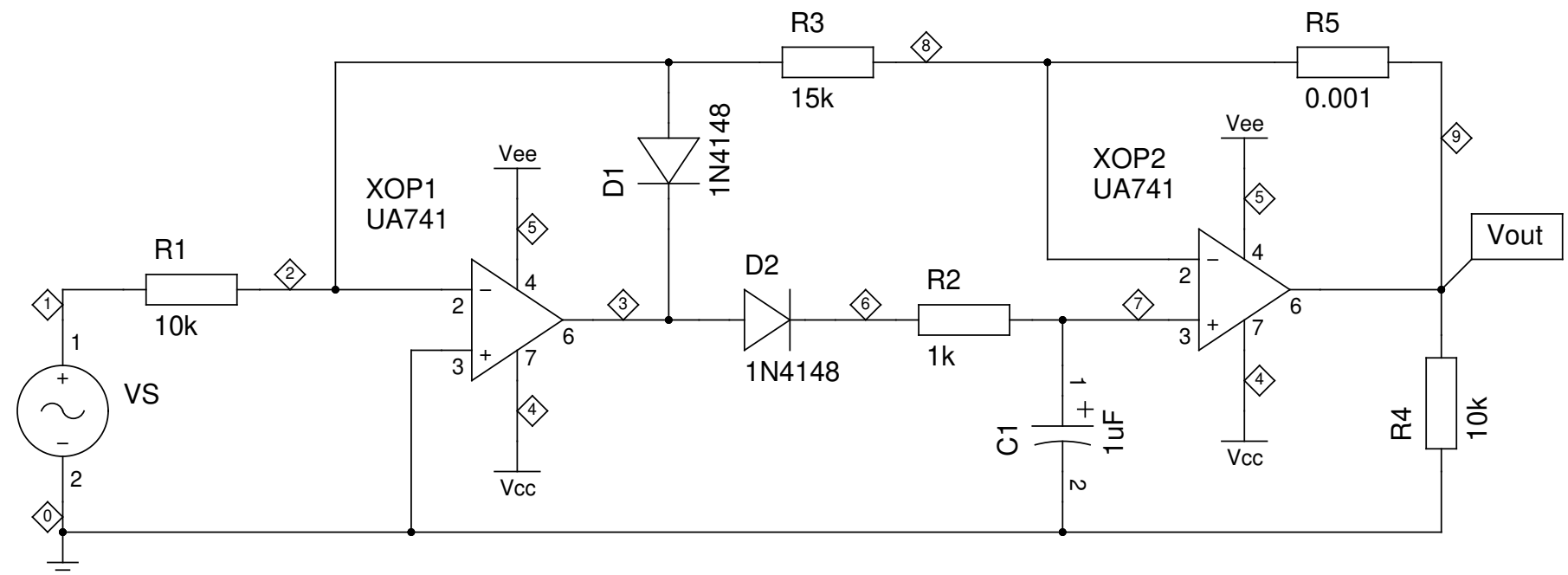

	OCTAVE_FILTER
	4 kHz Detector – Frequency response
TITLE	Schematic (DFS)

FILE: gnucap/26.017.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240607
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 017: 4 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1 4k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(9) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

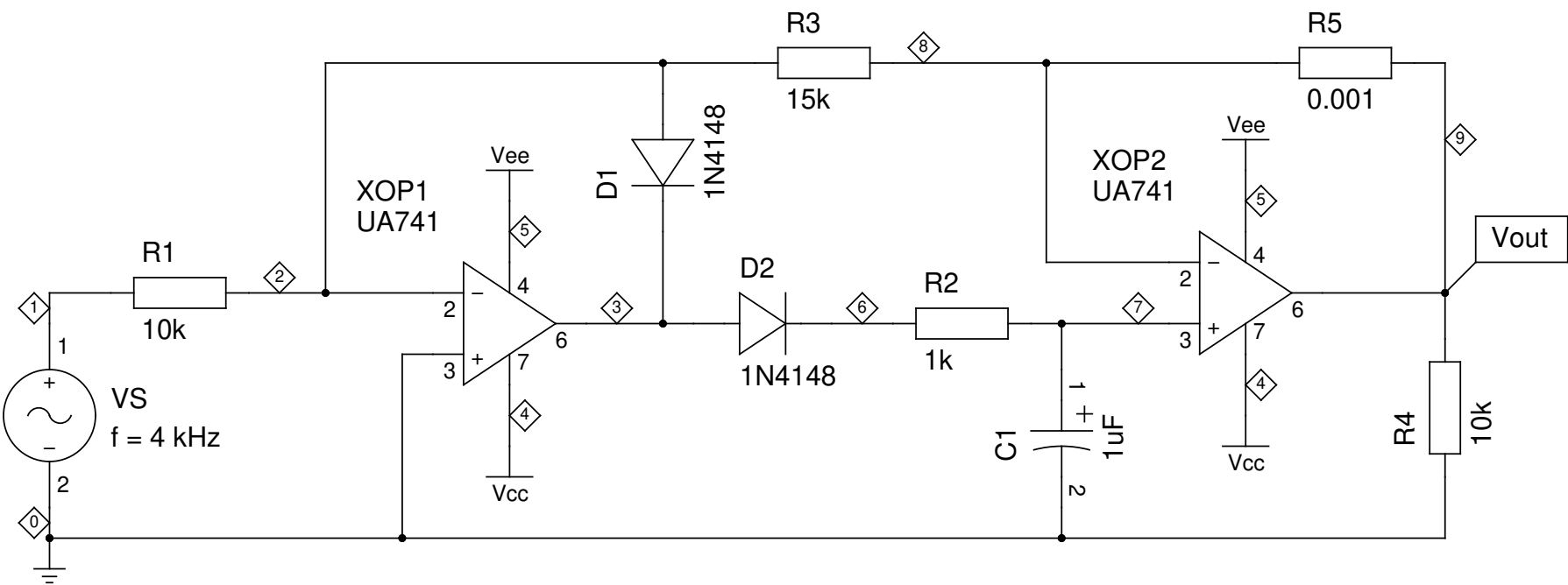

OCTAVE\_FILTER  
4 kHz Detector – Transient response (4 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.017.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240608  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 017: 4 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 4k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3) I(R4) I(R5) I(D1) I(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

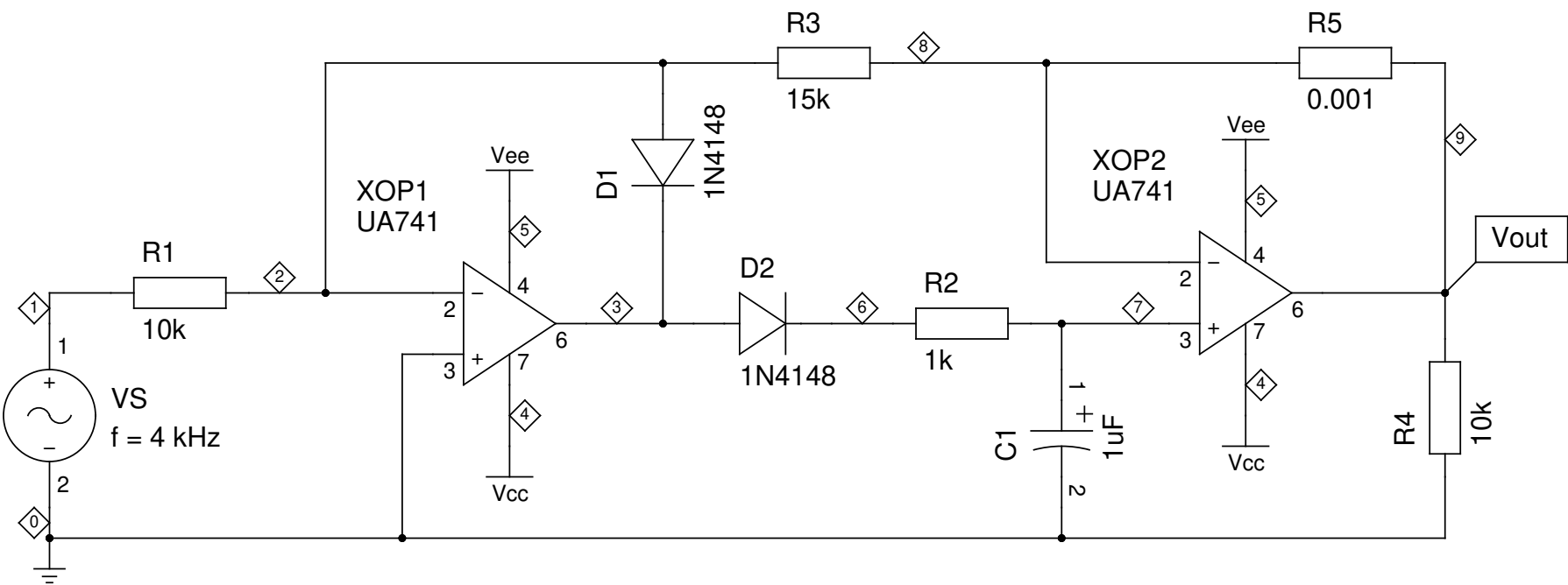

OCTAVE\_FILTER  
4 kHz Detector – Transient response (4 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.017.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240608  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 017: 4 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 4k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iiter(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3) P(R4) P(R5) P(D1) P(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

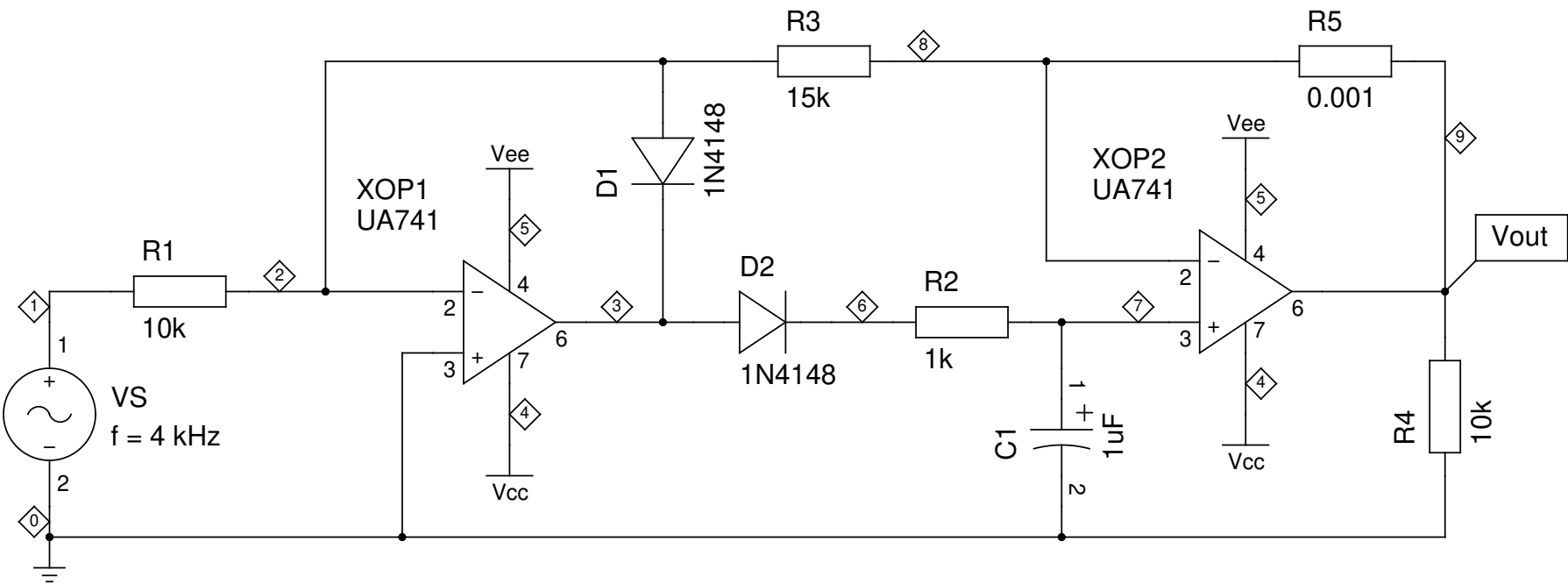

OCTAVE\_FILTER  
Octave Filter – Detector of the 4 kHz module (for simulation)  
TITLE Schematic (DFS)

FILE: gnuicap/26.017.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240608  
DRAWN BY: Bert Timmerman

A3



.TITLE OCTAVE FILTER – FUNCTION 018: 8 kHz BAND-PASS FILTER – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 1.41 8k)  
R1 1 2 26.7k  
R2 3 6 267K  
R3 0 2 14700  
C1 2 6 470pF  
C2 3 2 470pF  
XOP1 0 6 0 4 5 3 UA741


.PRINT OP Itr(0) V(3)

.PRINT AC VDB(3)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

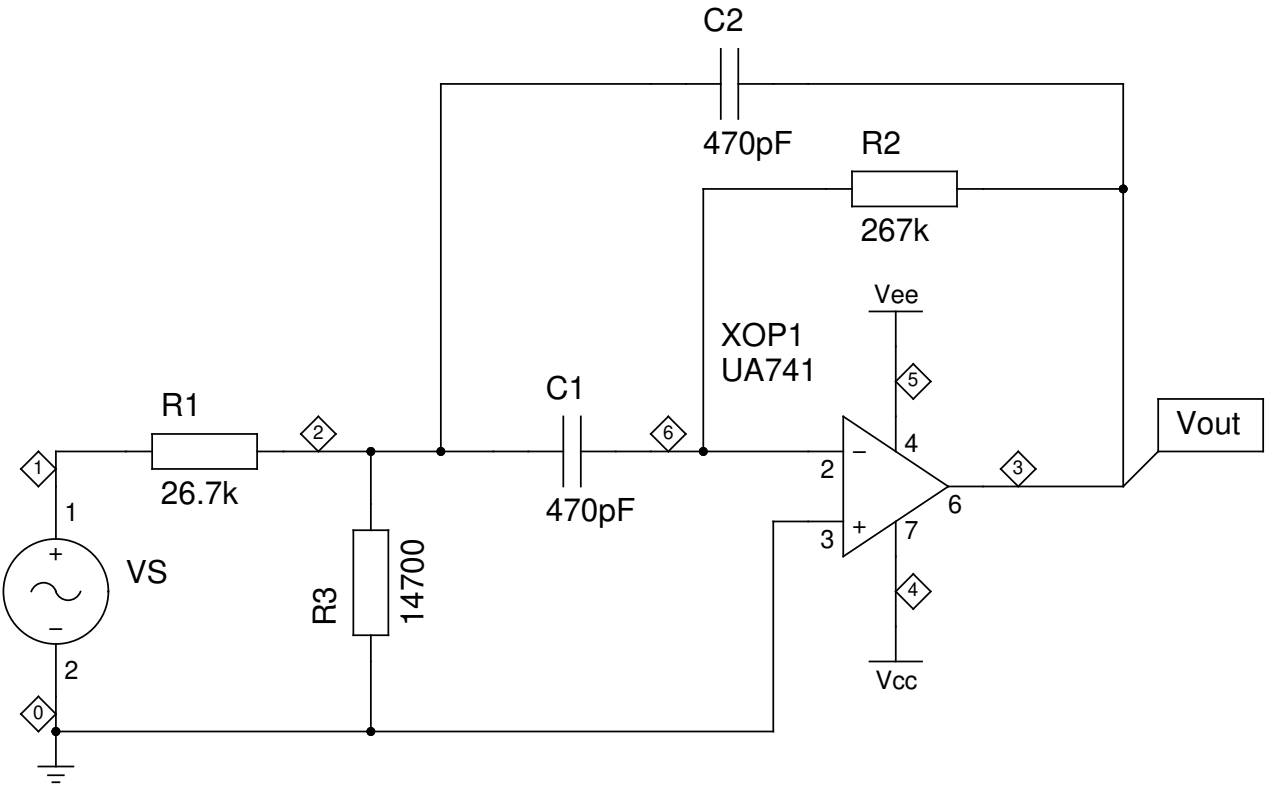

OCTAVE\_FILTER  
8 kHz Band-pass Filter – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.018.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240608  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 018: 8 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 8k)  
R1 1 2 26.7k  
R2 3 6 267K  
R3 0 2 14700  
C1 2 6 470pF  
C2 3 2 470pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.05 0.00001 TRACE ALL

.END

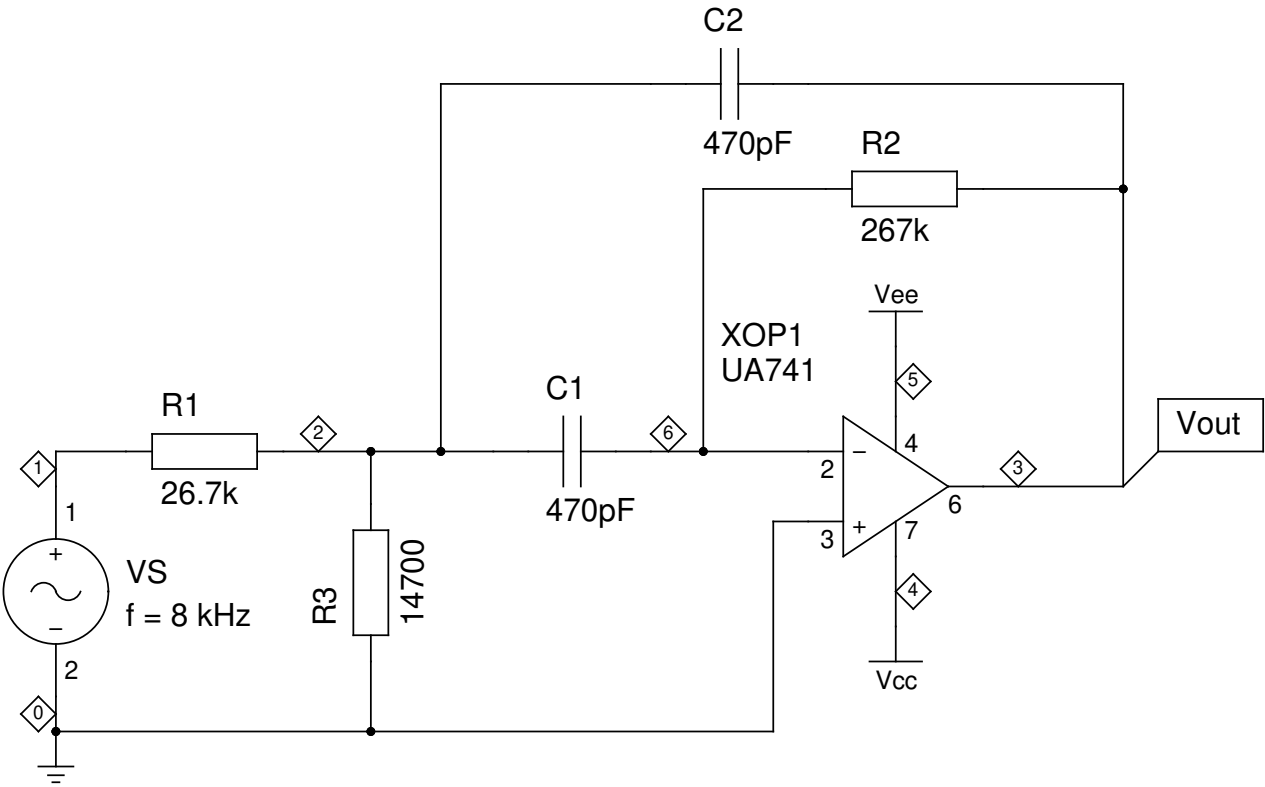

OCTAVE\_FILTER  
8 kHz Band-pass Filter – Transient response (8 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.018.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240608  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 018: 8 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 26.7k  
R2 3 6 267K  
R3 0 2 14700  
C1 2 6 470pF  
C2 3 2 470pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

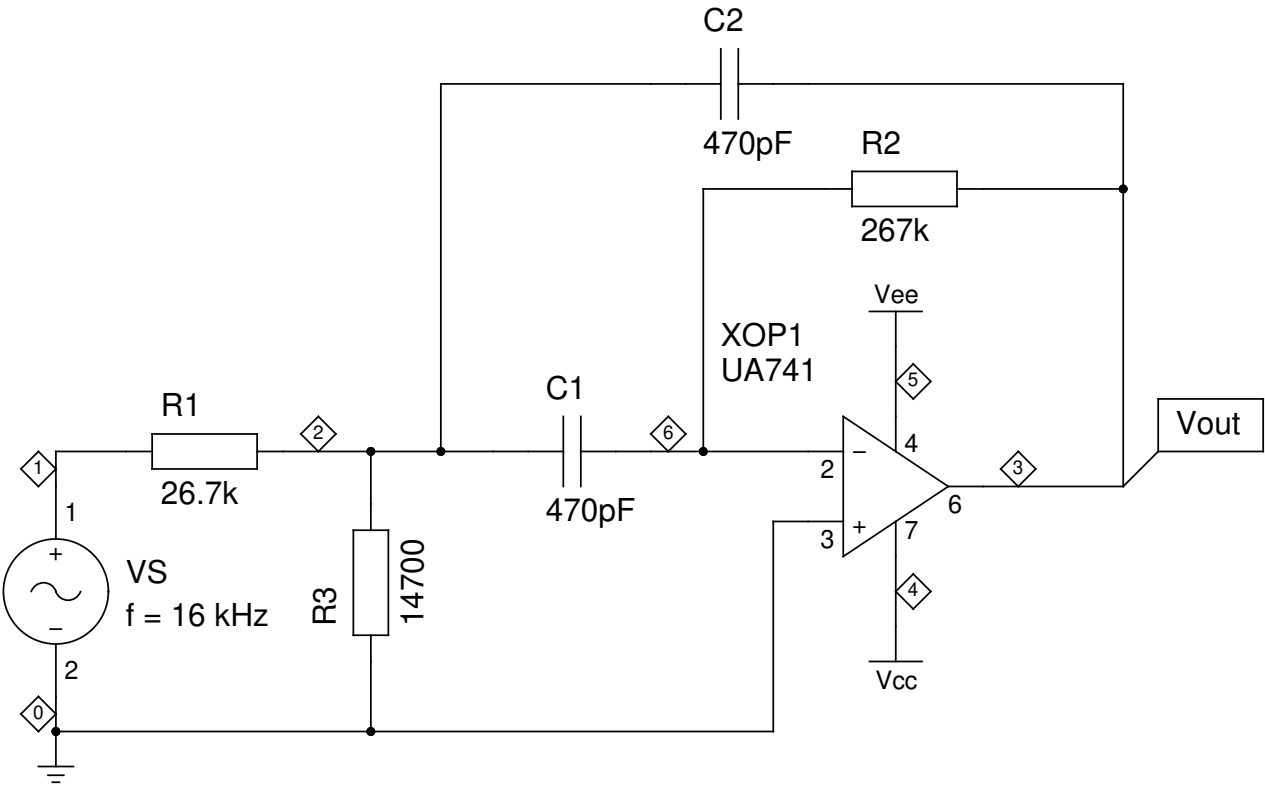

OCTAVE\_FILTER  
8 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.018.00.01.02.sch  
PAGE 01 OF 01

REVISION: 20240608  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 018: 8 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 26.7k  
R2 3 6 267K  
R3 0 2 14700  
C1 2 6 470pF  
C2 3 2 470pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

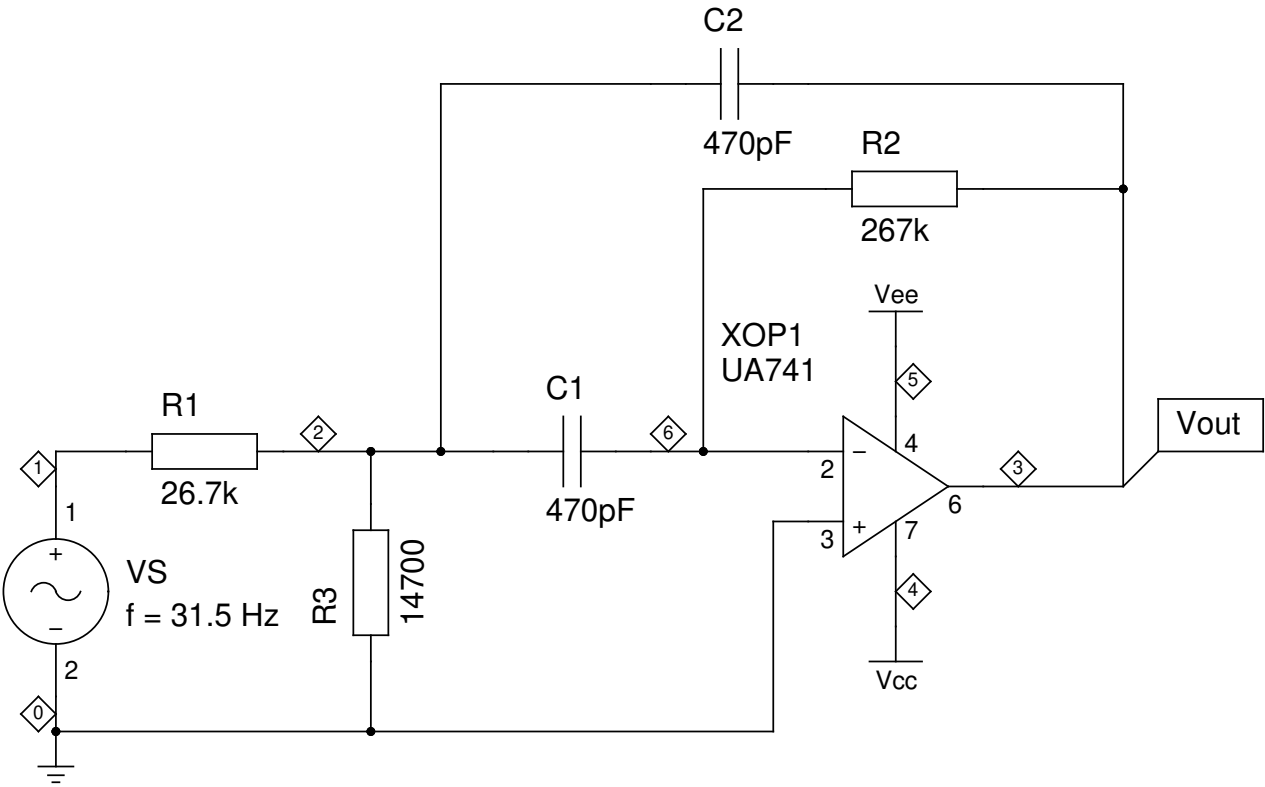

OCTAVE\_FILTER  
8 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.018.00.01.03.sch  
PAGE 01 OF 01

REVISION: 20240608  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 018: 8 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 8k)  
R1 1 2 26.7k  
R2 3 6 267K  
R3 0 2 14700  
C1 2 6 470pF  
C2 3 2 470pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

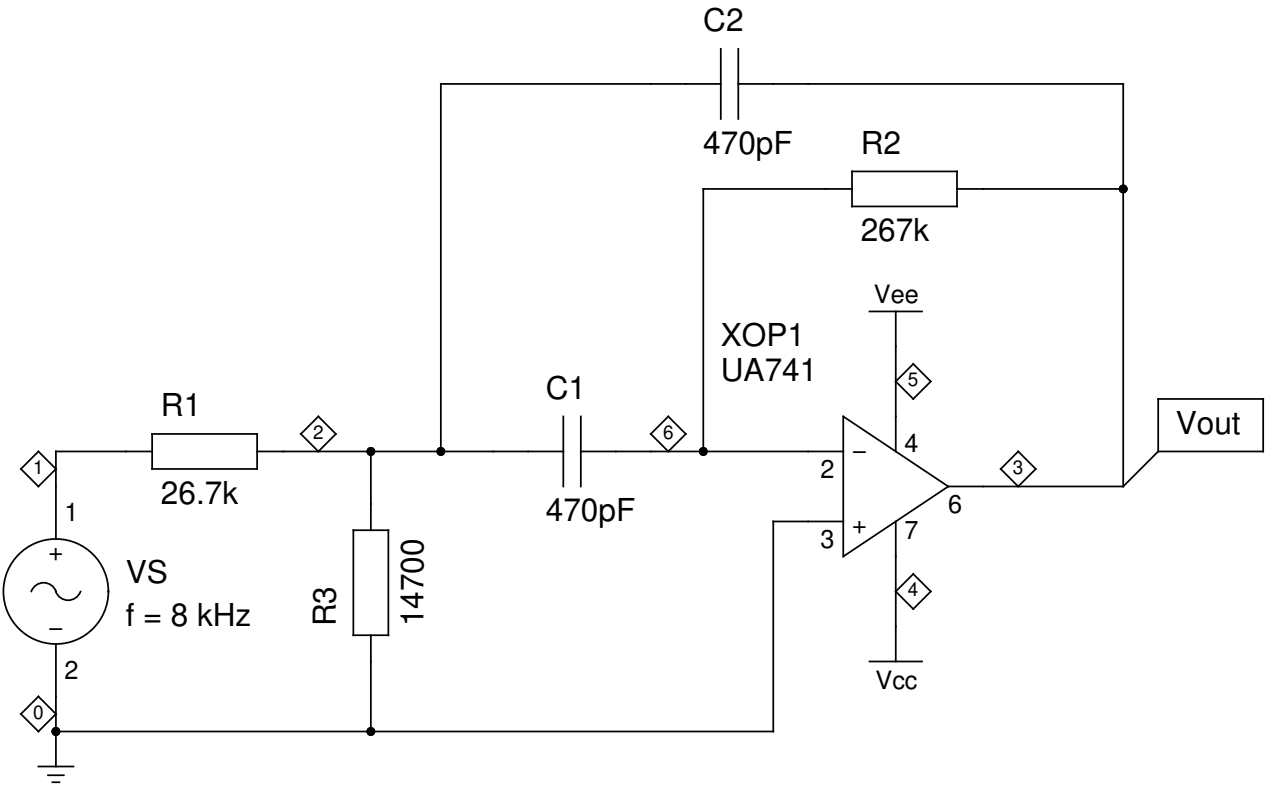

OCTAVE\_FILTER  
8 kHz Band-pass Filter – Transient response (8 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.018.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240608  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 018: 8 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 26.7k  
R2 3 6 267K  
R3 0 2 14700  
C1 2 6 470pF  
C2 3 2 470pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

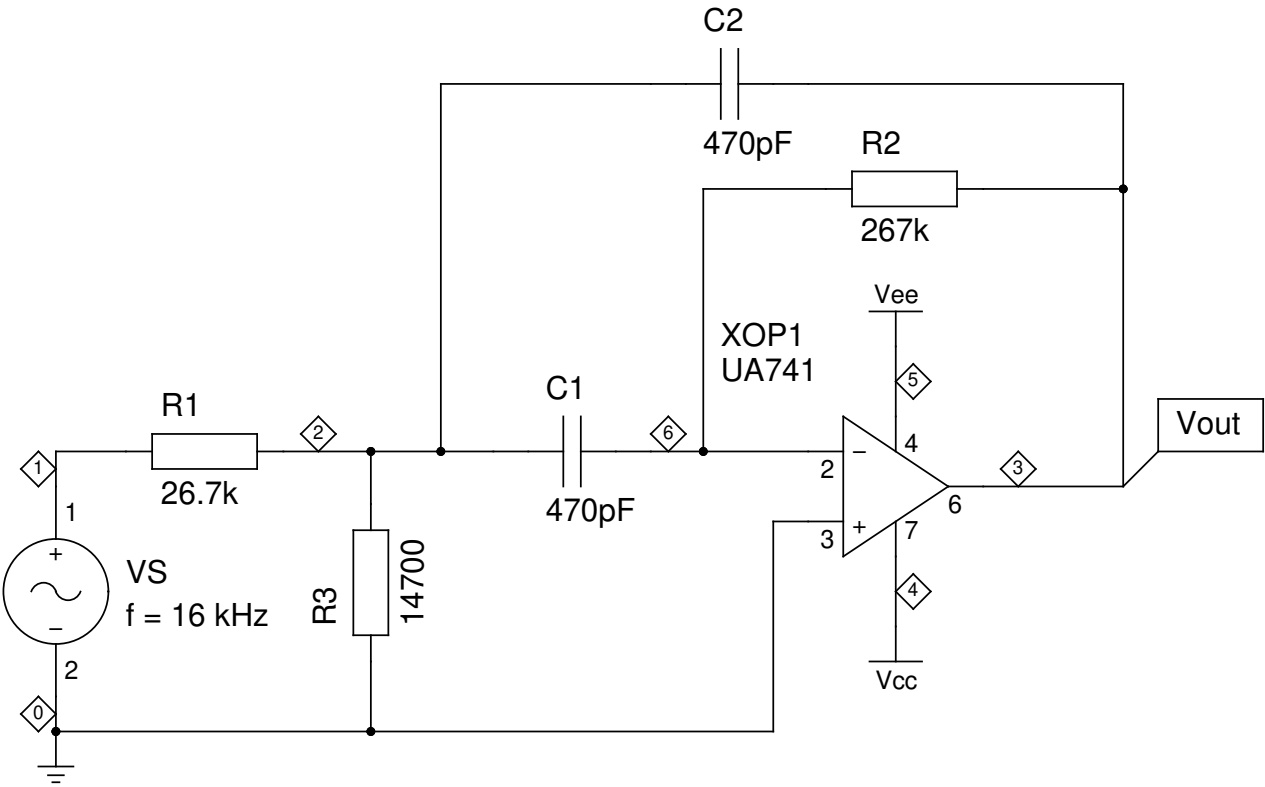

OCTAVE\_FILTER  
8 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.018.00.02.02.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 018: 8 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 26.7k  
R2 3 6 267K  
R3 0 2 14700  
C1 2 6 470pF  
C2 3 2 470pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

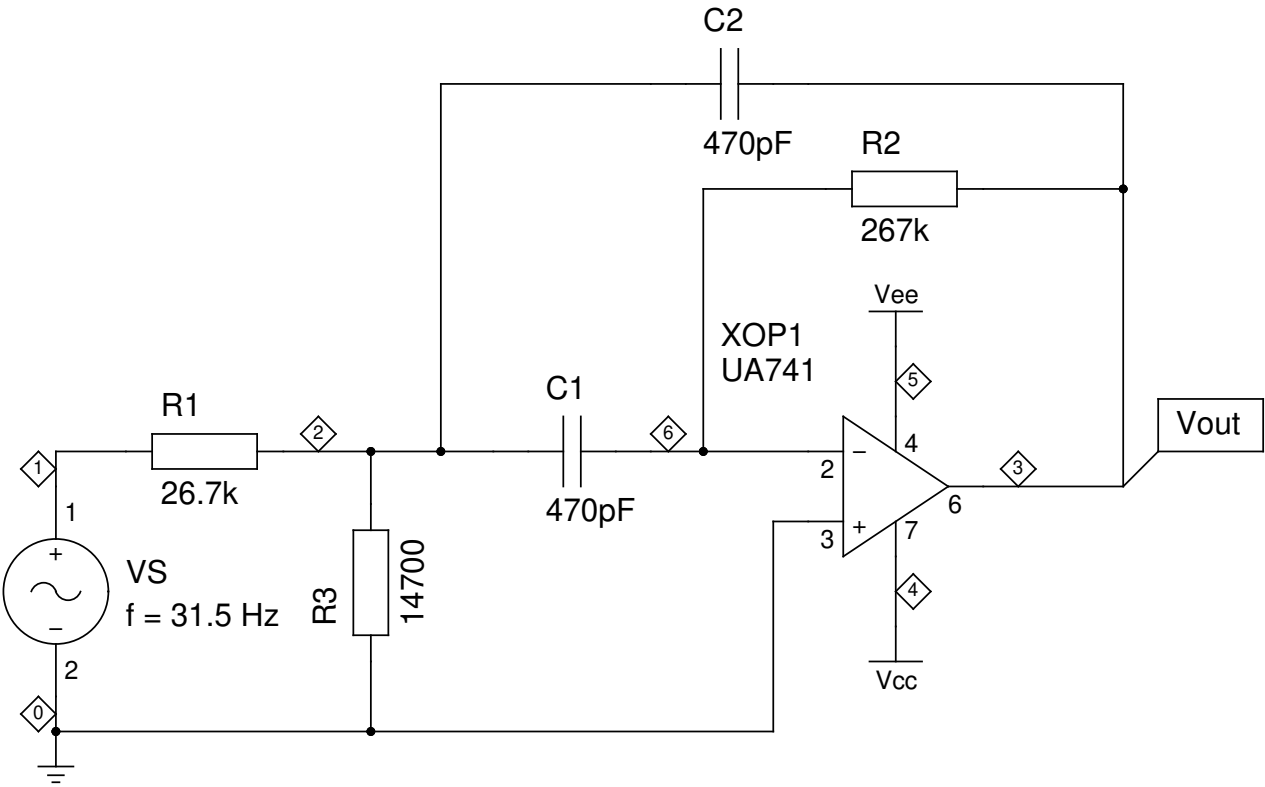

OCTAVE\_FILTER  
8 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.018.00.02.03.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 018: 8 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 8k)  
R1 1 2 26.7k  
R2 3 6 267K  
R3 0 2 14700  
C1 2 6 470pF  
C2 3 2 470pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

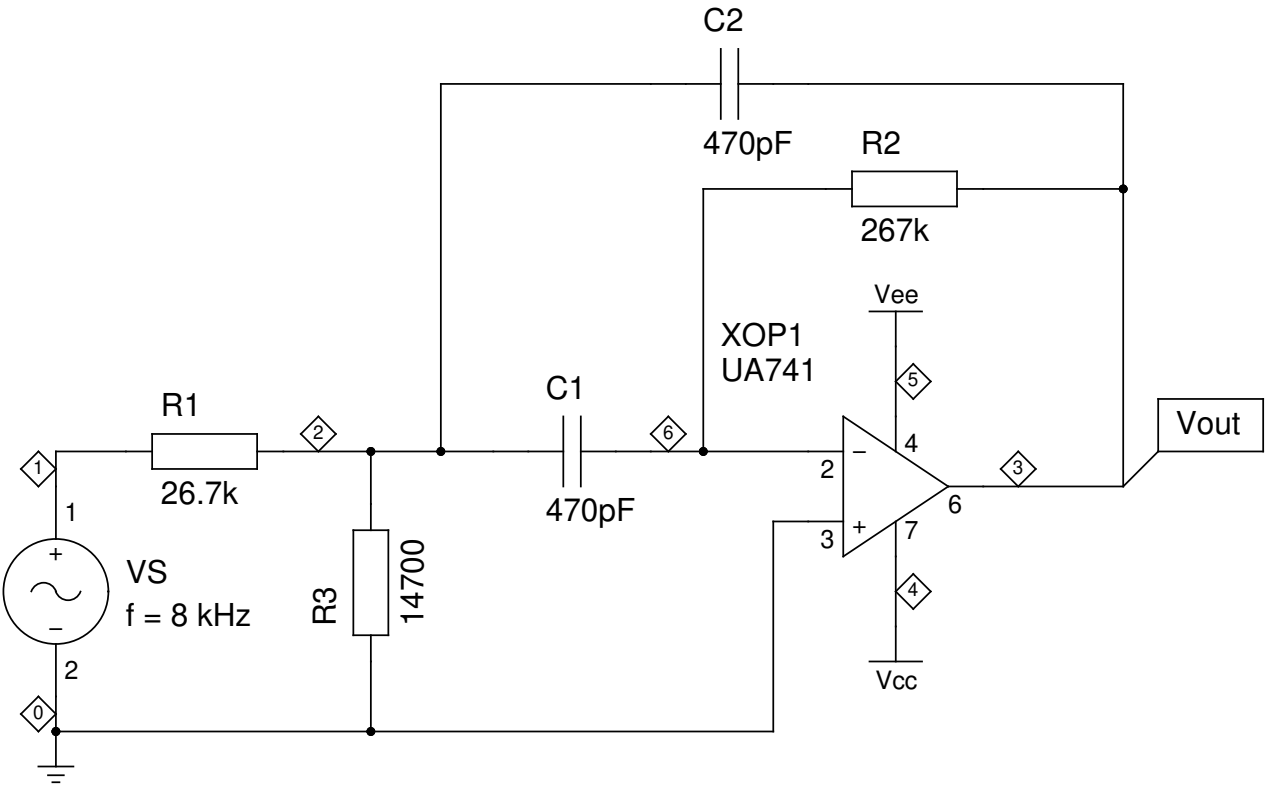

OCTAVE\_FILTER  
8 kHz Band-pass Filter – Transient response (8 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.018.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman



.TITLE OCTAVE FILTER – FUNCTION 018: 8 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 26.7k  
R2 3 6 267K  
R3 0 2 14700  
C1 2 6 470pF  
C2 3 2 470pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

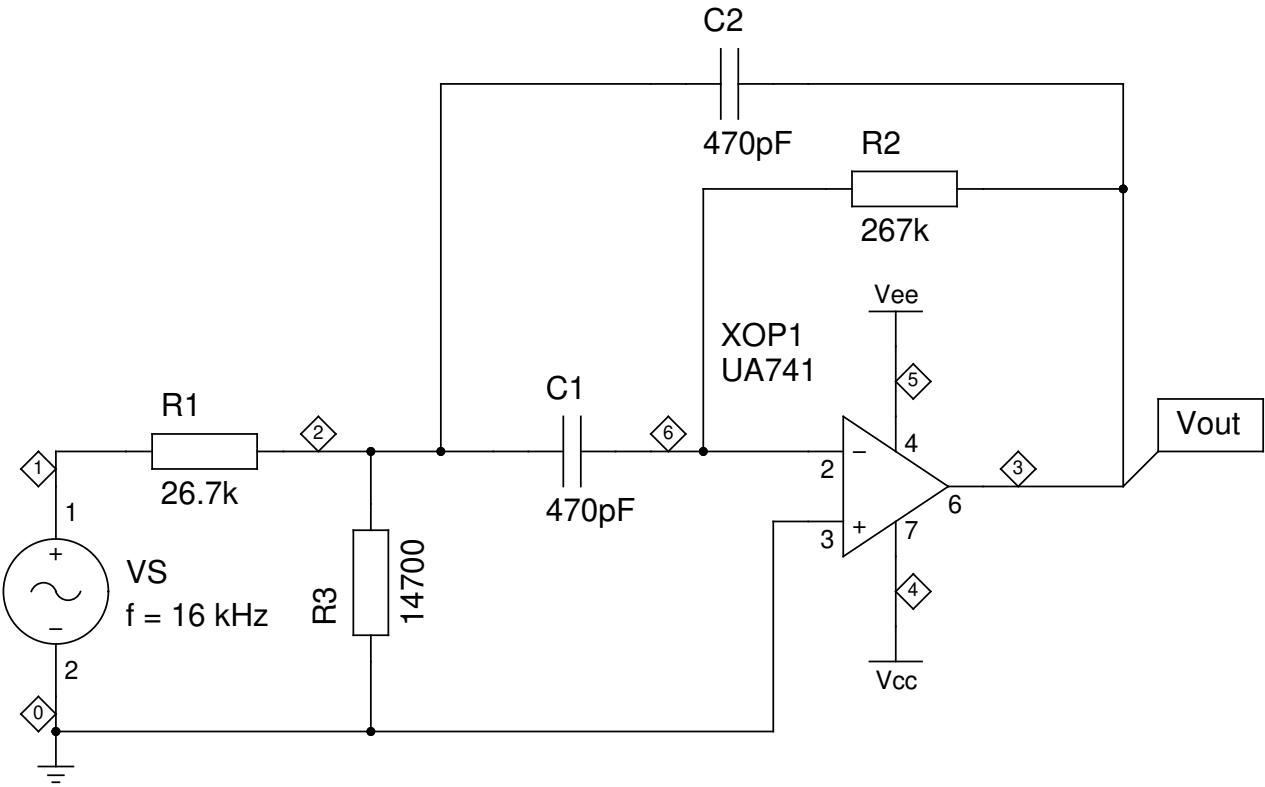

OCTAVE\_FILTER  
8 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.018.00.03.02.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 018: 8 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 26.7k  
R2 3 6 267K  
R3 0 2 14700  
C1 2 6 470pF  
C2 3 2 470pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END


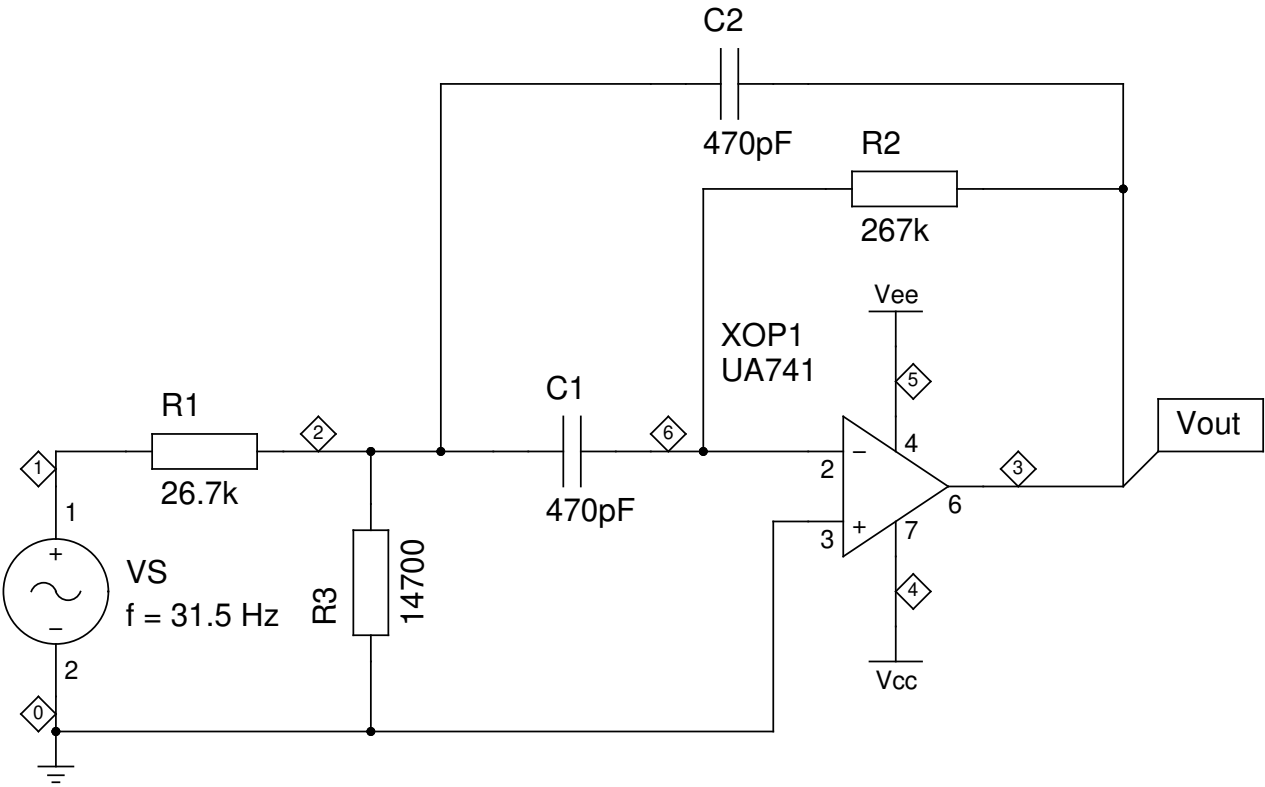


OCTAVE\_FILTER  
8 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.018.00.03.03.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

.END

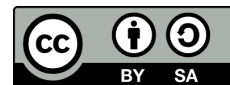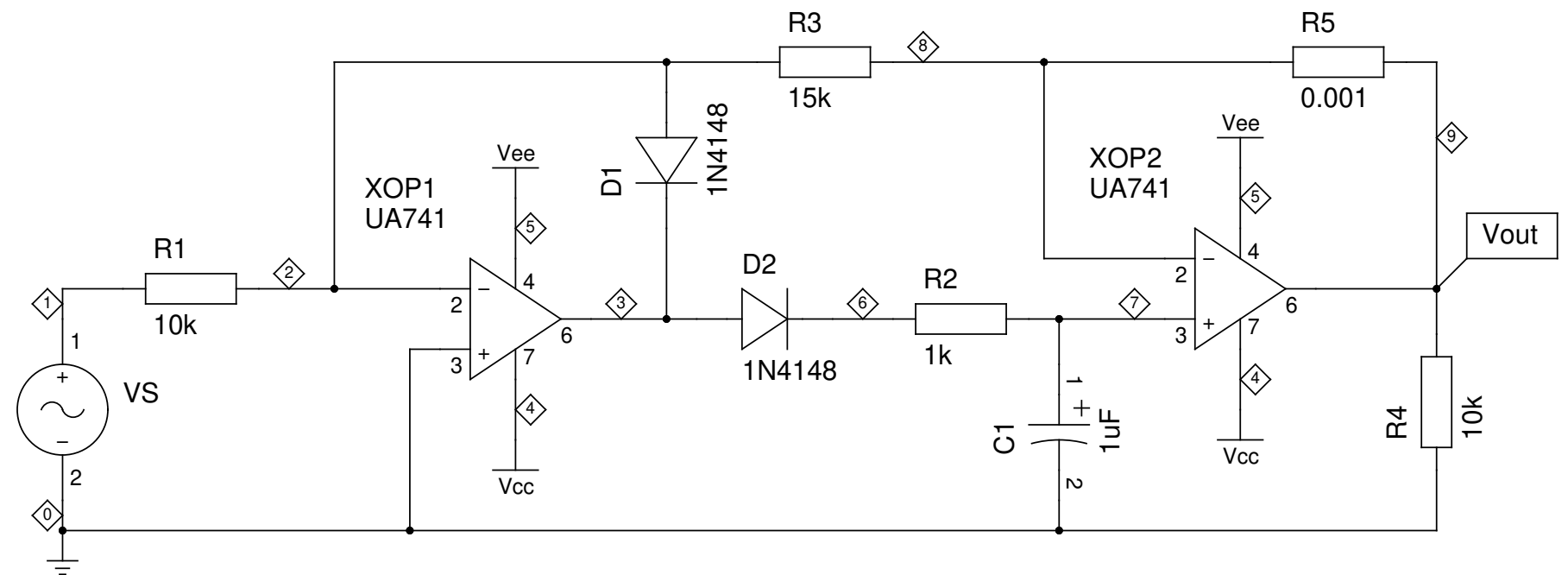

A3

.TITLE OCTAVE FILTER – FUNCTION 019: 8 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1 8k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(9) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.02 0.00001

.END

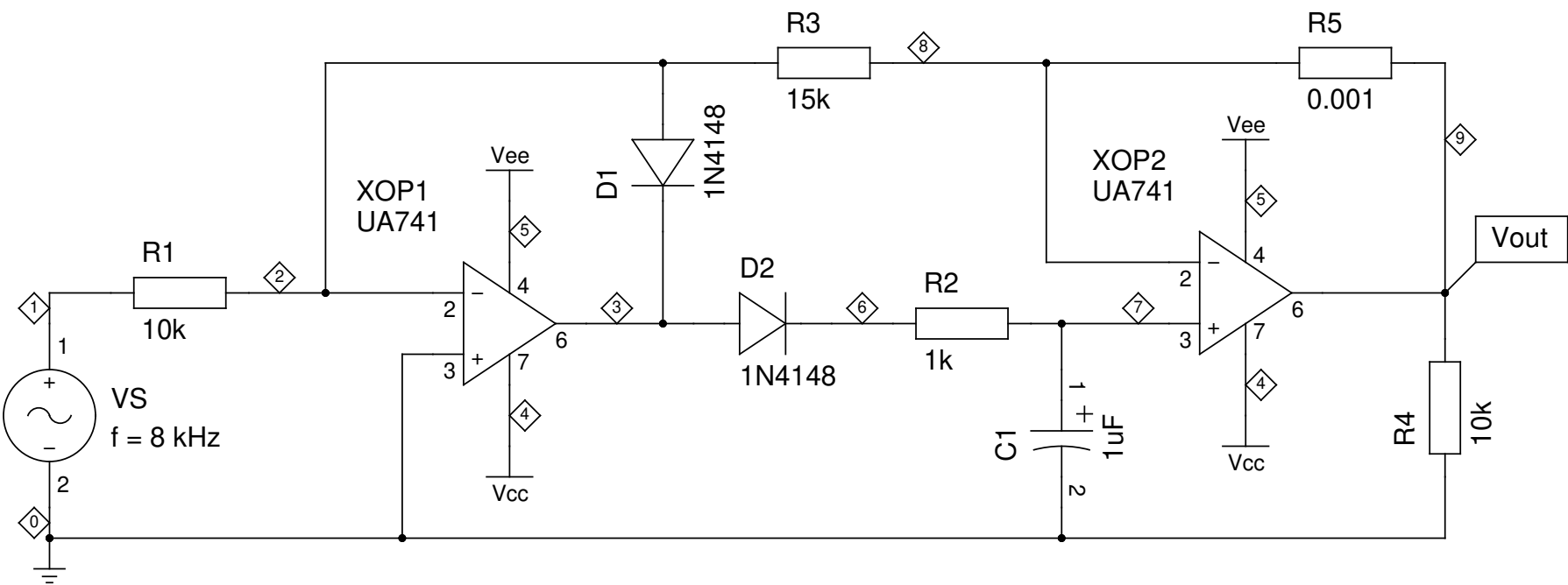

OCTAVE\_FILTER  
8 kHz Detector – Transient response (8 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.019.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 019: 8 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 8k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3) I(R4) I(R5) I(D1) I(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

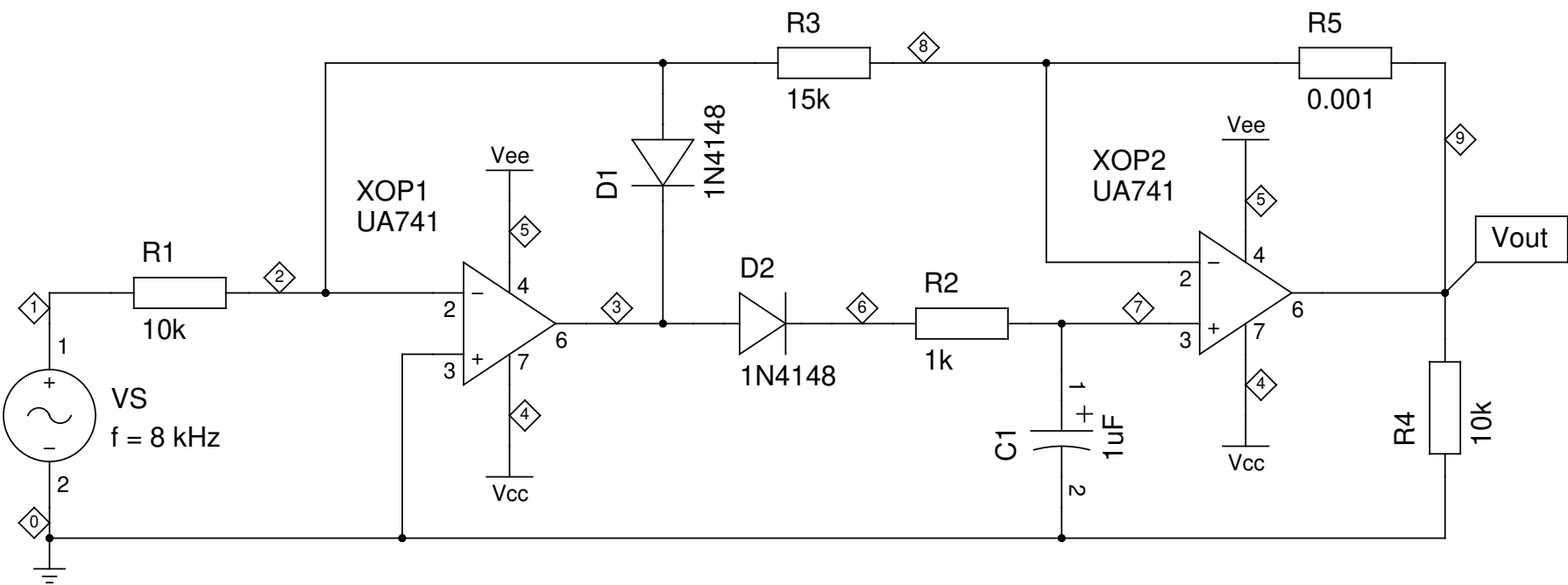

OCTAVE\_FILTER  
8 kHz Detector – Transient response (8 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.019.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 019: 8 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 8k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iiter(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3) P(R4) P(R5) P(D1) P(D2)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001

.END

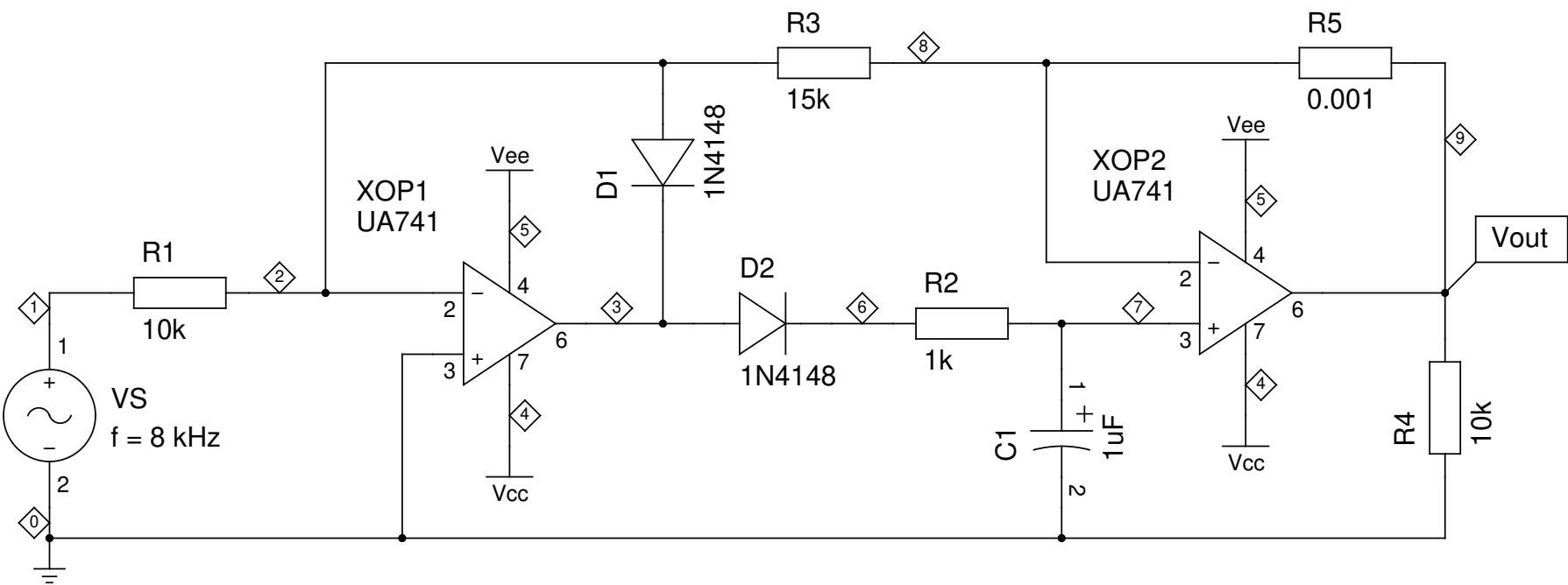

OCTAVE\_FILTER  
8 kHz Detector – Transient response (8 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.019.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 020: 16 kHz BAND-PASS FILTER – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 28k  
R2 3 6 280K  
R3 0 2 14700  
C1 2 6 220pF  
C2 3 2 220pF  
XOP1 0 6 0 4 5 3 UA741


.PRINT OP Iter(0) V(3)

.PRINT AC VDB(3)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

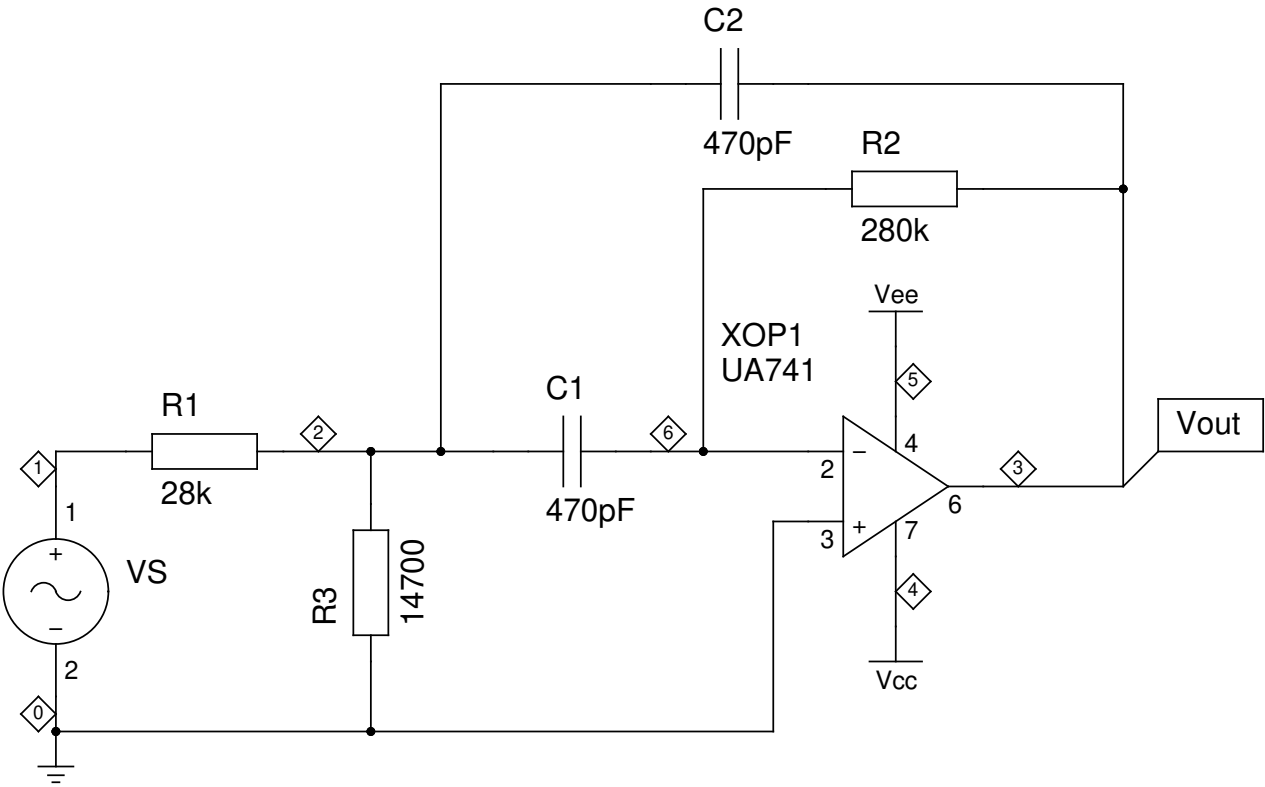

OCTAVE\_FILTER  
16 kHz Band-pass Filter – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.020.00.00.01.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 020: 16 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 28k  
R2 3 6 280K  
R3 0 2 14700  
C1 2 6 220pF  
C2 3 2 220pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.05 0.00001 TRACE ALL

.END

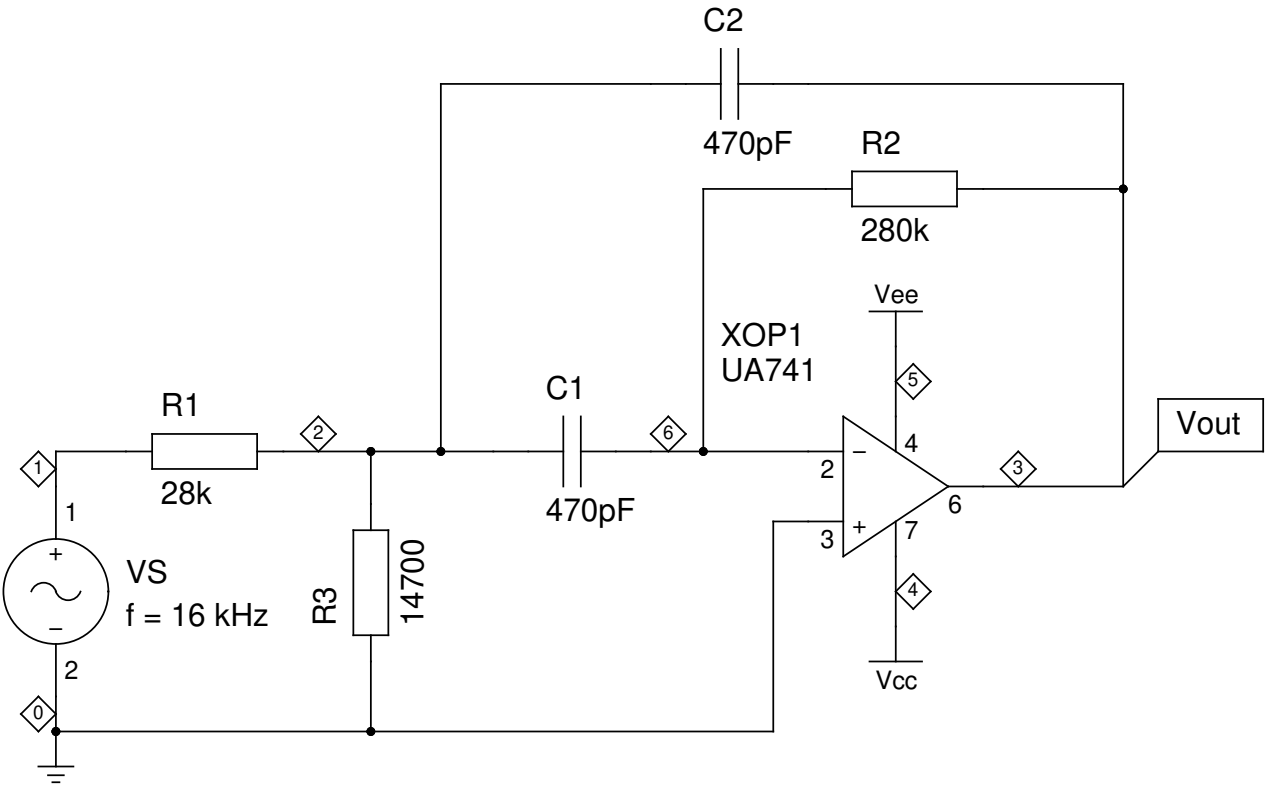

OCTAVE\_FILTER  
16 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.020.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman



.TITLE OCTAVE FILTER – FUNCTION 020: 16 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 28k  
R2 3 6 280K  
R3 0 2 14700  
C1 2 6 220pF  
C2 3 2 220pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

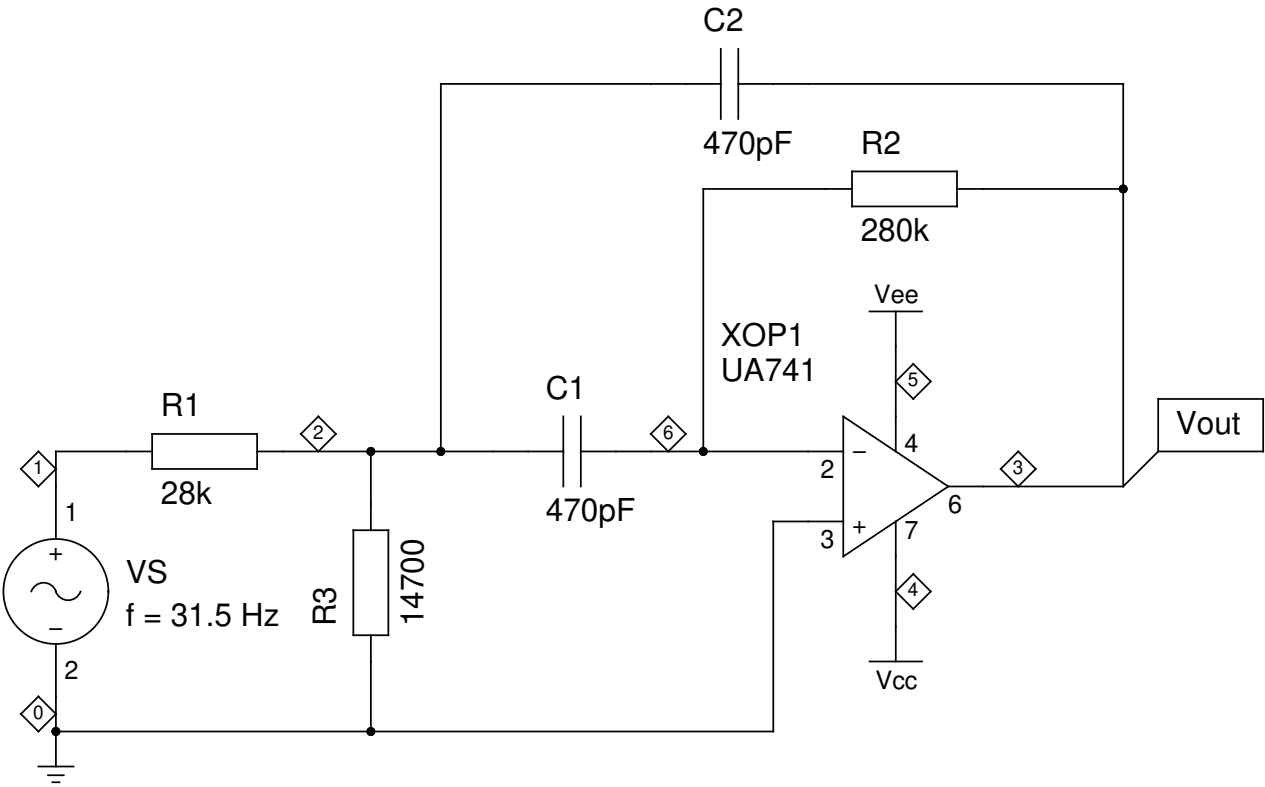

OCTAVE\_FILTER  
16 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.020.00.01.02.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 020: 16 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 28k  
R2 3 6 280K  
R3 0 2 14700  
C1 2 6 220pF  
C2 3 2 220pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.01 0.00001 TRACE ALL

.END

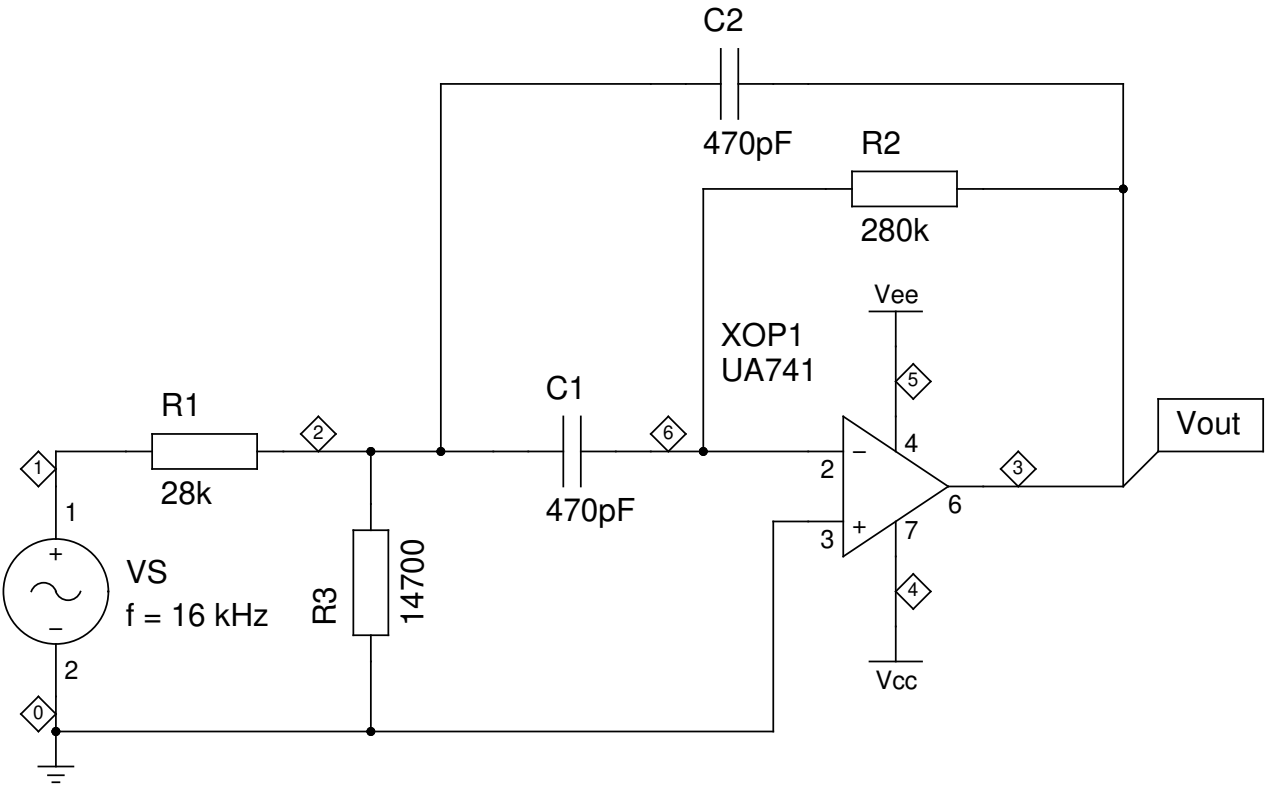

OCTAVE\_FILTER  
16 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.020.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 020: 16 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 28k  
R2 3 6 280K  
R3 0 2 14700  
C1 2 6 220pF  
C2 3 2 220pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3)

\* FROM TO STEP  
.TRAN 0 0.02 0.00001 TRACE ALL

.END

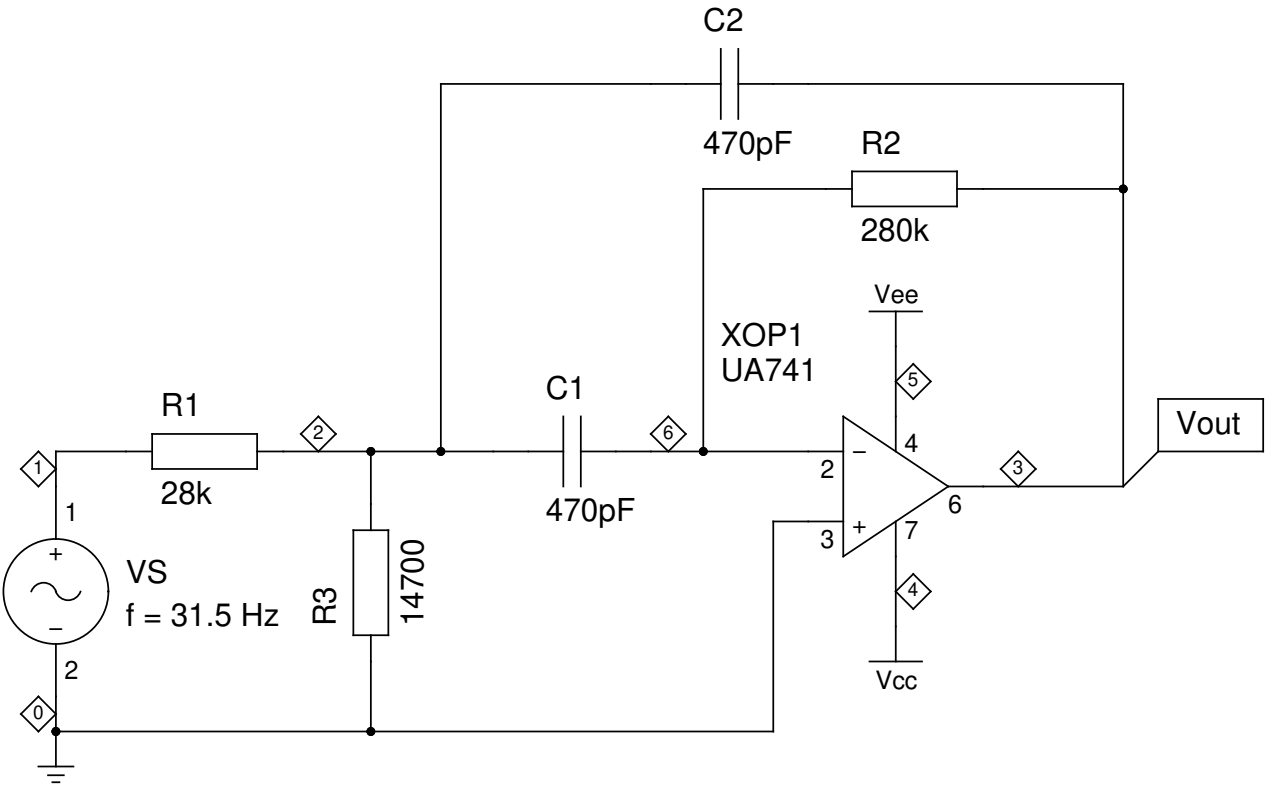

OCTAVE\_FILTER  
16 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.020.00.02.02.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 020: 16 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
R1 1 2 28k  
R2 3 6 280K  
R3 0 2 14700  
C1 2 6 220pF  
C2 3 2 220pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.02 0.00001 TRACE ALL

.END

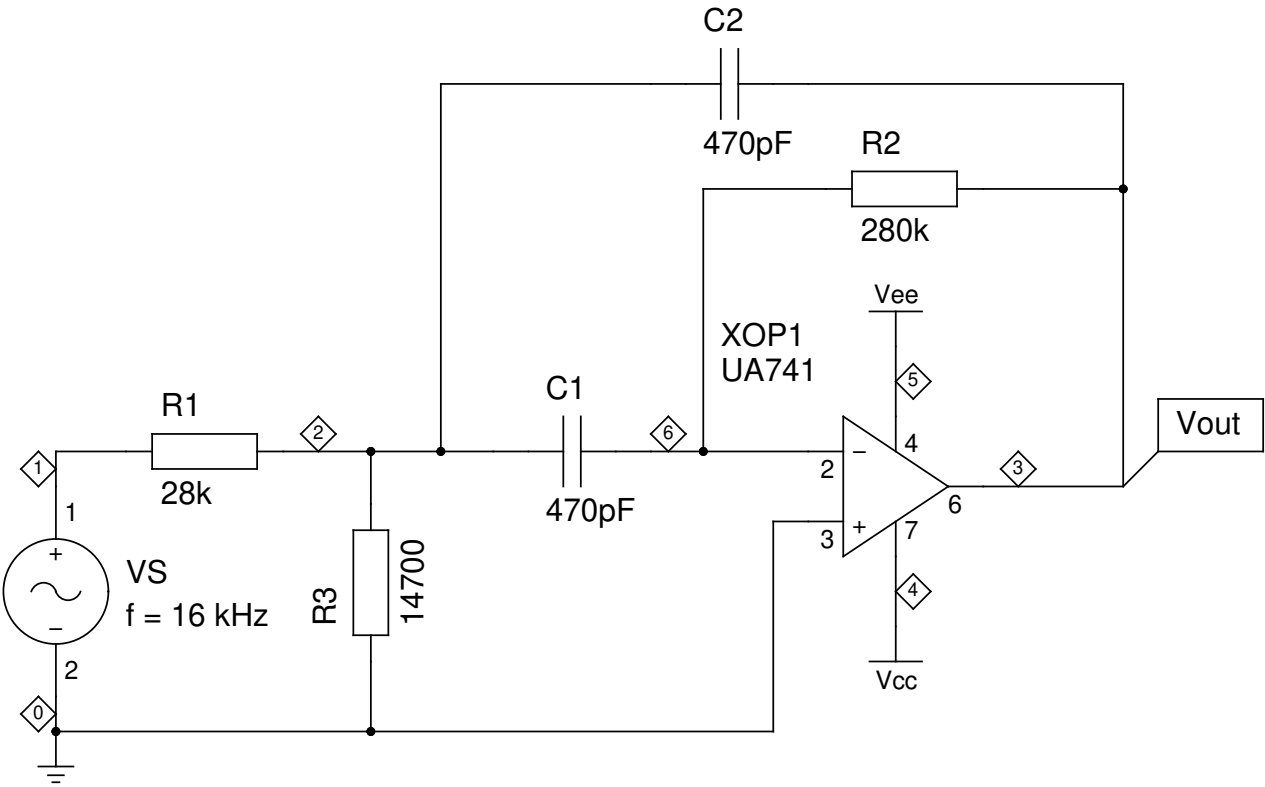

OCTAVE\_FILTER  
16 kHz Band-pass Filter – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.020.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 020: 16 KHZ BAND–PASS FILTER – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 31.5)  
R1 1 2 28k  
R2 3 6 280K  
R3 0 2 14700  
C1 2 6 220pF  
C2 3 2 220pF  
XOP1 0 6 0 4 5 3 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3)

\* FROM TO STEP  
.TRAN 0 0.1 0.00001 TRACE ALL

.END

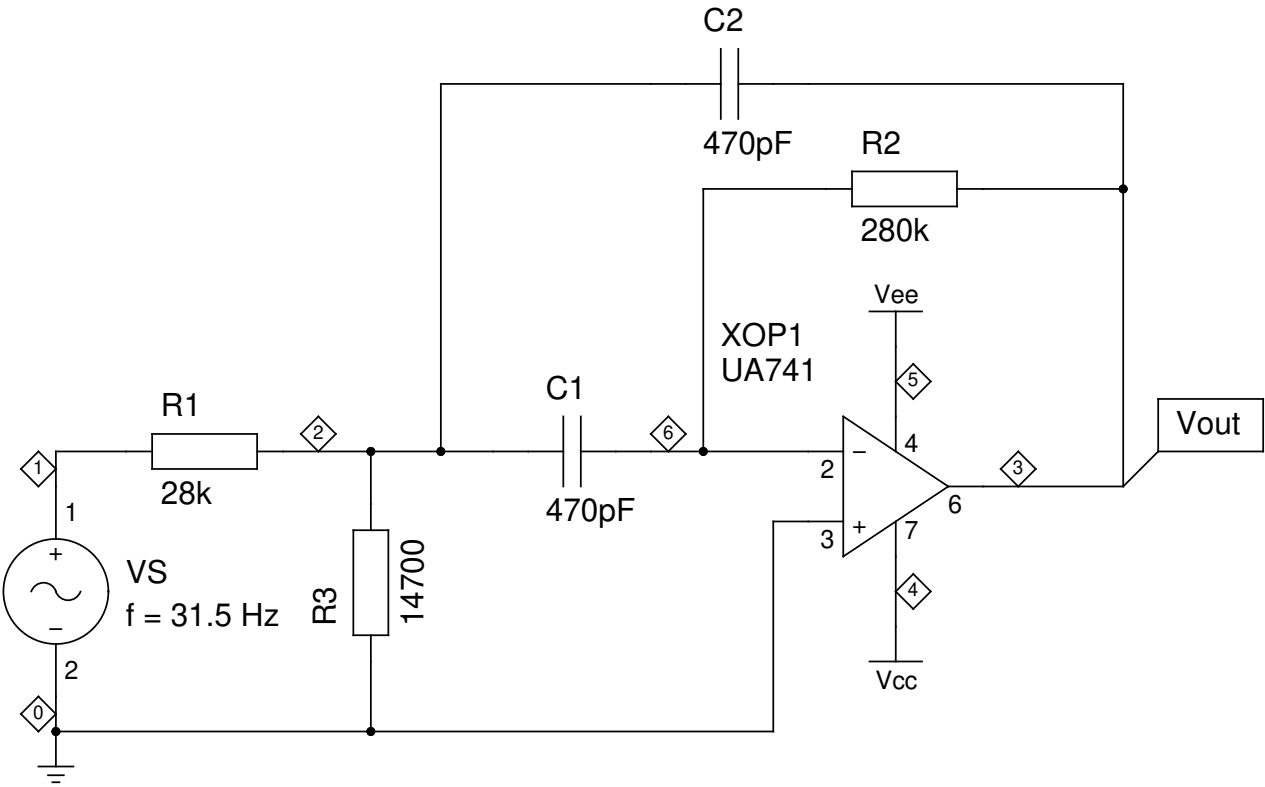

OCTAVE\_FILTER  
16 kHz Band-pass Filter – Transient response (31.5 Hz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.020.00.03.02.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 0121 16 KHZ DETECTOR – FREQUENCY RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 15  
VEE 5 0 -15

VS 1 0 AC 1 SIN(0 1 16k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741


.PRINT OP Iiter(0) V(3)

.PRINT AC VDB(3) VDB(9)

\* FROM TO STEP  
.TRAN 0.00001 0.2 0.0001

\* #STEPS/DECADE FROM TO  
.AC DEC 20 0.1 100k

.END

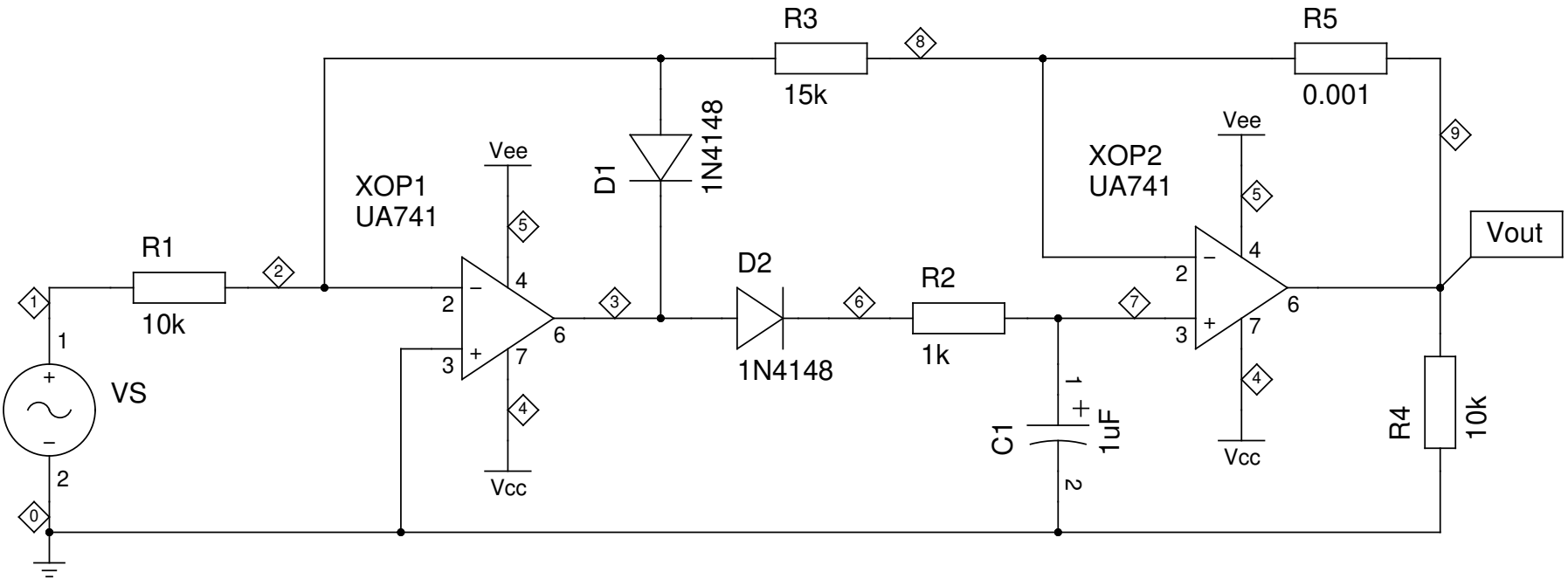

OCTAVE\_FILTER  
16 kHz Detector – Frequency response  
TITLE Schematic (DFS)

FILE: gnuicap/26.021.00.00.01.sch  
PAGE 01 OF 01

REVISION: 2020609  
DRAWN BY: Bert Timmerman

.TITLE OCTAVE FILTER – FUNCTION 021: 16 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1 16k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iter(0) V(3)

.PRINT TRAN V(1) V(3) V(9) V(4) V(5)

\* FROM TO STEP  
.TRAN 0 0.02 0.00001

.END

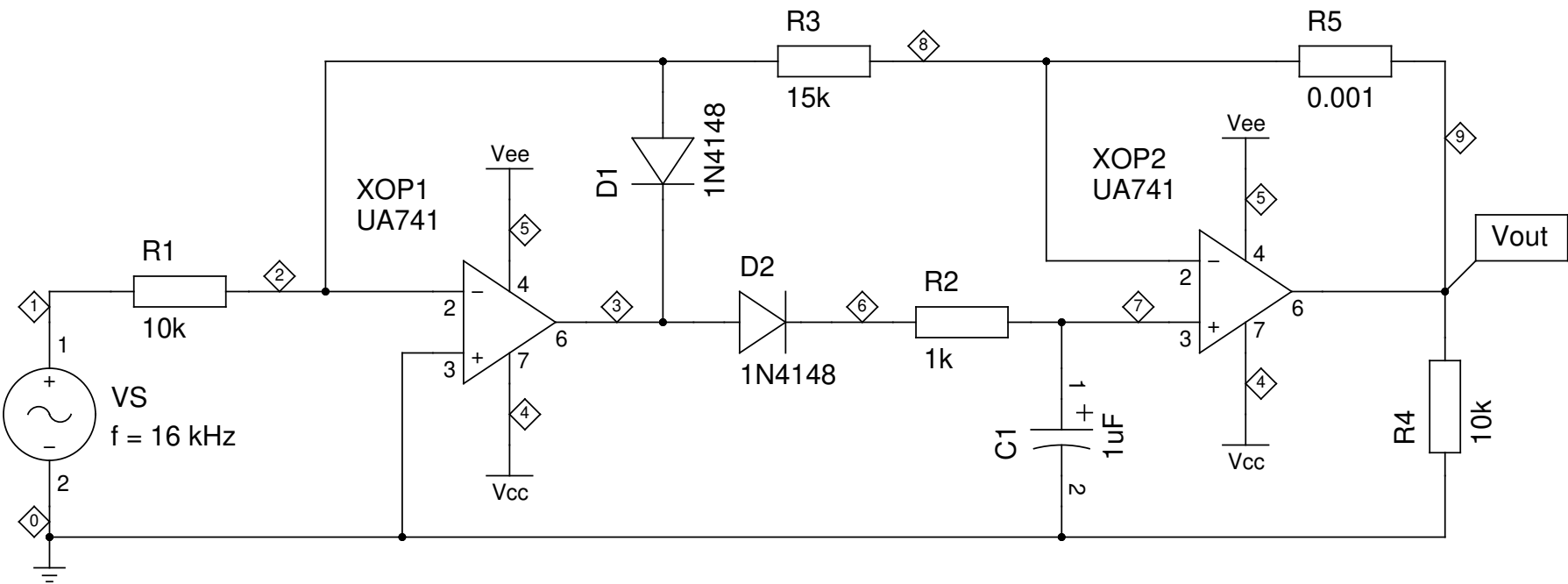

OCTAVE\_FILTER  
16 kHz Detector – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.021.00.01.01.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

A3

.TITLE OCTAVE FILTER – FUNCTION 021: 16 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)


VS 1 0 AC 1 SIN(0 1.41 16k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Itr(0) V(3)

.PRINT TRAN I(R1) I(R2) I(R3) I(R4) I(R5) I(D1) I(D2)

\* FROM TO STEP  
.TRAN 0 0.02 0.00001

.END

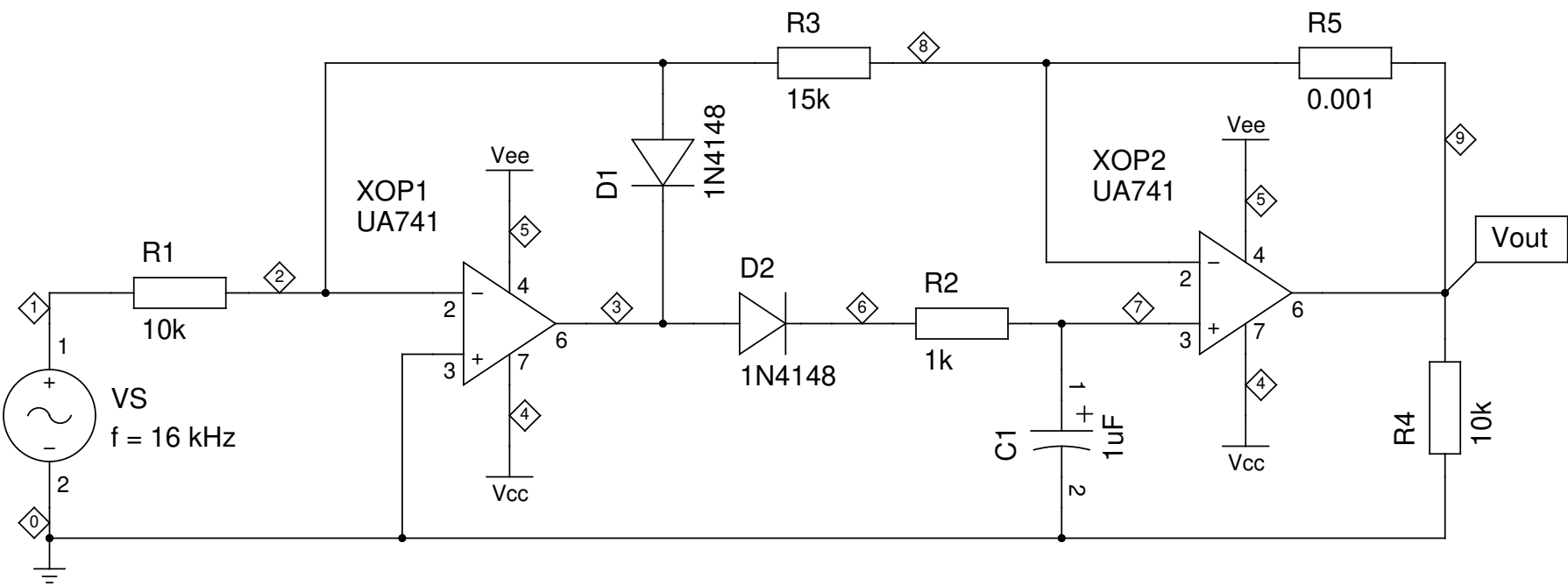

OCTAVE\_FILTER  
16 kHz Detector – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.021.00.02.01.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

A3



.TITLE OCTAVE FILTER – FUNCTION 021: 16 KHZ DETECTOR – TRANSIENT RESPONSE

.INCLUDE UA741.subckt

.MODEL 1N4148 D IS=2e-14

VCC 4 0 pulse(iv=0 pv=15 rise=0.01)  
VEE 5 0 pulse(iv=0 pv=-15 rise=0.01)



VS 1 0 AC 1 SIN(0 1.41 16k)  
C1 0 7 1uF  
D1 2 3 1N4148  
D2 3 6 1N4148  
R1 1 2 10000  
R2 6 7 1000  
R3 8 2 15000  
R4 0 9 10000  
R5 8 9 .001  
XOP1 0 2 0 4 5 3 UA741  
XOP2 7 8 0 4 5 9 UA741

.PRINT OP Iiter(0) V(3)

.PRINT TRAN P(R1) P(R2) P(R3) P(R4) P(R5) P(D1) P(D2)

\* FROM TO STEP  
.TRAN 0 0.02 0.00001

.END

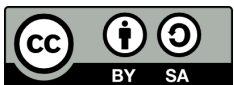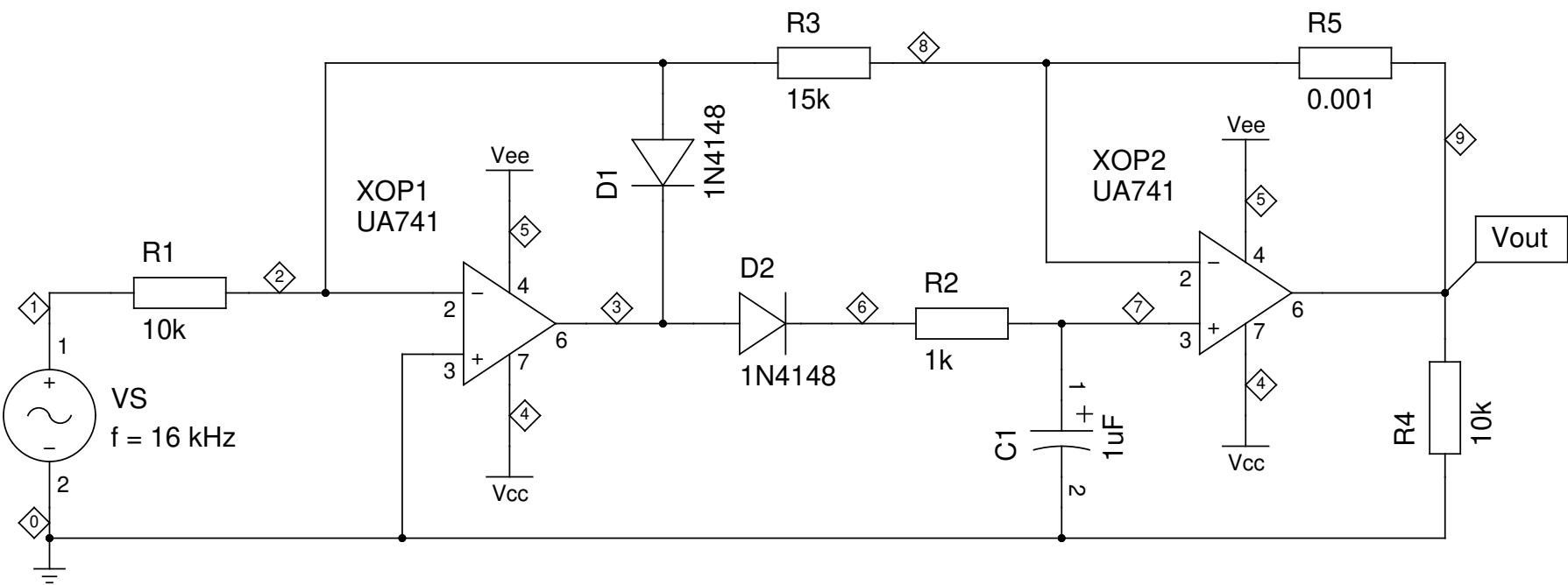

OCTAVE\_FILTER  
16 kHz Detector – Transient response (16 kHz)  
TITLE Schematic (DFS)

FILE: gnuicap/26.021.00.03.01.sch  
PAGE 01 OF 01

REVISION: 20240609  
DRAWN BY: Bert Timmerman

A3